

Design and Fabrication of a Radiation-Hard 500-MHz Digitizer Using Deep Submicron Technology

K.K. Gan

The Ohio State University

January 10, 2004

K.K. Gan, M.O. Johnson, R.D. Kass,
A. Rahimi, C. Rush
The Ohio State University

S. Smith
SLAC

Outline

- NLC Requirements
- ADC Design
- Progress Report
- Plans

Beam Position Monitor Requirements at NLC

- NLC will collide 180-bunch trains of e^- and e^+ :
 - bunch spacing: 1.4 ns
 - alignment of individual bunches in a train: $< 1 \text{ } \mu\text{m}$
 - BPM determines bunch-to-bunch misalignment
 - ⇒ high bandwidth kickers bring the train into better alignment on next machine cycle
 - ⇒ multi-bunch BPM system with digitizers:
 - ★ 11-bit effective resolution
 - ★ 500 MHz bandwidth
 - ★ 2 G samples/s

Requirements of NLC Digitizers


Function	Qty.	Resolution (eff. bits)	Bandwidth (MHz)	Comments
LLRF Control	13,000	11	100	Slightly beyond state-of-the-art
Structure BPM	22,000	8	5	Existing technology
“Qaud” BPM	10,000	11	12	Existing technology
Multi-bunch BPM	1,200	11	500	Well beyond state-of-the-art
Total	46,200			

- important to demonstrate feasibility of high speed/resolution digitizers
- ⇒ redesign of low level RF technology is needed without the digitizers

Proposal

- design a digitizer chip using deep-submicron technology (0.25 μ m)
 - use enclosed layout transistors and guard rings
 - ⇒ radiation hard: > 60 Mrad
 - ⇒ no need for costly shielding and long cables
 - ⇒ readily access to electronics for testing and maintenance
- extensive experience in chip design using Cadence
 - designed radiation-hard chips for CLEO III, ATLAS, CMS
- why OSU is interested?
 - help to solve a challenging NLC problem
 - potential applications in HEP
- 2002 Holtkamp Committee ranking: 2 on scale of 1 to 4 (lowest)
 - ⇒ funded for 2003-4

12-bit Pipelined Digitizer

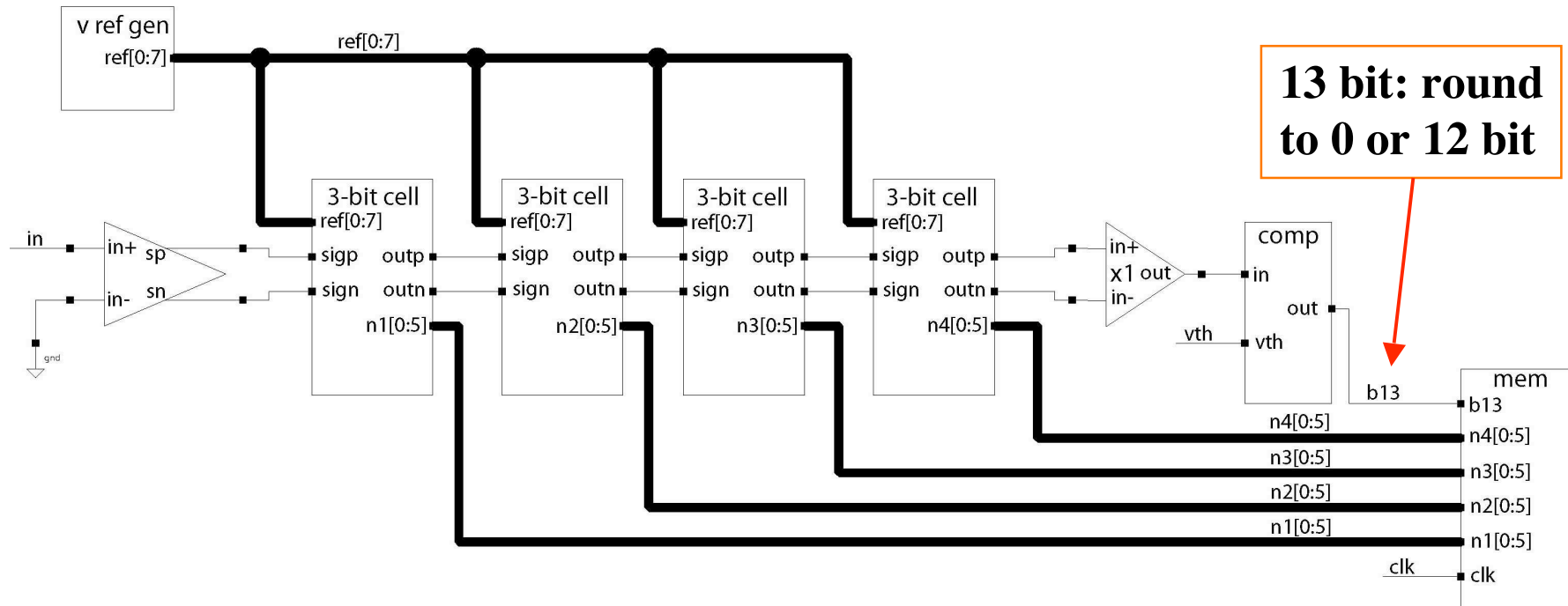

- input crudely digitized by 1st 3-bit cell
- ⇒ digitized value subtracted from input
- ⇒ difference is amplified by 8 and sent to 2nd 3-bit cell...

Digitizer for Multi-bunch BPM

- most challenging digitizer: 11 bit, 2 G samples/s, 500 MHz bandwidth
- input: sequence of doublets at 1.4 ns batch spacing
 - characterize with one parameter: pulse height
 - minimum sampling: $1/1.4 \text{ ns} = 714 \text{ MHz}$
 - ⇒ interleaving 3 digitizers for redundancy
 - ⇒ 2 G samples/s


Precision

- submicron CMOS supply voltage: 2.5 V
 - ⇒ differential signal: ~ 1.6 V full swing
 - ⇒ LSB: $1.6 \text{ V} / 2^{12} = 390 \text{ } \mu\text{V}$
 - ⇒ stability/accuracy of comparator thresholds, amplifier & S/H gains, charge injection:
 $195 \text{ } \mu\text{V} = 0.5 \text{ LSB} = 0.5 / 2^{12} = 0.012\%$


Fabrication Process

- gain-bandwidth requirement:
 - assume 0.7 ns for sample and 0.7 ns for hold
 - settling to 0.5 LSB for 12-bit digitizer requires $9 \times 0.5/2^{12} \sim e^{-9}$
 - ⇒ $\tau = 0.7 \text{ ns}/9 = 78 \text{ ps}$
 - ⇒ rise time = $2.2 \tau = 171 \text{ ps}$
 - ⇒ gain x bandwidth = $8 \times 1/2\tau = 16.4 \text{ GHz}$
 - ⇒ IBM process SiGe BiCMOS 6HP/6DM via MOSIS:
40 GHz NPN bipolar transistors

3-Bit Cell

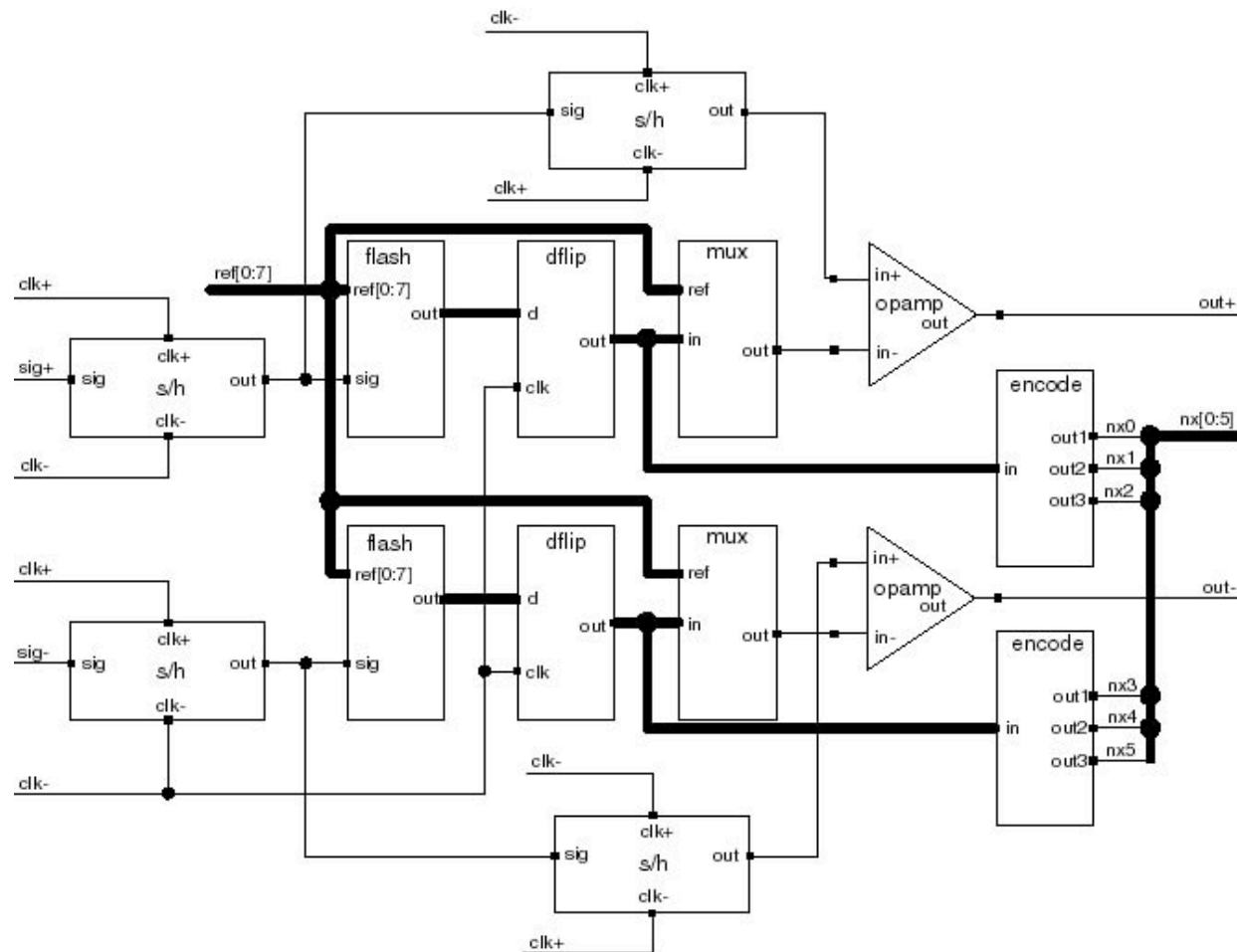


3-Bit Cell Status

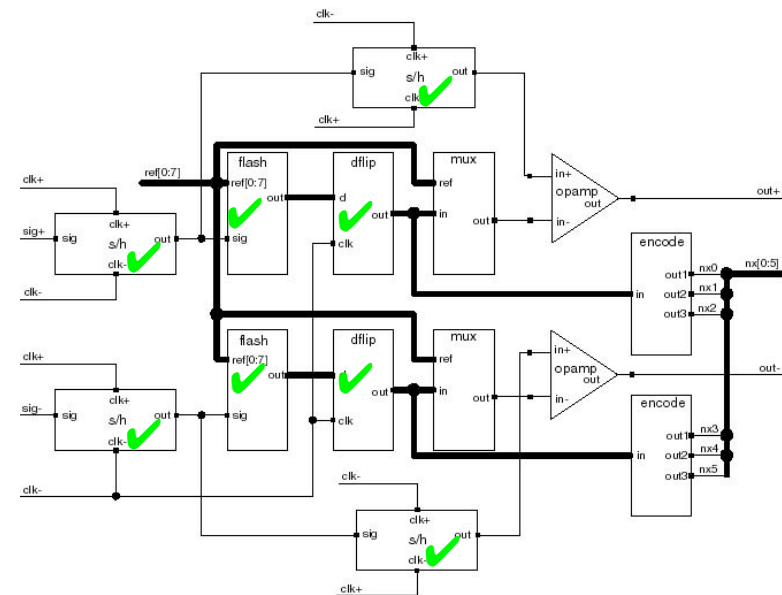

- simulated with Cadence
 - ✓ sample/hold + flash ADC/flip-flop:
designed/simulated from schematic with parasitic capacitances
 - multiplexer: logic is fast but somewhat noisy
 - op-amp + encoder: still use ideal devices in simulation


Sample/Hold Status

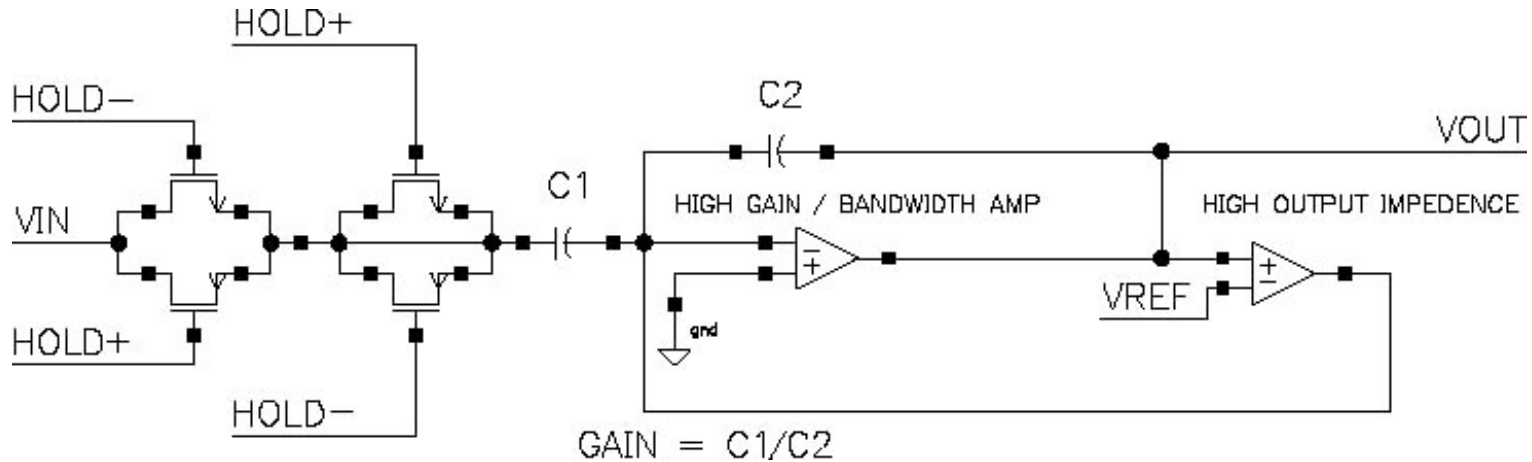


- design and simulated from schematic with parasitic capacitances
 - ✓ switch-on resistance small enough to allow 90° in 700 ps
 - ✓ switching offset (noise) largely cancelled with dummy switch:
 - 100 mV ⇒ 1 mV

Cadence Simulation of Sample/Hold

Amplifier: ideal

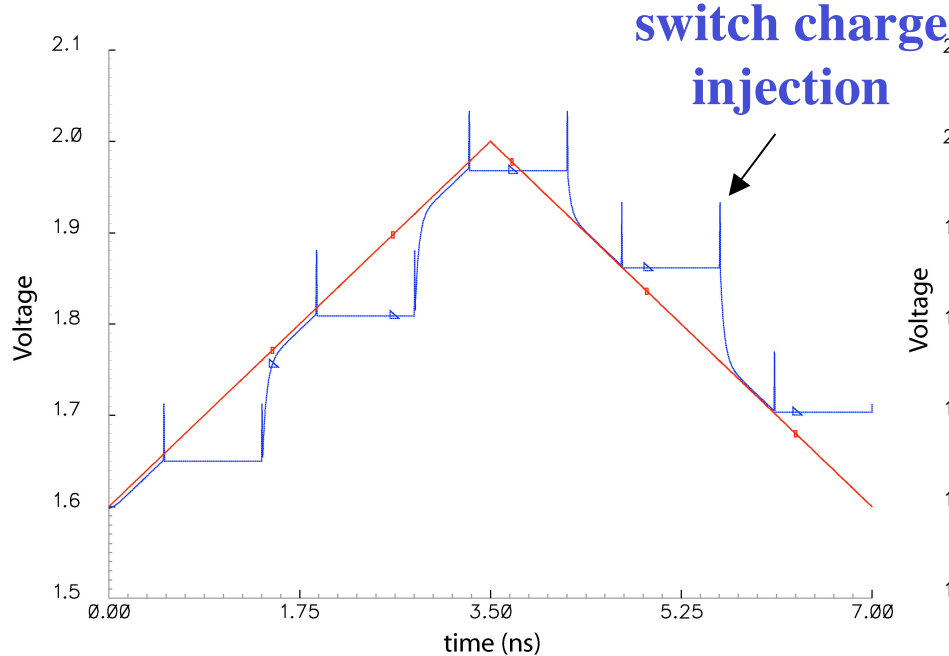

Amplifier: current design

 


- amplifier signal not yet settle to 0.5 LSB in 0.7 ns

Simulation of Amplifier

- rise time: 186 ps
- goal: 171 ps:
- precision at 0.7 ns:
 
$$\frac{298 \text{ } \mu\text{V}}{270 \text{ mV}} \approx 2^{-10}$$
- ⇒ need 4x improvement for 12-bit precision



Plans

- Year 2003-4:
 - complete design of amplifier + 3-bit cell
- Year 2004-5:
 - layout, submission, and testing of the building block circuits
 - radiation hardness tests
 - continued system design of a prototype 11-bit digitizer