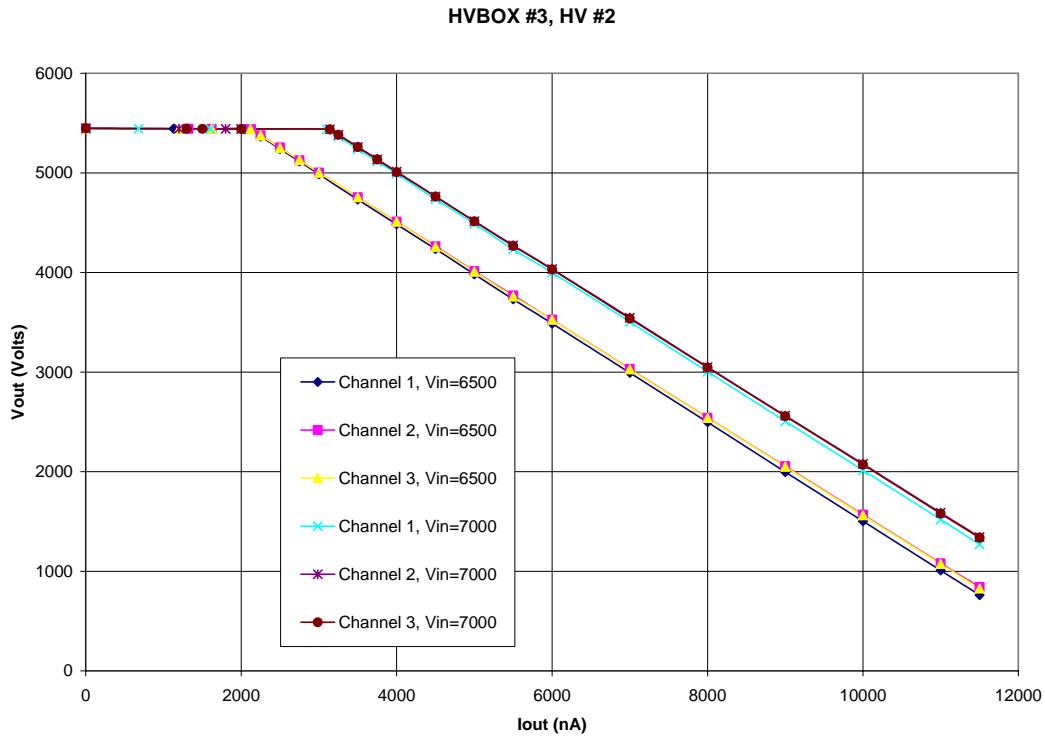


Quick Reminder: Automatic Current Limit (aka ZEUS Circuit)

- Each output channel has built in over current protection.
- As the current increases the output voltage is reduced to prevent damage to the LST tube



- The limit circuit kicks in when the current increases beyond
 $I_{Knee} = (HV_{Brick} - HV_{Set}) / 500M\Omega$
- Current configuration: $HV_{Brick} - HV_{Set} = 1000 \text{ V} \rightarrow I_{Knee} = 2000 \text{ nA}$
- Possible adjustments
 - max output Voltage (Ultravolt module) 10 KV
 - max internal voltage (resistor divider) 7.5 KV
 - max HV_{Brick} (low bits of DAC set to 0) 7.3 KV
 - max I_{Knee} with $HV_{Set} = 5.5 \text{ KV}$ 3600 nA
- Proposal
 - Set HV_{Brick} to $HV_{Set} + 1500 \text{ V}$
 - I_{Knee} (at 5.5 KV) = 3000 nA
 - Passed 100 hrs test at OSU