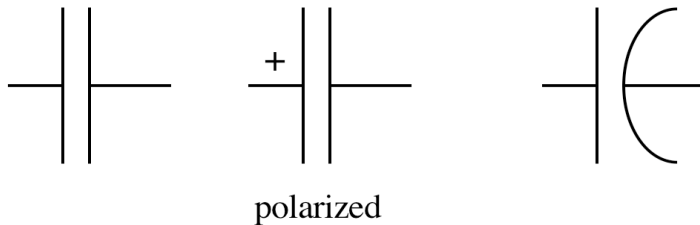


## Lecture 2: Resistors and Capacitors

### Capacitance:

- Capacitance ( $C$ ) is defined as the ratio of charge ( $Q$ ) to voltage ( $V$ ) on an object:
  - ◆  $C = Q/V = \text{Coulombs/Volt} = \text{Farad}$
  - ◆ Capacitance of an object depends on geometry and its dielectric constant.
  - ◆ Symbol(s) for capacitors:




- ◆ A capacitor is a device that stores electric charge (memory devices).
- ◆ A capacitor is a device that stores energy

$$E = \frac{Q^2}{2C} = \frac{CV^2}{2}$$


- ◆ Capacitors are easy to fabricate in small sizes ( $\mu\text{m}$ ), use in chips

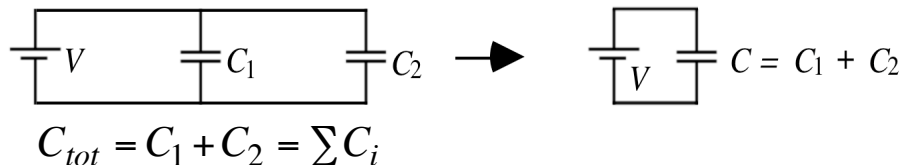- How to combine capacitance:
  - ◆ capacitors in parallel adds like resistors in series:



*Total capacitance is more than individual capacitance!*

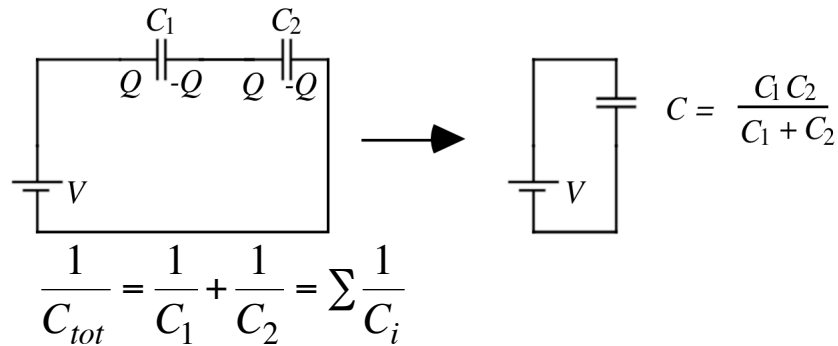- ♦ capacitors in series add like resistors in parallel:



*Total capacitance is less than individual capacitance!*

- Energy and Power in Capacitors

- ♦ How much energy can a "typical" capacitor store?

- Pick a 4  $\mu\text{F}$  Cap (it would read 4 mF) rated at 3 kV

$$E = \frac{1}{2} CV^2 = \frac{1}{2} 4 \times 10^{-6} \cdot 3000^2 = 18 \text{ J}$$

- This is the same as dropping a 2 kg weight (about 4 pounds) 1 meter

- ♦ How much power is dissipated in a capacitor?

$$\text{Power} = \frac{dE}{dt}$$

$$= \frac{d}{dt} \left( \frac{CV^2}{2} \right)$$

$$P = CV \frac{dV}{dt}$$

- $dV/dt$  must be finite otherwise we source (or sink) an infinite amount of power!

THIS WOULD BE UNPHYSICAL.

- the voltage across a capacitor cannot change instantaneously
  - ☞ a useful fact when trying to guess the transient (short term) behavior of a circuit
- the voltage across a resistor can change instantaneously
  - ☐ the power dissipated in a resistor does not depend on  $dV/dt$ :  

$$P = I^2 R \text{ or } V^2/R$$

◆ Why do capacitors come in such small values?

- Example: Calculate the size of a 1 Farad parallel capacitor with air between the plates.

$$C = \frac{k\epsilon_0 A}{d}$$

$k$  = dielectric constant (= 1 for air)

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ N}^{-1} \text{ m}^{-2}$$

$d$  = distance between plates (assumed 1 mm)

$$A = \text{area of plates} = 1.1 \times 10^8 \text{ m}^2 !!!$$


☞ square plate of 6.5 miles per side

☐ breakthroughs in capacitor technologies (driven by the computer industries)

☞ fabrication of 0.5-5 F capacitors of small size (1-2 cm high) and low cost (< \$5)

◆ How small can we make capacitors?

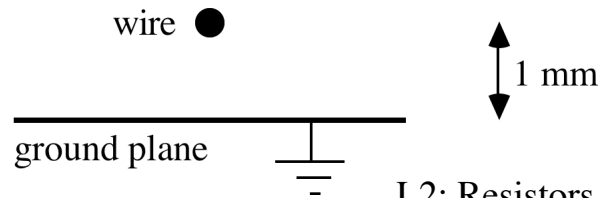- A wire near a ground plane has  $C \sim 0.1 \text{ pf} = 10^{-13} \text{ F}$ .



- ◆ Some words to the wise on capacitors and their labeling.
  - Typical capacitors are multiples of micro Farads ( $10^{-6}$  F) or picoFarads ( $10^{-12}$  F).
    - ☞ Whenever you see mF it almost always is micro, *not* milli F and *never* mega F.
    - ☞ picoFarad ( $10^{-12}$  F) is sometimes written as pf and pronounced *puff*.
  - no *single* convention for labeling capacitors
    - Many manufacturers have their own labeling scheme (See Horowitz and Hill lab manual).
- Resistors and Capacitors
  - ◆ Examine voltage and current vs. time for a circuit with one  $R$  and one  $C$ .
    - Assume that at  $t < 0$  all voltages are zero,  $V_R = V_C = 0$ .
    - At  $t \geq 0$  the switch is closed and the battery ( $V_0$ ) is connected.
    - Apply Kirchhoff's voltage rule:

$$V_0 = V_R + V_C$$

$$= IR + \frac{Q}{C}$$


$$= R \frac{dQ}{dt} + \frac{Q}{C}$$

- Solve the differential equation by differentiating both sides of above equation:

$$\frac{dV_0}{dt} = \frac{1}{C} \frac{dQ}{dt} + R \frac{d^2Q}{dt^2}$$

$$0 = \frac{I}{C} + R \frac{dI}{dt}$$

$$\frac{dI}{dt} = -\frac{I}{RC}$$

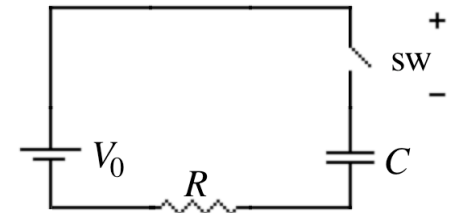

- This is just an exponential decay equation with time constant  $RC$  (sec).
- The current as a function of time through the resistor and capacitor is:

$$I(t) = I_0 e^{-t/RC}$$

◆ What's  $V_R(t)$ ?


- By Ohm's law:

$$V_R(t) = I_R \cdot R$$

$$= I_0 R e^{-t/RC}$$

$$= V_0 e^{-t/RC}$$

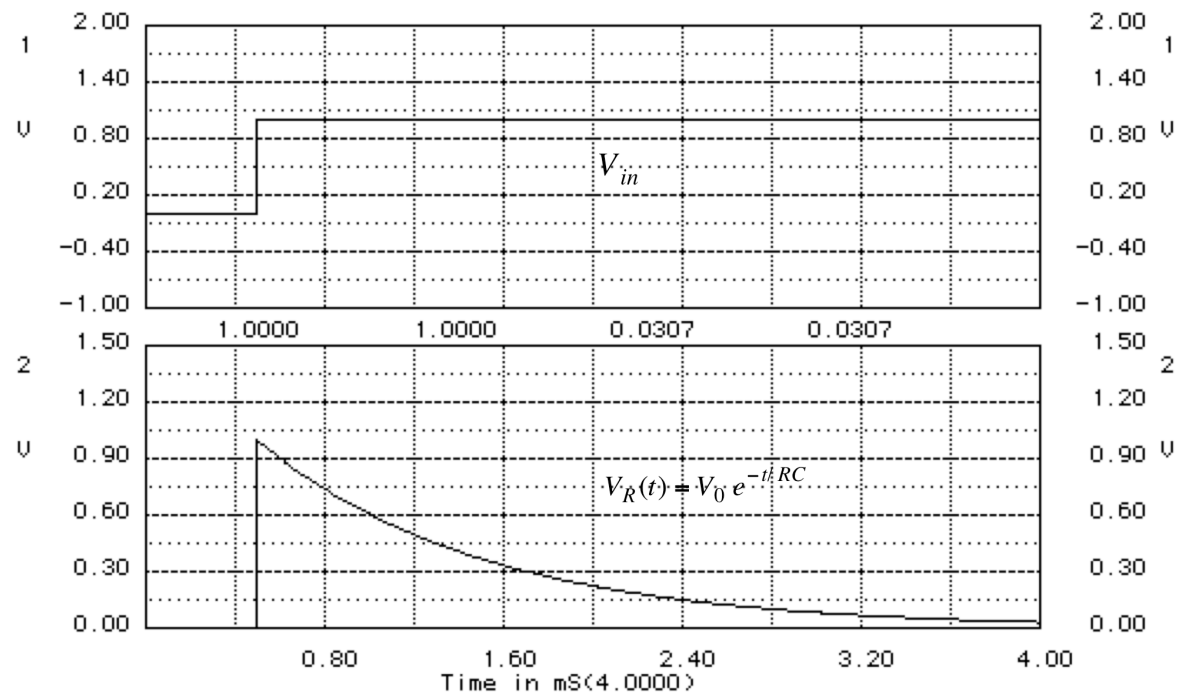- At  $t = 0$  all the voltage appears across the resistor,  $V_R(0) = V_0$ .
- At  $t = \infty$ ,  $V_R(\infty) = 0$ .



◆ What's  $V_C(t)$ ?

- Easiest way to answer is to use the fact that  $V_0 = V_R + V_C$  is valid for all  $t$ .

$$V_C = V_0 - V_R$$

$$V_C = V_0(1 - e^{-t/RC})$$

- ☞ At  $t = 0$  all the voltage appears across the resistor so  $V_C(0) = 0$ .

- ☞ At  $t = \infty$ ,  $V_C(\infty) = V_0$ .

◆ Suppose we wait until  $I = 0$  and then short out the battery.

$$0 = V_R + V_C$$

$$V_R = -V_C$$

$$R \frac{dQ}{dt} = -\frac{Q}{C}$$

$$\frac{dQ}{dt} = -\frac{Q}{RC}$$

- Solving the exponential equation yields,


$$Q(t) = Q_0 e^{-t/RC}$$

- We can find  $V_C$  using  $V = Q/C$ ,

$$V_C(t) = V_0 e^{-t/RC}$$

- Finally we can find the voltage across the resistor using  $V_R = -V_C$ ,

$$V_R(t) = -V_0 e^{-t/RC}$$

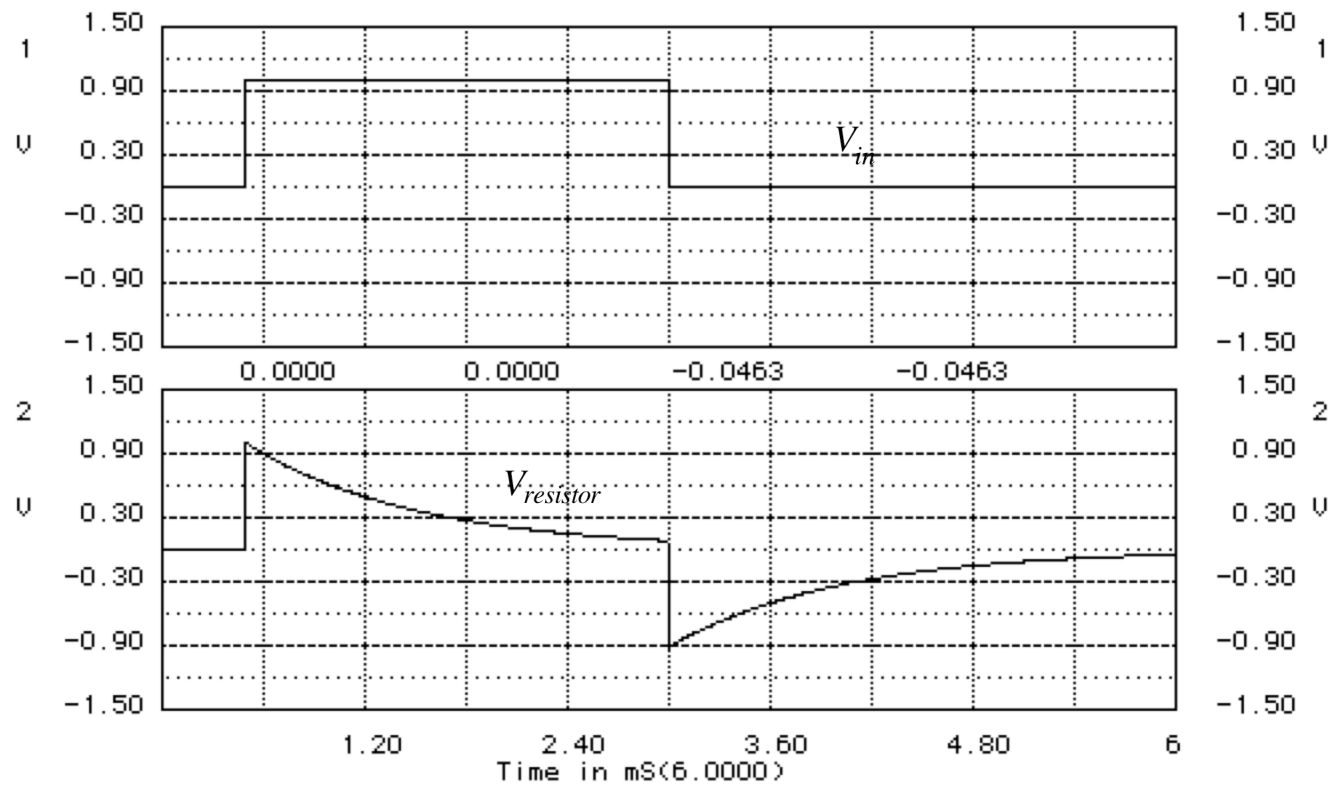

- Suppose  $V_C(t) = V_0 \sin \omega t$  instead of DC

What happens to  $V_C$  and  $I_C$ ?

$$Q(t) = CV(t)$$

$$= CV_0 \sin \omega t$$

$$I_C = dQ/dt$$

$$= \omega CV_0 \cos \omega t$$

$$= \omega CV_0 \sin(\omega t + \pi/2)$$

current in capacitor varies like a sine wave too, but  $90^\circ$  out of phase with voltage.

- We can write an equation that looks like Ohm's law by defining  $V^*$ :

$$V^* = V_0 \sin(\omega t + \pi/2)$$

- ☞ the relationship between the voltage and current in  $C$  looks like:

$$V^* = I_C / \omega C$$

$$= I_C R^*$$

- ☞  $1/\omega C$  can be identified as a kind of resistance, capacitive reactance:

$$X_C \equiv 1/\omega C \text{ (Ohms)}$$

- $X_C = 0$  for  $\omega = \infty$

- ☞ high frequencies: a capacitor looks like a short circuit

- $X_C = \infty$  for  $\omega = 0$


- ☞ low frequencies: a capacitor looks like an open circuit (high resistance).

## Inductance:

- Define inductance by:  $V = L di/dt$

- ◆ Unit: Henry

- ◆ Symbol:

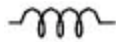

- ◆ Inductors are usually made from a coil of wire

- tend to be bulky and are hard to fabricate in small sizes ( $\mu\text{m}$ ), not used in chips.

- ◆ Two inductors next to each other (transformer) can step up or down a voltage

- no change in the frequency of the voltage

- provide isolation from the rest of the circuit



- How much energy is stored in an inductor?

$$dE = VdQ$$

$$I = \frac{dQ}{dt}$$

$$dE = VIdt$$

$$V = L \frac{dI}{dt}$$

$$dE = LI dI$$

$$E = L \int_0^I IdI$$

$$E = \frac{1}{2} LI^2$$

- How much power is dissipated in an inductor?

$$Power = \frac{dE}{dt}$$

$$= \frac{d}{dt} \left( \frac{LI^2}{2} \right)$$


$$P = LI \frac{dI}{dt}$$

- $dI/dt$  must be finite as we can't source (or sink) an infinite amount of power in an inductor!

THIS WOULD BE UNPHYSICAL.

the *current* across an inductor cannot change *instantaneously*.

- ◆ Two inductors in series:

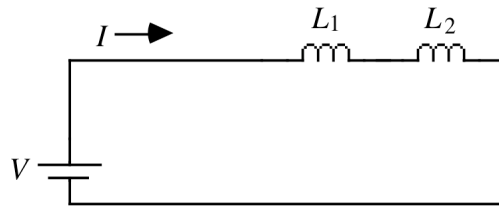

- Apply Kirchhoff's Laws,

$$V = V_1 + V_2$$

$$= L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt}$$

$$\equiv L_{tot} \frac{dI}{dt}$$


$$L_{tot} = L_1 + L_2$$

$$= \sum L_i$$

- ☞ Inductors in series add like resistors in series.

The *total* inductance is *greater* than the individual inductances.

- ◆ Two inductors in parallel:

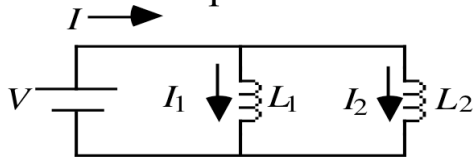

- Since the inductors are in parallel,

$$V_1 = V_2 = V$$

- The total current in the circuit is

$$I = I_1 + I_2$$

$$\frac{dI}{dt} = \frac{dI_1}{dt} + \frac{dI_2}{dt}$$

$$= \frac{V}{L_1} + \frac{V}{L_2}$$

$$\equiv \frac{V}{L_{tot}}$$

$$\frac{1}{L_{tot}} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$L_{tot} = \frac{L_1 L_2}{L_1 + L_2}$$

- ☞ If we have more than 2 inductors in parallel, they combine like:

$$\frac{1}{L_{tot}} = \sum \frac{1}{L_i}$$


- ☐ Inductors in parallel add like resistors in parallel.

The *total* inductance is *less* than the individual inductances.

- Resistors and Inductors

- ◆ Examine voltage and current versus time for a circuit with one  $R$  and one  $L$ .

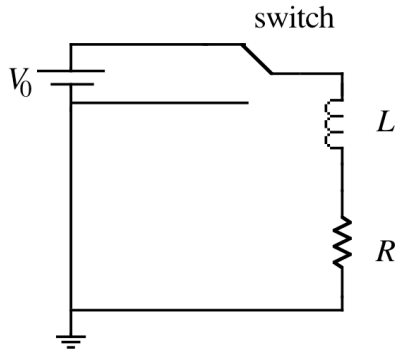- Assume that at  $t < 0$  all voltages are zero,  $V_R = V_L = 0$ .
- At  $t \geq 0$  the switch is closed and the battery ( $V_0$ ) is connected.



- Like the capacitor case, apply Kirchhoff's voltage rule:

$$\begin{aligned} V_0 &= V_R + V_L \\ &= IR + L \frac{dI}{dt} \end{aligned}$$

- Solving the differential equation, assuming at  $t = 0$ ,  $I = 0$ :

$$I(t) = \frac{V_0}{R} \left( 1 - e^{-tR/L} \right)$$

☞ This is just an exponential decay equation with time constant  $L/R$  (seconds).

- ◆ What's  $V_R(t)$ ?

- By Ohm's law  $V_R = I_R R$  at any time:

$$V_R = I(t)R = V_0 \left( 1 - e^{-tR/L} \right)$$

- At  $t = 0$ , none of the voltage appears across the resistor,  $V_R(0) = 0$ .
- At  $t = \infty$ ,  $V_R(\infty) = V_0$ .

◆ What's  $V_L(t)$ ?


- Easiest way to answer is to use the fact that  $V_0 = V_R + V_L$  is valid for all  $t$ .

$$V_L = V_0 - V_R$$

$$V_L(t) = V_0 e^{-tR/L}$$

- At  $t = 0$ , all the voltage appears across the inductor so  $V_L(0) = V_0$ .
- At  $t = \infty$ ,  $V_L(\infty) = 0$ .

Pick  $L/R = 1$  ms

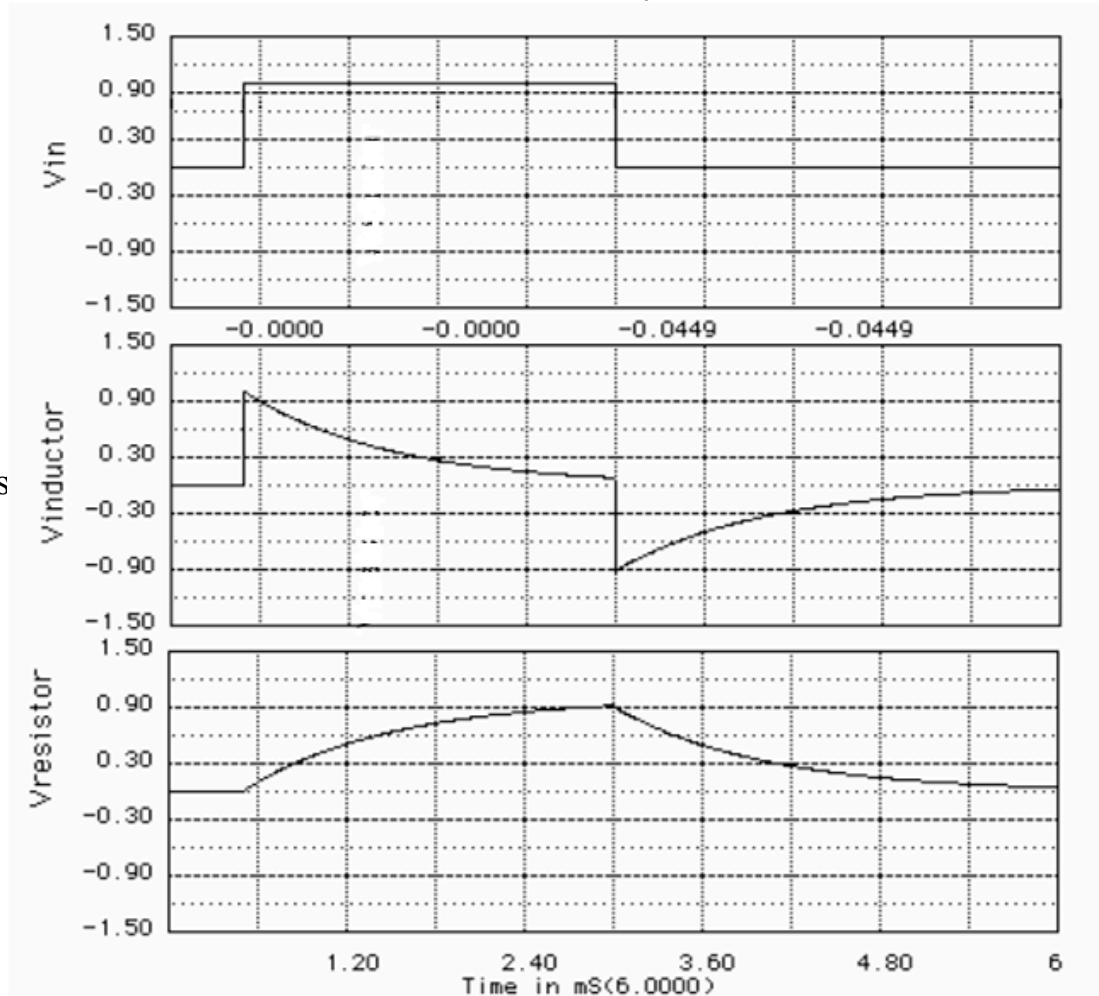

- ◆ Suppose  $V_C(t) = V_0 \sin \omega t$  instead of DC, what happens to  $V_L$  and  $I_L$ ?

$$V = L \frac{dI_L}{dt}$$

$$I_L = \frac{1}{L} \int_0^t V dt$$

$$= -\frac{V_0}{\omega L} \cos \omega t$$

$$I_L(t) = \frac{V_0}{\omega L} \sin(\omega t - \pi/2)$$

- ☞ The current in an inductor varies like a sine wave too, but  $90^\circ$  out of phase with the voltage.

- We can write an equation that looks like Ohm's law by defining  $V^*$ :

$$V^* = V_0 \sin(\omega t - \pi/2)$$

- ☞  $V^* = I_L \omega L = I_L R^*$

- $\omega L$  can be identified as a kind of resistance, inductive reactance:

$$X_L \equiv \omega L \text{ (Ohms)}$$


- $X_L = 0$  if  $\omega = 0$


- ☞ low frequencies: an inductor looks like a short circuit (low resistance).

- $X_L = \infty$  if  $\omega = \infty$

- ☞ high frequencies: an inductor looks like an open circuit.

- Some things to remember about  $R$ ,  $L$ , and  $C$ 's.
  - ◆ For DC circuits, after many time constants ( $L/R$  or  $RC$ ):
    - ☞ Inductor acts like a wire ( $0\ \Omega$ ).
    - ☞ Capacitor acts like an open circuit ( $\infty\ \Omega$ ).
  - ◆ For circuits where the voltage changes very rapidly or transient behavior:
    - ☞ Capacitor acts like a wire ( $0\ \Omega$ ).
    - ☞ Inductor acts like an open circuit ( $\infty\ \Omega$ ).
  - ◆ Example, RLC circuit with DC supply:
    - At  $t = 0$ , voltages on  $R$ ,  $C$  are zero and  $V_L = V_0$ .
    - At  $t = \infty$ , voltages on  $R$ ,  $L$  are zero and  $V_C = V_0$ .

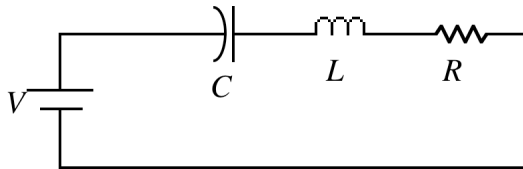

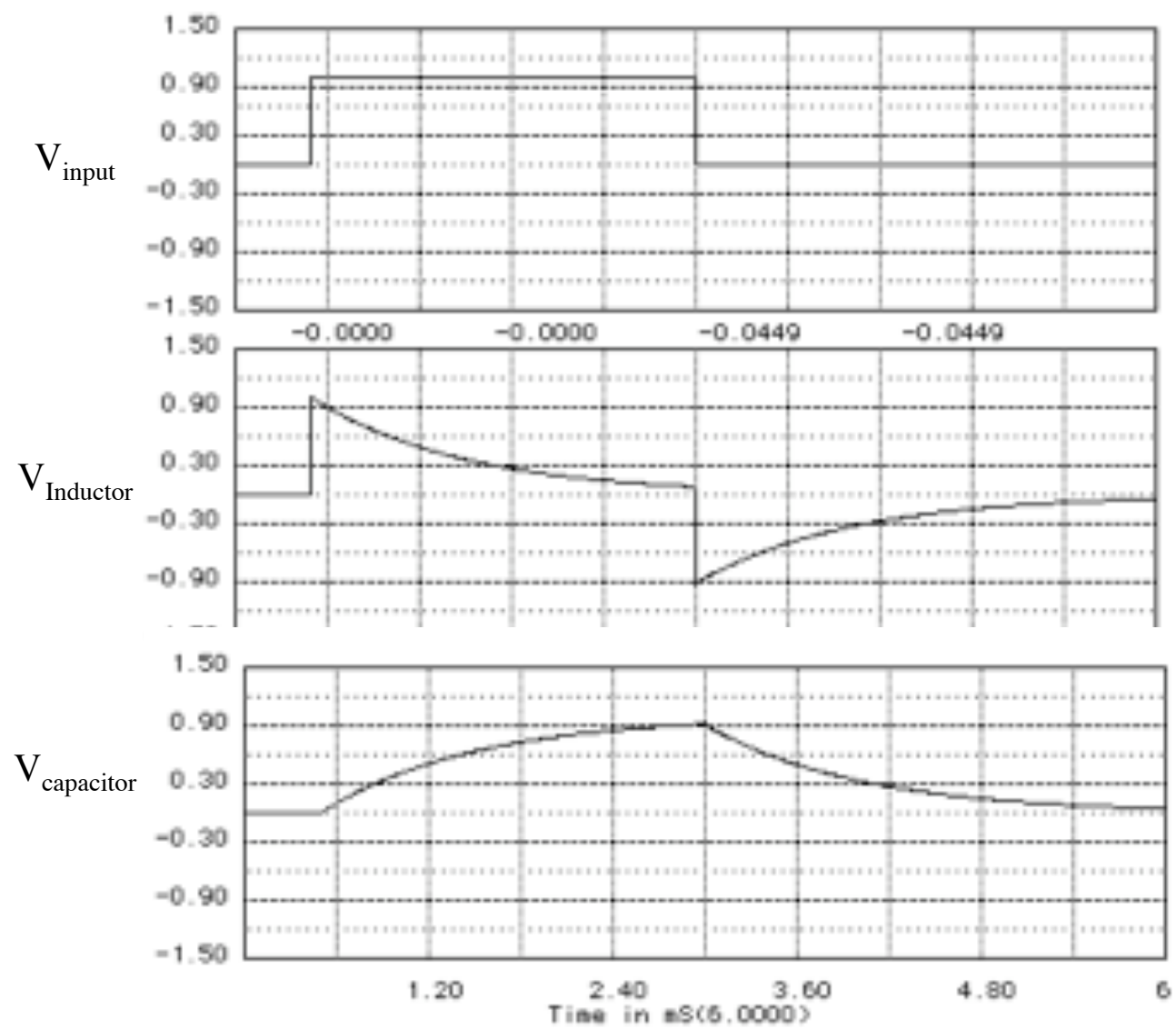

L2: Resistors and Capacitors