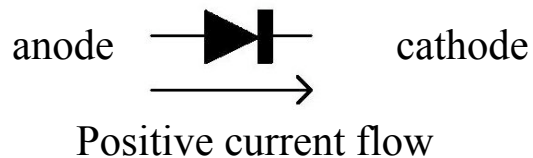


Lecture 5: Diodes and Transistors


Diodes:

- What do we use diodes for?
 - protect circuits by limiting the voltage (clipping and clamping)
 - turn AC into DC (voltage rectifier)
 - voltage multipliers (e.g. double input voltage)
 - non-linear mixing of two voltages (e.g. amplitude modulation)



Diode conducts when
 $V_{\text{anode}} > V_{\text{cathode}}$

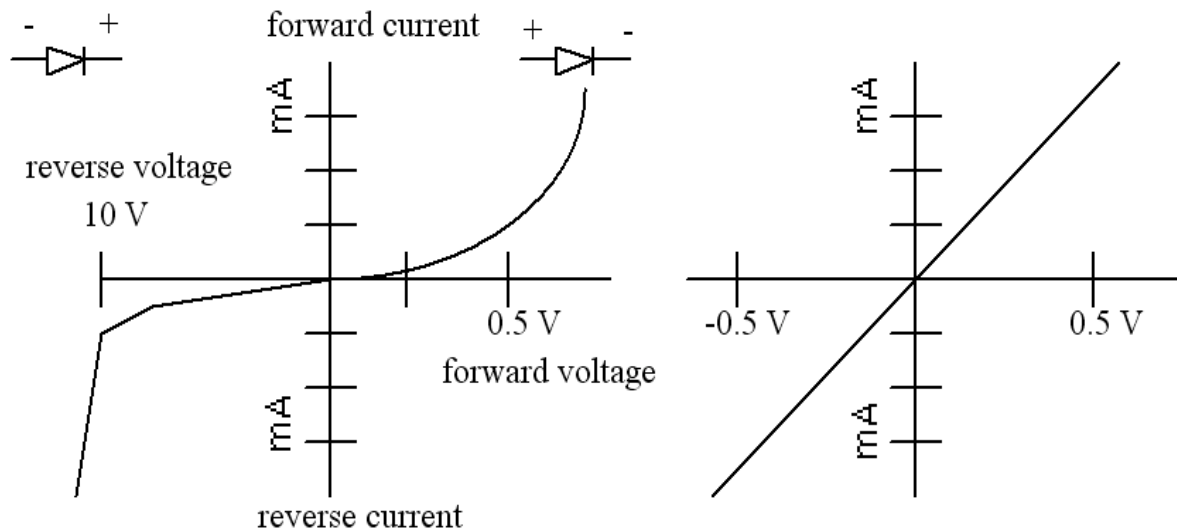- Diodes (and transistors) are non-linear device: $V \neq IR$!



- ◆ Diode is **forward** biased when $V_{\text{anode}} > V_{\text{cathode}}$.
 - Diode conducts current strongly
 - Voltage drop across diode is (almost) independent of diode current
 - Effective resistance (impedance) of diode is small
- ◆ Diode is **reverse** biased when $V_{\text{anode}} < V_{\text{cathode}}$.
 - Diode conducts current very weakly (typically $< \mu\text{A}$)
 - Diode current is (almost) independent of voltage, until breakdown
 - Effective resistance (impedance) of diode is very large
- ◆ Current-voltage relationship for a diode:


$$I = I_s (e^{eV/kT} - 1)$$
 - "diode", "rectifier", or "Ebers-Moll" equation
 - I_s = reverse saturation current (typically $< \mu\text{A}$)
 - k = Boltzmann's constant, e = electron charge, T = temperature
 - At room temperature, $kT/e = 25.3 \text{ mV}$,

$$I = I_s e^{39V} \quad \text{if } V > 0$$

$$I = -I_s \quad \text{if } V < 0.$$
- ◆ Effective resistance of forward biased diode ($V > 0$):


$$dV/dI = (kT/e)/I \approx 25 \text{ } \Omega/I, I \text{ in mA}$$

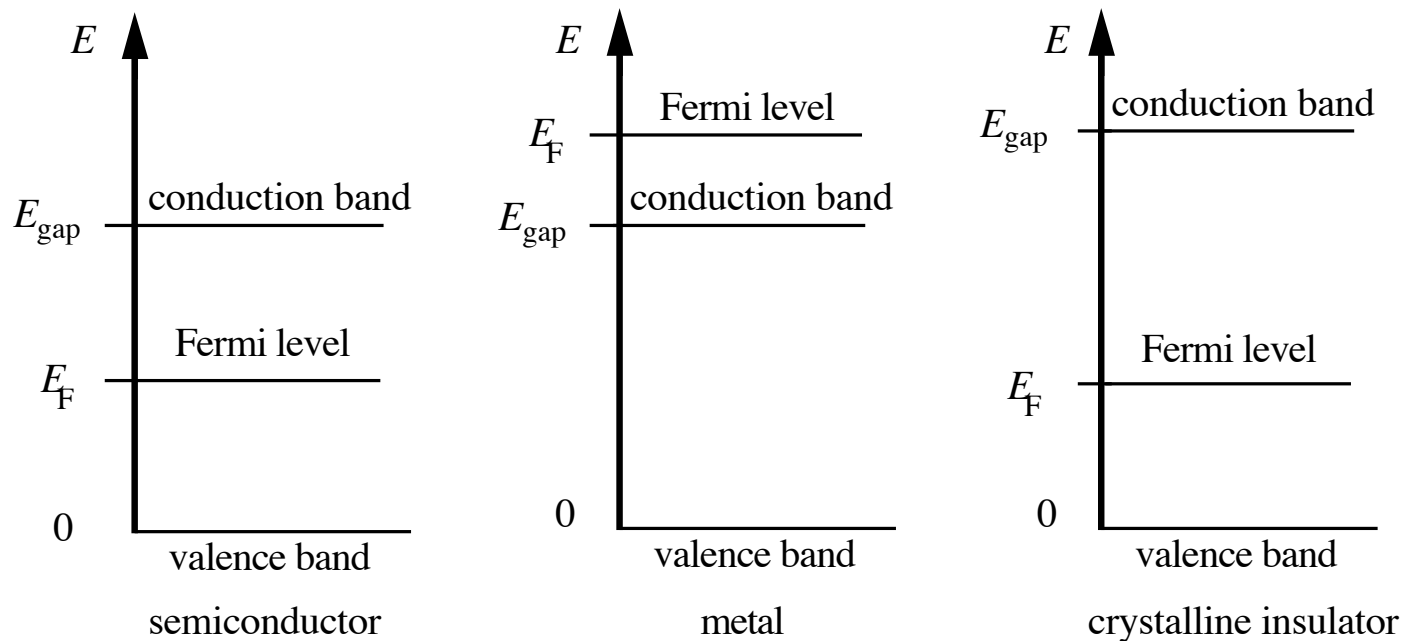- What's a diode made out of?
 - ◆ Semiconductors!
 - ◆ The energy levels of a semiconductor can be modified
 - 👉 a material (e.g. silicon or germanium) that is normally an insulator will conduct electricity.
 - ◆ Energy level structure of a semiconductor is complicated, requires quantum mechanical treatment.




| Material | Example | Resistivity ($\Omega\text{-cm}$) |
|-----------------|----------------|--|
| Conductor | Copper | 1.56×10^{-6} |
| Semiconductor | Silicon | $10^3\text{-}10^6$ |
| Insulator | Ceramics | $10^{11}\text{-}10^{14}$ |


- How do we turn a semiconductor into a conductor?
 - ◆ *Dope it!*
 - ◆ Doping is a process where impurities are added to the semiconductor to lower its resistivity
 - ◆ Silicon has 4 electrons in its valence level
 - ◆ We add atoms with 3 or 5 valence shell electrons to a piece of silicon.
 - Phosphorous, Arsenic, Antimony have 5 valence electrons
 - Boron, Aluminum, Indium have 3 valence electrons
- N type silicon:
 - ◆ Adding atoms which have 5 valence electrons makes the silicon more negative.
 - ◆ The majority carriers are the excess electrons.
- P type silicon
 - ◆ Adding atoms which have 3 valence electrons makes the silicon more positive.
 - ◆ The majority carriers are "holes".
 - A hole is the lack of an electron in the valence shell.

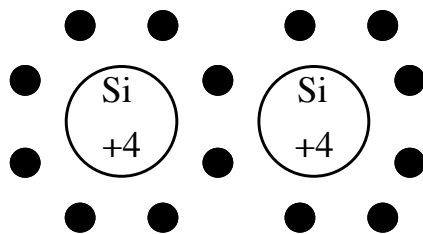

Normal Silicon

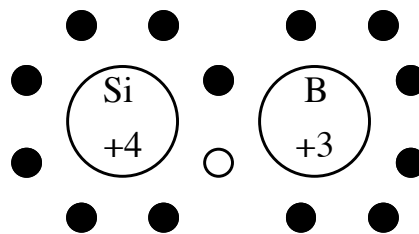


P Type Silicon

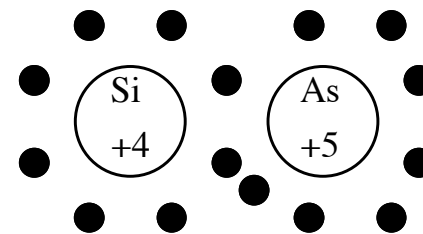

N Type Silicon

- How do we make a diode?
 - Put a piece of N type silicon next to a piece of P type silicon.


- Unbiased diode

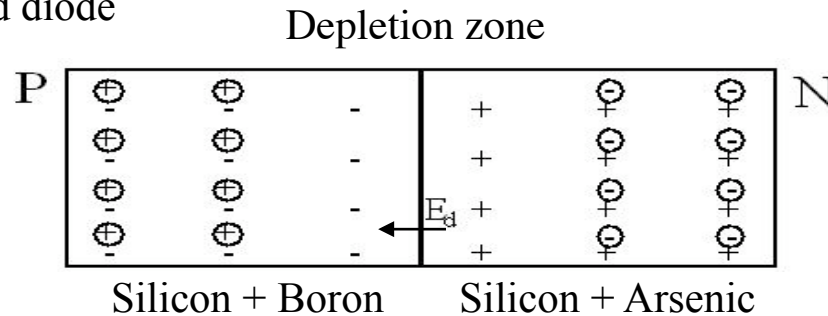

Very small leakage current


- \ominus mobile electron
- \oplus mobile hole
- fixed ionized acceptor atom
- + fixed ionized doner atom

- Forward biased diode

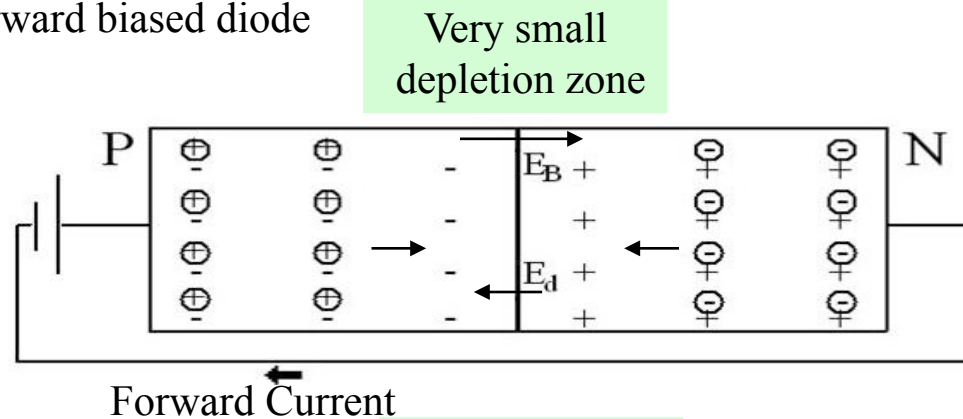

Barrier due to depletion region very small
→ large current can flow

- Reversed biased diode


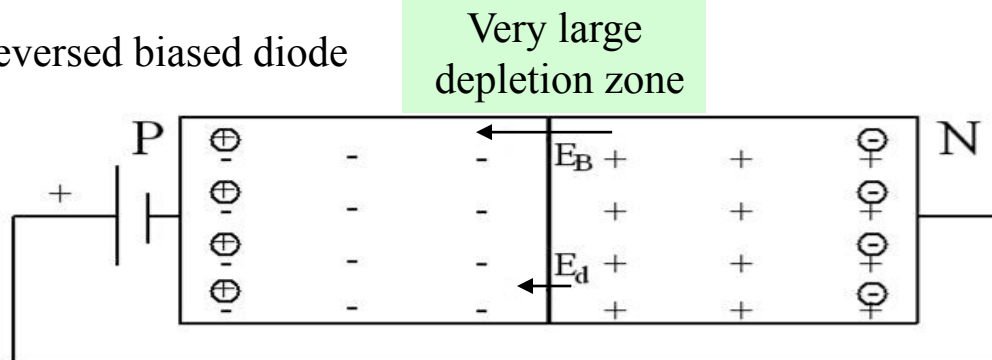


Barrier due to depletion region very large
→ small leakage current

- diode characteristics
 - ◆ reverse voltage and current
 - ◆ peak current and voltage
 - ◆ capacitance
 - ◆ recovery time
 - ◆ sensitivity to temperature
- types of diodes
 - ◆ junction diode (ordinary type)
 - ◆ light emitting (LED)
 - ◆ photodiodes (absorbs light, gives current)
 - ◆ Schottky (high speed switch, low turn on voltage, Al. on Silicon)
 - ◆ tunnel (I vs. V slightly different than jd's, negative resistance!)
 - ◆ varactor (junction capacitance varies with voltage)
 - ◆ zener (special junction diode, use reversed biased)

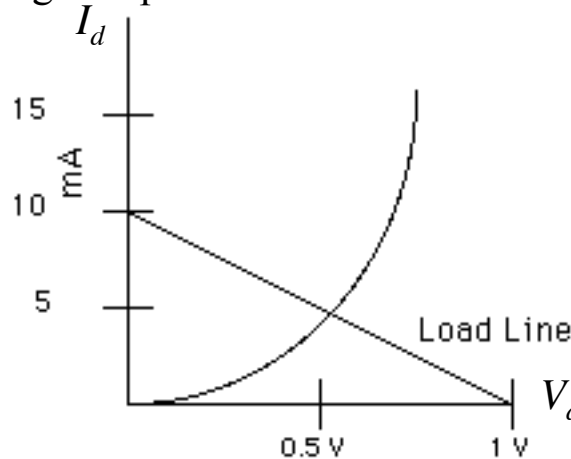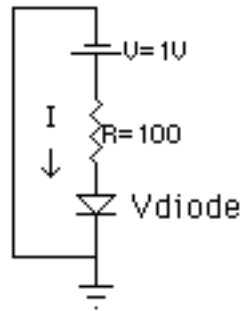- Examples of Diode Circuits

- ◆ Simplest Circuit: What's voltage drop across diode?



- ◆ In diode circuits we still use Kirchhoff's law:

$$V_{in} = V_d + I_d R$$

$$I_d = V_{in}/R - V_d/R$$


- ◆ For this circuit I_d vs. V_d is a straight line with the following limits:

$$V_d = 0 \Rightarrow I_d = V_{in}/R = 10 \text{ mA}$$


$$V_d = 1 \text{ V} \Rightarrow I_d = 0$$

- The straight line (load line) is all possible (V_d, I) for the **circuit**.
- The diode curve is all possible (V_d, I) for the **diode**.
- The place where these two lines intersect gives the actual voltage and current for this circuit.

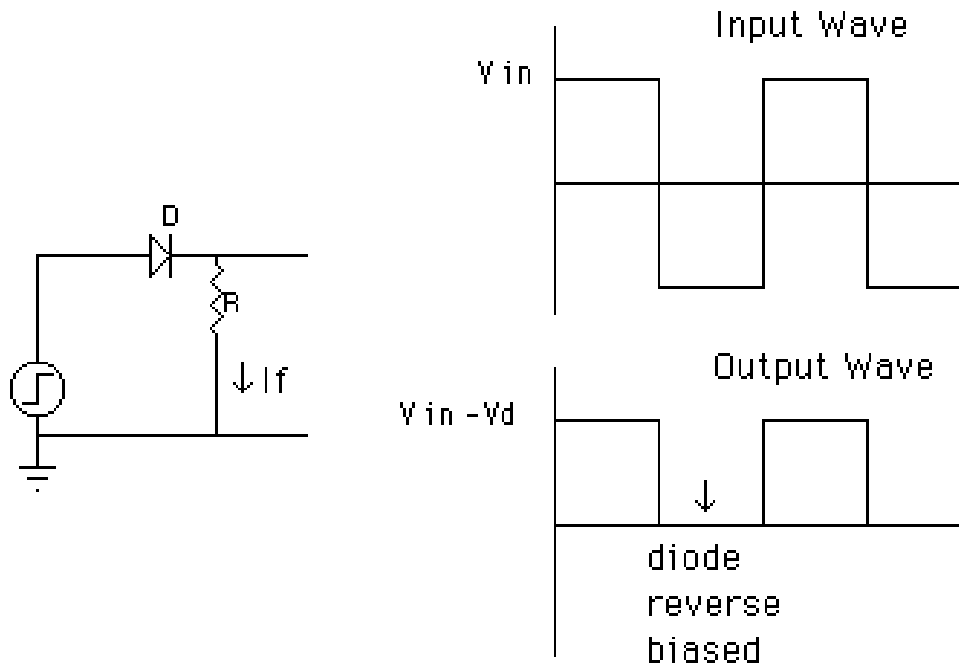- Diode Protection (clipping and clamping)
 - ◆ The following circuit will get rid of the negative part of the input wave.
 - ◆ When the diode is negative biased, no current can flow in the resistor, so $V_{out} = 0$.




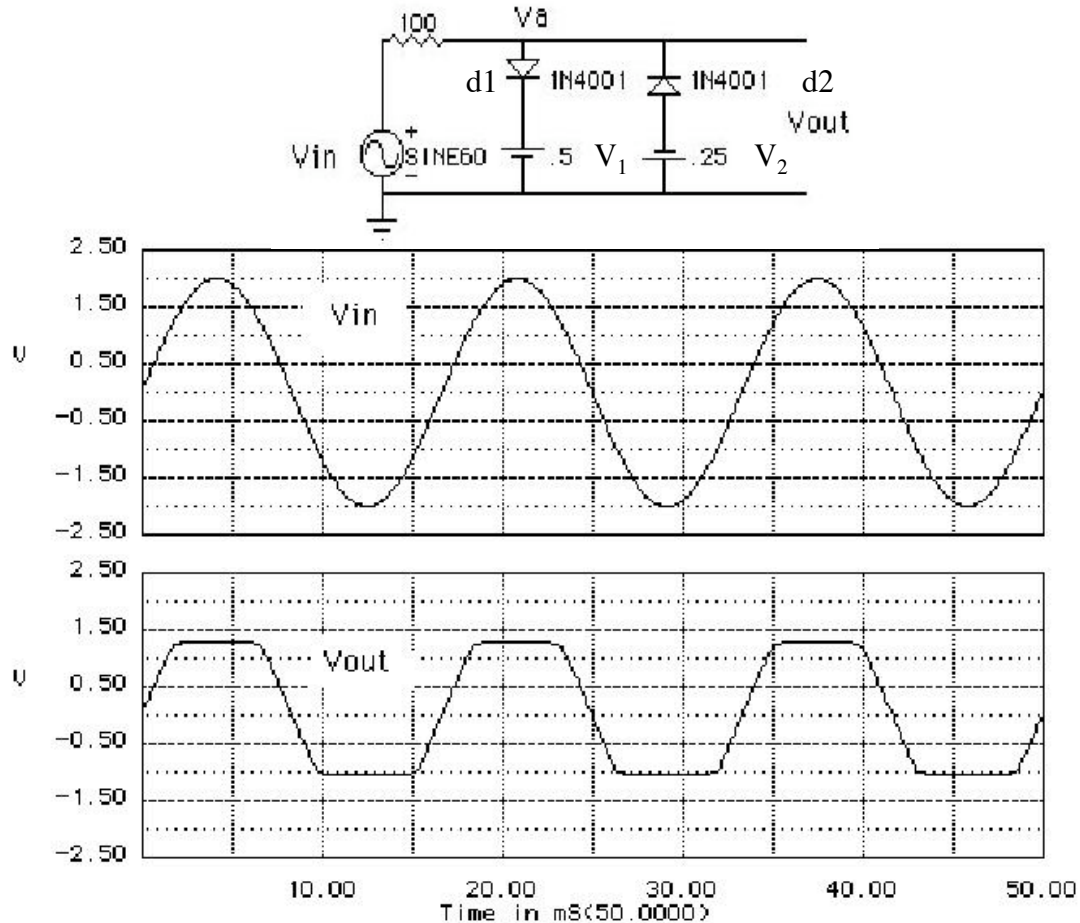- For more protection consider the following "clipping" circuit: for silicon $V_d \approx 0.6\text{-}0.7\text{ V}$




- ◆ If $V_a > V_{d1} + V_1$, then diode 1 conducts so $V_{out} \leq V_{d1} + V_1$.
- ◆ If $V_a < -V_{d2} - V_2$, then diode 2 conducts so $V_{out} \geq -V_{d2} - V_2$.
- ◆ If we assume $V_{d1} = V_{d2} \approx 0.7\text{ V}$ and $V_1 = 0.5$, $V_2 = 0.25\text{ V}$,
 - for $V_{in} > 1.2\text{ V}$, $d1$ conducts
 - for $V_{in} < -0.95\text{ V}$, $d2$ conducts

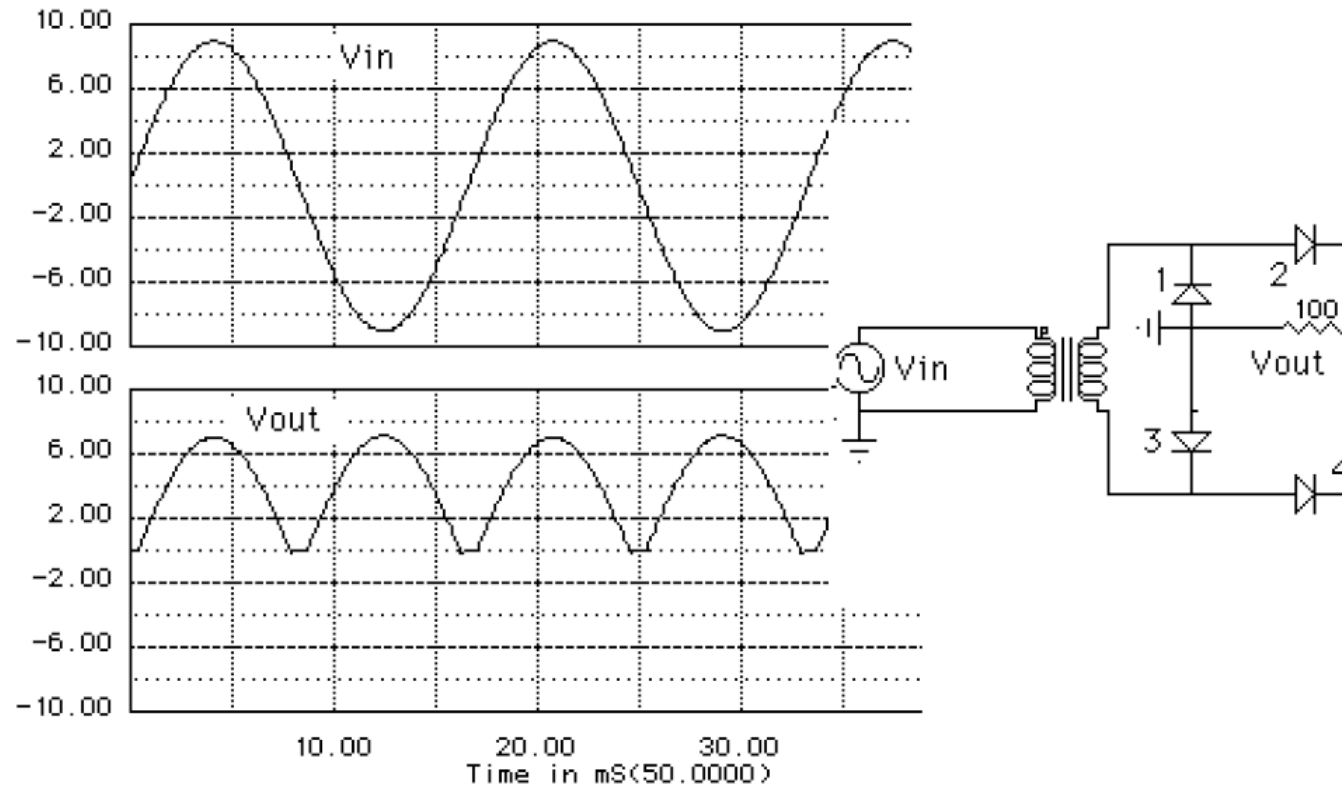- Turning AC into DC (rectifier circuits)
 - ◆ Consider the following circuit with 4 diodes: full wave rectifier.




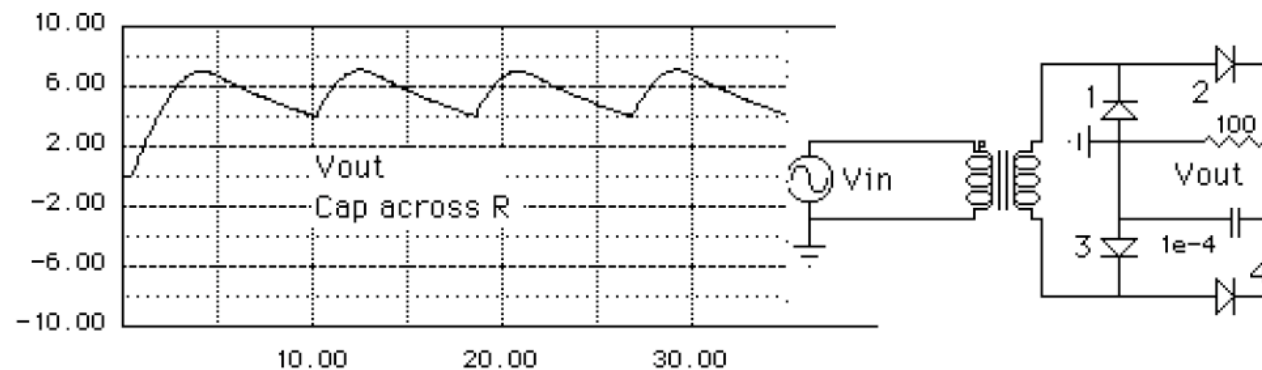- ◆ In the positive part of V_{in} , diodes 2 and 3 conduct.
- ◆ In negative part of the cycle, diodes 1 and 4 conduct.
- ◆ This circuit has lots of ripple.
 - We can reduce ripple by putting a capacitor across the load resistor.
 - Pick RC time constant such that: $RC > 1/(60 \text{ Hz}) = 16.6 \text{ msec}$.
 - example: $R = 100 \, \Omega$ and $C = 100 \, \mu\text{F}$ to reduce ripple



Transistors:



- Transistors are the heart of modern electronics (replaced vacuum tubes)
 - ◆ voltage and current amplifier circuits
 - ◆ low power and small size, can pack thousands of transistors in mm^2 (computers)
- In this class we will only consider *bipolar* transistors.
 - ◆ Bipolar transistors have 3 leads: emitter, base, collector
 - ◆ Bipolar transistors are two diodes back to back and come in two forms:

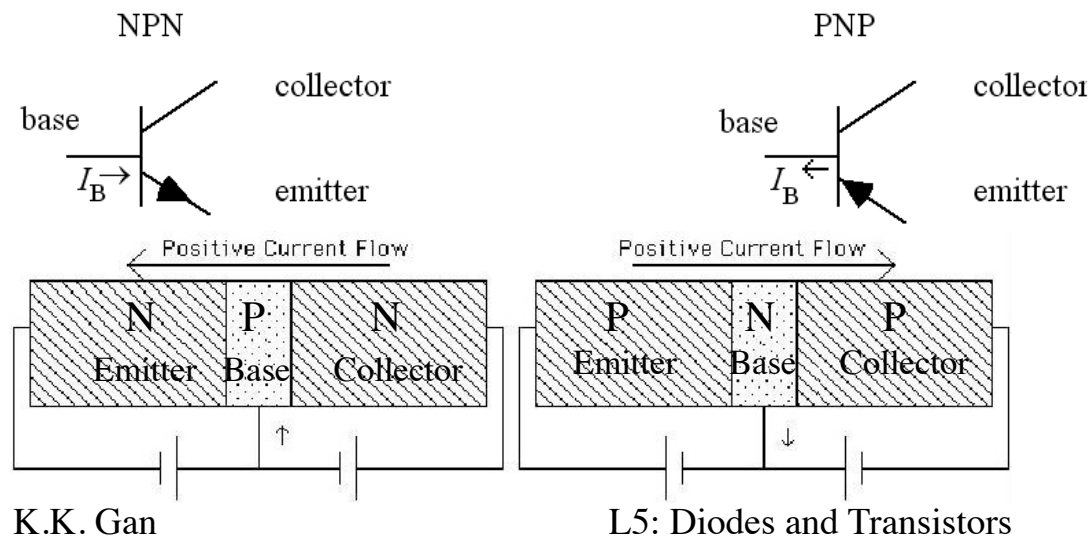

Arrow is always on the emitter and is in the direction of positive current flow

- N material has excess negative charge (electrons).
- P material has excess positive charge (holes).

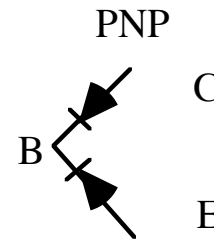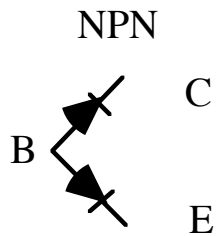- Some **simple** rules for getting transistors to work
 - For NPN (PNP) collector must be more positive (negative) in voltage than emitter.
 - Base-emitter and base-collector are like diodes:




For silicon transistors, $V_{BE} \approx 0.6-0.7 \text{ V}$ when transistor is **on**.


- The currents in the base (I_B), collector (I_C) and emitter (I_E) are related as follows:
 - always: $I_B + I_C = I_E$
 - rough rule: $I_C \approx I_E$, and the base current is very small ($\approx 0.01 I_C$)
 - Better approximation uses 2 related constants, α and β .
 - $I_C = \beta I_B$
 - β is called the current gain, typically 20-200
 - $I_C = \alpha I_E$
 - α typically 0.99
 - Still better approximation:
 - uses 4 (hybrid) parameters to describe transistor performance ($\beta = h_{fe}$)
 - when all else fails, resort to the data sheets!
- Common sense: must not exceed the power rating, current rating etc. or else the transistor dies.

- Transistor Amplifiers
 - ◆ Transistor has 3 legs, one of them is usually grounded.
 - ◆ Classify amplifiers by what is common (*grounded*).


Common Emitter

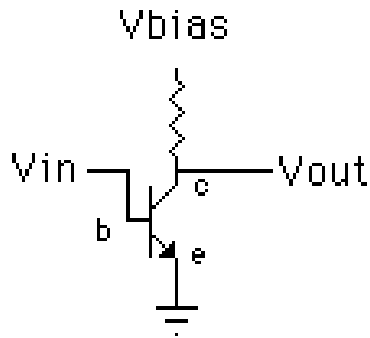

Common Base

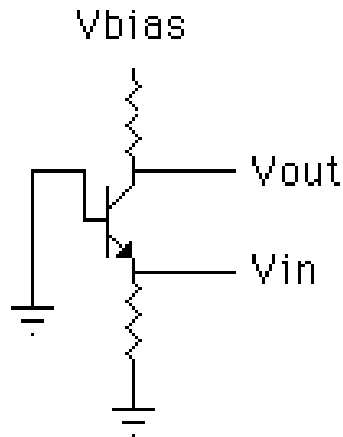


Common Collector
(emitter follower)

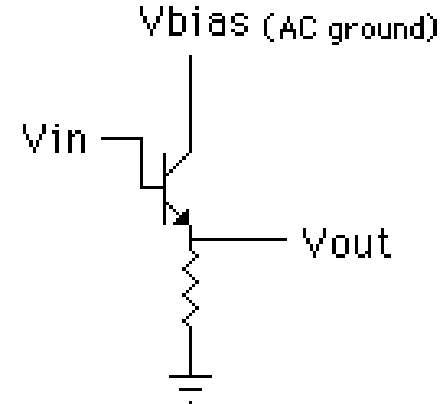

Properties of Amplifiers

| | C E | C B | C C |
|-----------------------------|-------------------------------|-----------------------------|-------------------------------|
| Power gain | Y | Y | Y |
| Voltage gain | Y | Y | N |
| Current gain | Y | N | Y |
| Input impedance | $\approx 3.5 \text{ k}\Omega$ | $\approx 30 \text{ }\Omega$ | $\approx 500 \text{ k}\Omega$ |
| Output impedance | $\approx 200 \text{ k}\Omega$ | $\approx 3 \text{ M}\Omega$ | $\approx 35 \text{ }\Omega$ |
| Output voltage phase change | 180° | none | none |

- Biasing Transistors
 - ◆ For an amplifier to work properly it must be biased **on** all the time, not just when a signal is present.
 - ◆ “**On**” means current is flowing through the transistor (therefore $V_{BE} \approx 0.6\text{-}0.7\text{ V}$).
 - ◆ We usually use a DC circuit (R_1 and R_2 in the circuit below) to achieve the biasing.
- Calculating the operating (DC or quiescent) point of a Common Emitter Amplifier:

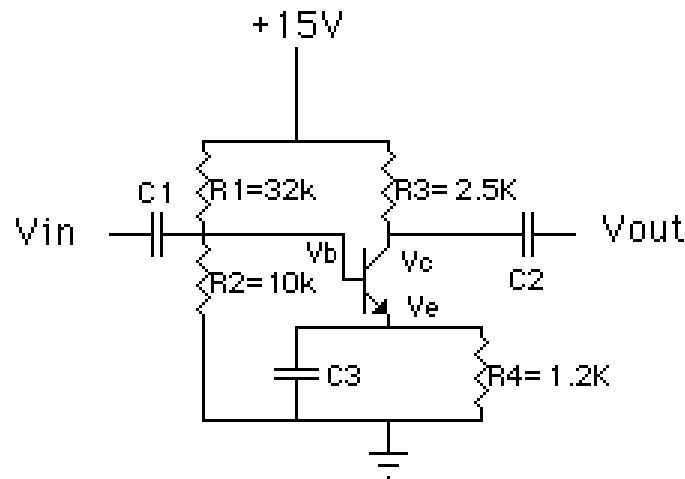

Common Emitter Amp

- ◆ We want to determine the operating (quiescent) point of the circuit.
- ◆ This is a fancy way of saying what's V_B , V_E , V_C , V_{CE} , I_C , I_B , I_E when the transistor is **on**, but $V_{in} = 0$.
- ◆ The capacitors C_1 and C_2 are decoupling capacitors, they block DC voltages.
- ◆ C_3 is a bypass capacitor that provides the AC ground (common).

- **Crude Method** for determining operating point when no spec sheets are available.

a. Remember $I_B = I_C / \beta$ and $\beta \approx 100$ (typical value).

☞ we can neglect the current into the base since it's much smaller than I_C or I_E .

b. If transistor is "working" then $V_{BE} \approx 0.6\text{-}0.7\text{ V}$ (silicon transistor).

c. Determine V_B using R_1 and R_2 as a voltage divider

$$V_B = 15\text{ V} \frac{R_2}{R_1 + R_2} = 3.6\text{ V}$$

d. Find V_E using $V_B - V_E = 0.6\text{ V} \Rightarrow V_E = 3\text{ V}$.


e. $I_E = V_E / R_4 = 3\text{ V} / 12\text{ k}\Omega = 2.5\text{ mA}$.

f. Use the approximation $I_C = I_E \Rightarrow I_C = 2.5\text{ mA}$.

g. $V_C = 15\text{ V} - I_C R_3 = 15 - 2.5\text{ mA} \times 2.5\text{ k}\Omega = 8.75\text{ V}$.

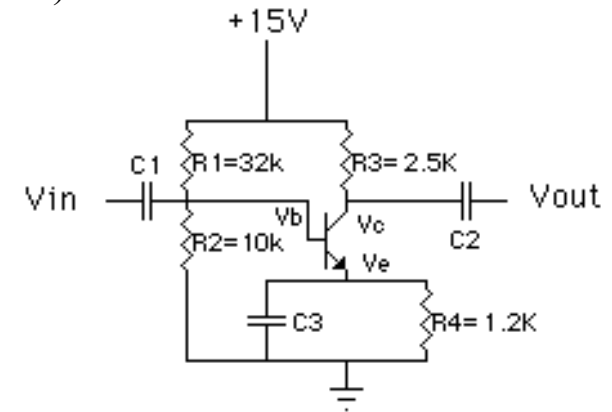h. $V_{CE} = 8.75 - 3 = 5.75\text{ V}$.

☞ The voltages at every point in the circuit are now determined!!!



Common Emitter Amp

- **Spec Sheet or Load line method**

- ☞ Much more accurate than previous method.

- ◆ Load line is set of all possible values of I_C vs. V_{CE} for the circuit in hand.

- ◆ Assume same circuit as previous page and we know R_3 and R_4 .

- ◆ If we neglect the base current, then

$$15 = I_C(R_3 + R_4) + V_{CE}$$


$$I_C = 15 / (R_3 + R_4) - V_{CE} / (R_3 + R_4)$$

- ◆ The above is a straight line in (I_C, V_{CE}) space.

- ☞ This line is the **load line**.


- ◆ Assume $R_3 + R_4 = 3.75 \text{ k}\Omega$, then we can plot the load line from the two limits:
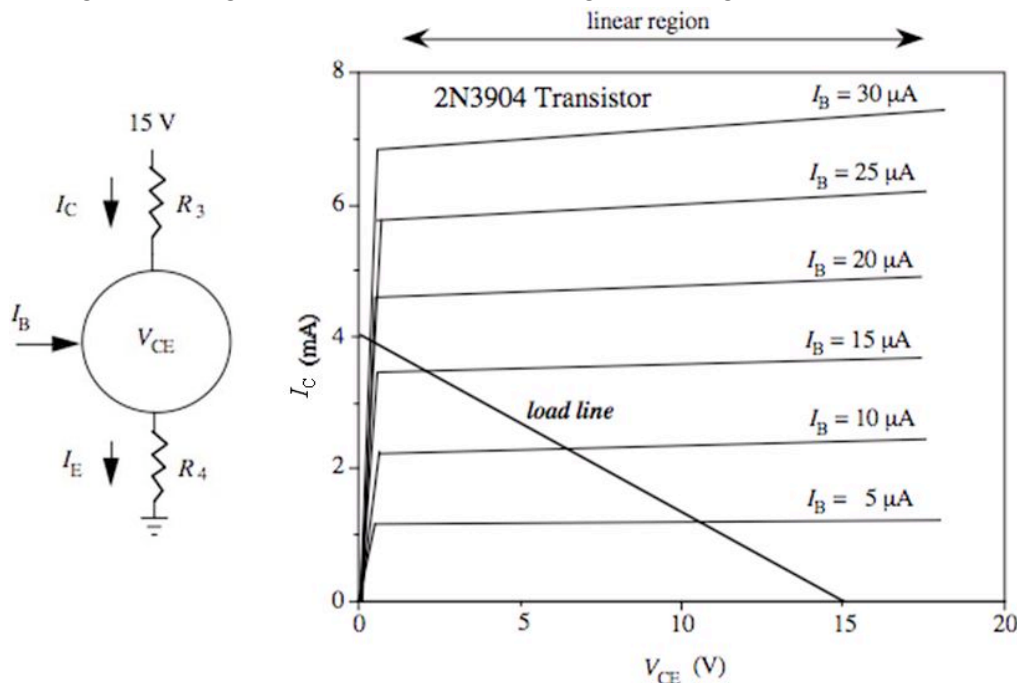
$$I_C = 0, V_{CE} = 15 \text{ V} \quad \text{and} \quad V_{CE} = 0, I_C = 15 \text{ V} / 3.75 \text{ k}\Omega = 4 \text{ mA}$$



Spec. Sheet of 2N3904 transistor:
 I_C vs. V_{CE} for various I_B

- ◆ We want the operating point to be in the linear region of the transistor
 - ☞ we want the output to be a linear representation of the input.
- ◆ Pick the operating point such that for reasonable changes in V_{CE} , I_C
 - ☞ the circuit stays out of the non-linear region and has $I_C > 0$.
 - I_C must be > 0 or transistor won't conduct current in the "correct" direction!
 - If circuit is in nonlinear region then V_{out} is a distorted version of V_{in} .
 - If circuit is in region where $I_C = 0$ then V_{out} is "clipped".
- ◆ If we pick $I_C = 2.5$ mA as operating point
 - $V_{CE} > 0.5$ is the linear region.
 - Usually pick I_C to be in the middle of the linear region.
 - ☞ amp will respond the same way to symmetric (around operating point) output voltage swings.
- ◆ If $I_C = 2.5$ mA and $I_B = 10$ - 11 μ A
 - ☞ $V_{CE} = 5$ - 6 V
- ◆ Can now choose the values for resistors (R_1 , R_2) to give the above voltages and currents.

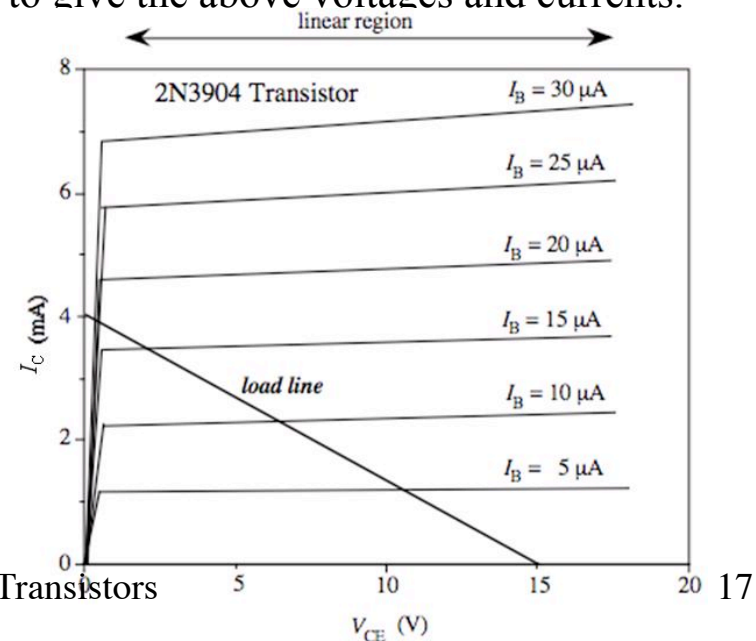

- **Current Gain Calculation from Spec Sheet**

- ◆ We define current gain as:

$$G = \Delta I_{\text{out}} / \Delta I_{\text{in}}$$

- This quantity is often called β .

- In our example I_B is the input and I_C is the output.

- ◆ If we are in the linear region ($V_{CE} > 0.5 \text{ V}$) and the base current changes from 5 to 10 μA

- ☞ the collector current (I_C) changes from ~ 1.1 to 2.2 mA.

- ☞ $G = (2.2 - 1.1 \text{ mA}) / (10 - 5 \mu\text{A}) \approx 200$

- ◆ Like almost all transistor parameters, the exact current gain depends on many parameters:

- frequency of input voltage

- V_{CE}

- I_C

- I_B

