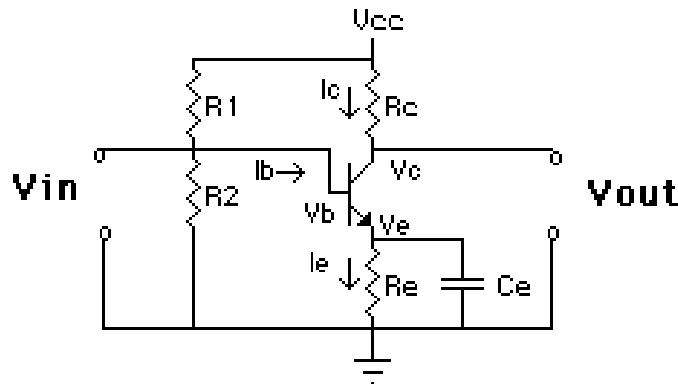


Lecture 6: Transistors Amplifiers

Common Emitter Amplifier (“Simplified”):

- What's common (ground) in a common emitter amp?
 - ◆ The emitter!
 - The emitter is connected (tied) to **ground** usually by a capacitor
 - To an AC signal this **looks** like the emitter is connected to ground.



- What use is a Common Emitter Amp?
 - ◆ Amplifies the input voltage (the voltage at the base of the transistor).
 - ◆ The output voltage has the **opposite** polarity as the input voltage.
 - ◆ We want to calculate the following for the common emitter amp:
 - Voltage Gain $\equiv V_{out}/V_{in}$
 - Input Impedance
 - Output Impedance

- DC Voltage Gain:

- ◆ The voltage gain we are about to derive is for **small signals** only.
 - A small signal is defined here to be in the range of a few mV.
- ◆ As in all of what follows we assume that the transistor is biased on at its DC operating point.

$$V_{out} = V_{cc} - I_C R_C$$

- ◆ Since V_{cc} is fixed (its a DC power supply) we have for a change in output voltage V_{out}

$$\Delta V_{out} = -\Delta I_C R_C$$

- Δ stands for a small change in either the voltage or current.

- ◆ The input voltage is related the emitter voltage by a diode drop:

$$V_{in} = V_B$$

$$= V_E + 0.6 \text{ V}$$

$$\Delta V_{in} = \Delta V_E$$

- ◆ We want to relate the emitter voltage to the emitter current (I_E):

$$V_E = I_E R_E$$

$$\Delta V_E = \Delta I_E R_E$$


- ◆ We can relate the emitter and collector currents by remembering that for a transistor:

$$I_E \approx I_C$$

$$\Delta I_E \approx \Delta I_C$$

$$\Delta V_E = \Delta I_E R_E = \Delta I_C R_E$$
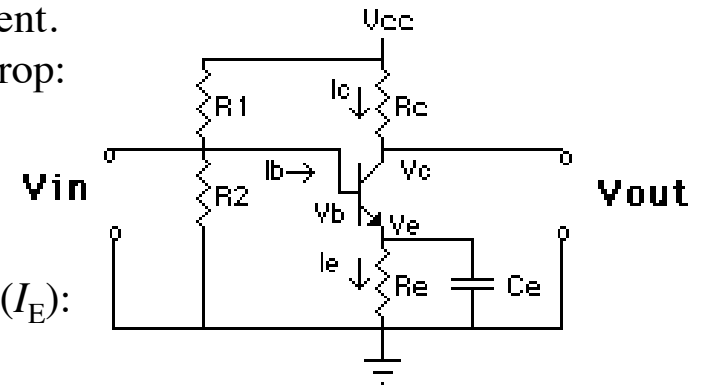
$$\Delta V_{in} = \Delta V_E = \Delta I_C R_E = (-\Delta V_{out} / R_C) R_E$$



- ☞ DC voltage gain (G) for a common emitter amp:

$$\text{Gain} = \frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = -\frac{R_C}{R_E}$$

The minus sign in the gain means that the output is the opposite polarity as the input (180° out of phase).

- What happens if $R_E = 0$???
- Do we have infinite gain?
- **No**, we get a new model for the transistor.
- The base-emitter junction is a diode.

- ☞ Describe the behavior of the junction using the Ebers-Moll equation:

$$I = I_s [e^{qV/kT} - 1]$$

- $V = V_{\text{BE}}$

- $kT/q = 25 \text{ mV at } 20^\circ\text{C}$

- Neglecting the -1 term:

$$V_{\text{BE}} = \frac{kT}{q} [\ln I - \ln I_s]$$

- Calculate the dynamic resistance of the base-emitter junction,

$$r_{\text{BE}} = \frac{dV_{\text{BE}}}{dI}$$

$$= \frac{kT}{qI}$$

$$= 25 \times 10^{-3} / I$$

$r_{\text{BE}} = 25 \, \Omega$ for current of 1 mA

$$\text{Gain} = -\frac{R_C}{r_{\text{BE}} + R_E \parallel X_{\text{CE}}}$$

- We can now write the gain for the case $R_E = 0$ (neglecting X_{CE} too):

$$\text{Gain} = -R_C / r_{BE} = -R_C (I_C / 25) \text{ with } I_C \text{ measured in mA.}$$

Simpson (page 227) writes an equivalent formula for the gain using the transistor parameter β and a slightly different temperature, $T = 300^\circ\text{K}$.

- In terms of the hybrid parameter model (we will see this model soon)

$$r_{BE} = h_{ie} / h_{fe}$$
- Using r_{BE} to design a circuit is a dangerous practice as it depends on temperature
 - varies from transistor to transistor even for same type of transistor.

- Input impedance


- ◆ Input impedance of the common emitter amp can be calculated from the equivalent circuit:

$$\frac{1}{R_{in}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{tin}}$$

$$\begin{aligned} R_{tin} &\approx \frac{\Delta V_B}{\Delta I_B} \\ &= \frac{\Delta V_E}{\Delta I_E / \beta} \\ &= \frac{\Delta I_E R_E}{\Delta I_E / \beta} \\ &= \beta R_E \end{aligned}$$

- ◆ For AC case, we usually have R_1 and $R_2 > R_{tin}$

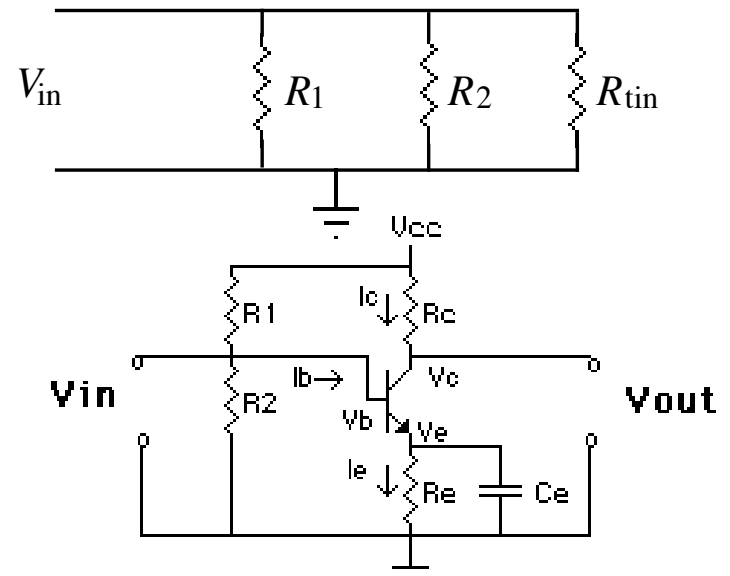👉 $R_{tin} = \beta R_E = \beta r_{BE} = 2500 \Omega$ for 1 mA of collector current and $\beta = 100$.



- Output impedance
 - ◆ Harder to calculate than the input impedance and only a hand waving argument will be given.
 - ◆ The output impedance of the amp is the parallel impedance of R_C and the output impedance of the transistor looking into the collector junction.
 - ◆ The collector junction is reversed biased and hence looks like a huge resistor compared to R_C .
 - ☞ The output impedance is simply R_C
 - assume that the load impedance (the thing the amp is hooked up to) is less than R_C .

Common Collector Amplifier:



- Sometimes this amp is called an *emitter follower*.
- What's common (ground) in a common collector amp?
 - ◆ The collector!
 - ◆ The collector is connected (tied) to a DC power supply.
 - ◆ To an AC signal this *looks* like the collector is connected to ground.
- We want to calculate: voltage and current gain, and input and output impedance.
- Voltage Gain:
 - ◆ The input is the base and the output is taken at the emitter

$$V_E = V_B - 0.6 \text{ V}$$

$$\Delta V_E = \Delta V_B$$

$$\Delta V_{out} = \Delta V_{in}$$

- ☞ The amp has **unity** gain!

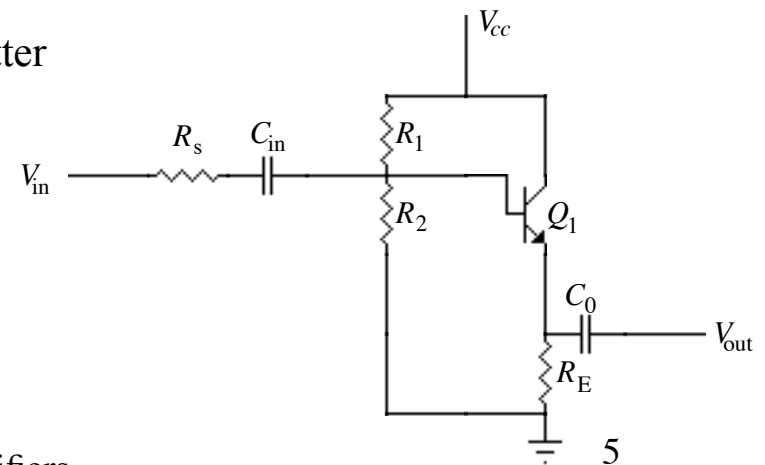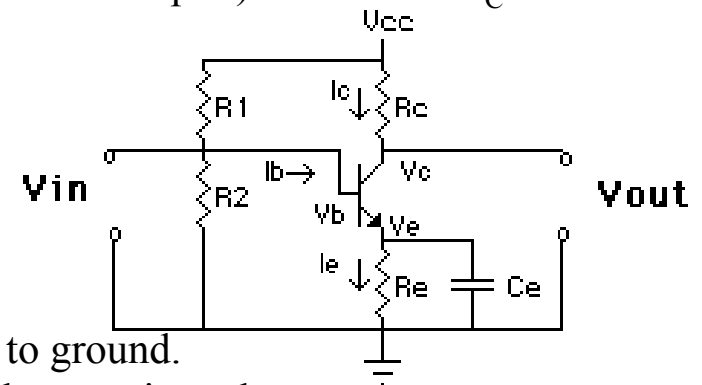

- Current Gain: As always we can use Kirchhoff's current rule.

$$I_E = I_B + I_C$$

$$= I_B(\beta + 1)$$

$$\frac{\Delta I_E}{\Delta I_B} = \beta + 1$$

$$\frac{\Delta I_{out}}{\Delta I_{in}} = \beta + 1$$

- ◆ Since a typical value for β is 100, there is lots of current gain.

- Input impedance:

- ◆ By definition the input impedance is

$$R_{in} = \frac{\Delta V_{in}}{\Delta I_{in}}$$


$$= \frac{\Delta V_B}{\Delta I_B}$$

$$= \frac{\Delta V_E}{\Delta I_E / (\beta + 1)}$$

$$= \frac{\Delta I_E R_E}{\Delta I_E / (\beta + 1)}$$



$$R_{in} = (\beta + 1)R_E$$

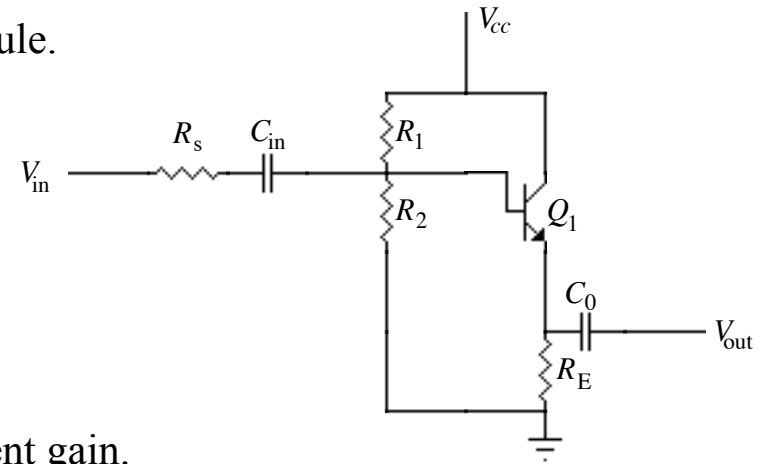- Since R_E is usually a few $k\Omega$ and β is typically 100
 the input impedance of the common collector amp is large.



- Output impedance: This is trickier to calculate than the input impedance.

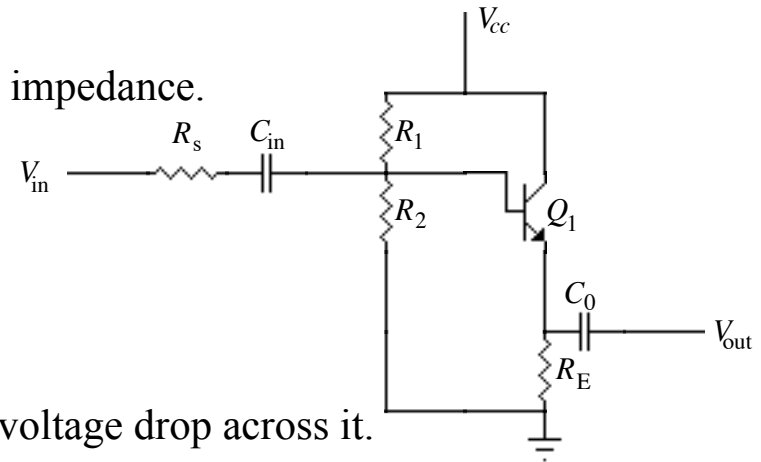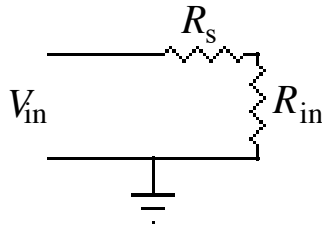- ◆ In the figure below we are looking **into** the amp:



- ◆ R_{in} is the input impedance of the transistor and V_{tin} is the voltage drop across it.

$$V_{tin} = \frac{V_{in} R_{in}}{R_{in} + R_s}$$


$$\approx \frac{V_{in} \beta R_E}{\beta R_E + R_s}$$

- ◆ If we look from the other (output) side of the amp with R_{out} the output impedance of the transistor
 - The voltage drop at A is the same as the voltage at the base (V_B) since the amp has unity gain.
 - 👉 We can rewrite the equation into a voltage divider equation to find R_{out} .

$$V_A = \frac{V_{in} R_E}{R_E + R_{out}}$$


$$= V_{tin} = \frac{V_{in} \beta R_E}{\beta R_E + R_s} = \frac{V_{in} R_E}{R_E + R_s / \beta}$$

$$R_{out} = \frac{R_s}{\beta}$$

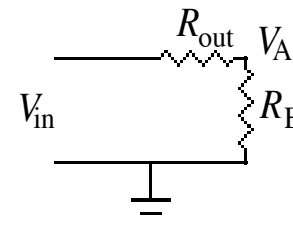

- 👉 R_{out} is small since β is typically 100.

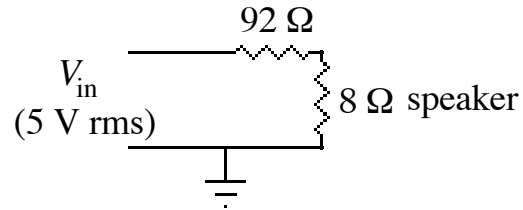- What good is the common collector amp?
 - ◆ Example: In stereo systems very often loud speakers have $8\ \Omega$ input impedance. Assume that you want to drive the speakers with a 5 Volt voltage source with $92\ \Omega$ of series resistance. Lets look at 2 ways of driving the speakers and the power each method delivers to the speaker.
 - a. Hook the speakers directly to the voltage source:




- The voltage delivered to the speaker is $(8/100)V_{in}$.
- The power delivered is:

$$P = V^2/R = (5 \times 8 / 100)^2 / 8 = 0.02 \text{ Watts}$$

👉 not much power!

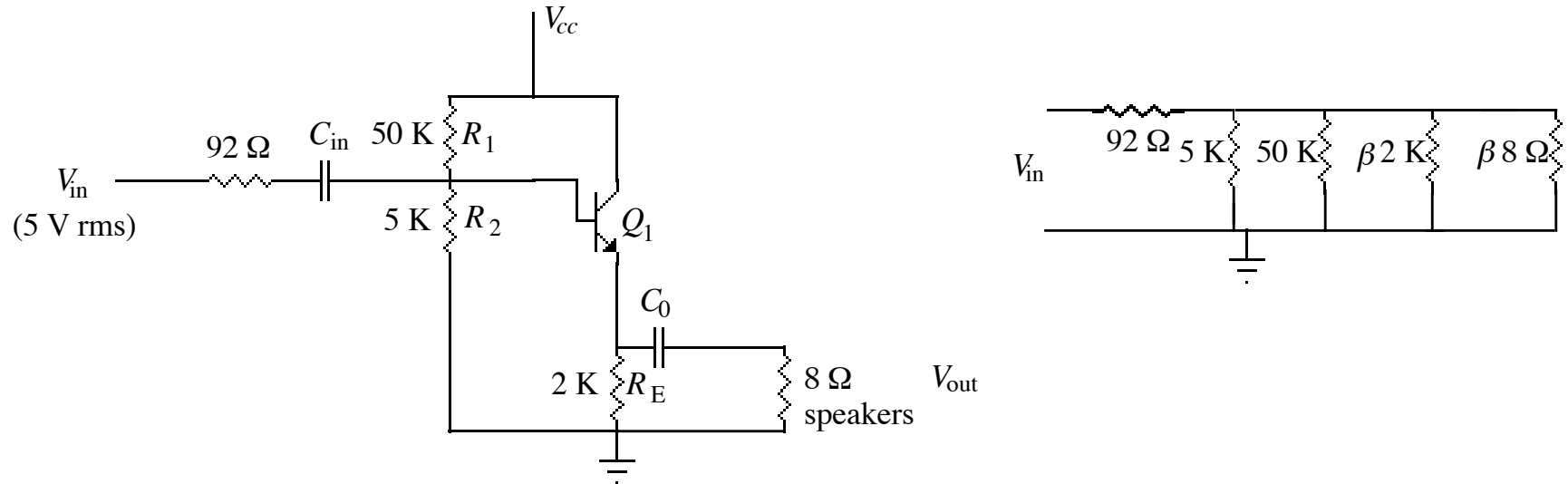b. Use a common collector (emitter follower):



- An AC signal at the input sees
 $\beta R_{sp} = \beta 8\ \Omega = 800\ \Omega$
- From the speakers point of view the amp impedance looks like
 $92\ \Omega / \beta \sim 1\ \Omega$
- The power delivered to the speaker can now be calculated:
 $V_{sp} = (\beta 8\ \Omega V_{in}) / (\beta 8\ \Omega + 92\ \Omega) = 0.9 V_{in}$
 $P_{sp} = V_{sp}^2 / R_{sp} = (0.9 \times 5)^2 / 8 = 2.5\text{ Watts (rms)}$
 over a **hundred** times more power delivered to the speaker.

Emitter Followers (common collectors) are used to match high impedances to low impedances