

Lecture 9: Digital Electronics

Introduction:

- We can classify the building blocks of a circuit or system as being either analog or digital in nature.
 - ◆ If we focus on voltage as the circuit parameter of interest:
 - Analog: The voltage can take on a range of voltages, e.g. any value between 0.1 and 2 Volts.
 - Digital: The voltage can have only two values, e.g. 0 or 5 Volts
 - We say the voltage is either on or off
 - ☞ Digital circuits are useful when we don't need a continuous range of voltage or current.
 - Examples: Representing numbers, binary logic, counting circuits.
 - Example: Represent base 10 numbers using the binary system:
$$2|_{10} = 10|_2 = 1 \times 2^1 + 0 \times 2^0$$
$$10|_{10} = 1010|_2 = 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 0 \times 2^0$$
- Digital circuits use standard voltages (or currents) to denote ON (high, 1) or OFF (low, 0).
 - ◆ These standards are called "Logic Families" and there are several families.
 - ◆ Two of the most popular families are:
 - TTL (**T**ransistor-**T**ransistor-**L**ogic): ON = 5 Volts, OFF = 0 Volts
 - ECL (**E**mitter-**C**oupled-**L**ogic): ON = -1 Volt, OFF = -1.6 Volts
 - ☞ For practical reasons both ON and OFF are given by a range of voltages or currents.
 - ◆ ON for an input to a circuit might have slightly different voltage than ON for an output to a circuit.

- A description of several logic families is given in the table below:

	Delay (ns)	Max. FF Rate (MHz)	Power/Gate (mW)	High (V)	Low (V)
Standard TTL (7400)	10	35	15	3.5	0.2
Low-power Schottky (74LS00)	9.0	33	2	3.5	0.2
Fast TTL (74F00)	3.5	125	5.5	2.7	0.5
CMOS (74C00)	25 @ 10 V 50 @ 25 V	10 @ 10 V 3.5 @ 5 V	0.01	5-15	0
High-speed CMOS (74HC00)	8.0	40	0.01	2-6	0.1
ECL	2	250	25	-0.9	-1.8
100k ECL	0.75	500	40	-1.0	-1.7

- ◆ Advantages of Digital:


- only deal with two voltage levels (either ON or OFF)
- voltages (or currents) are standardized
- do not deal with individual transistors...

- ◆ Disadvantages of Digital:

- too many "black" boxes
- need good power supplies, clocks etc. for circuits to work properly


Logic Gates:

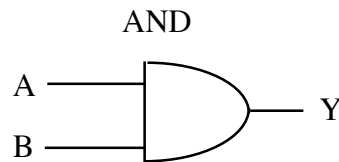- We want to make decisions based on digital information.
 - ◆ For now consider the basic building blocks with one or two inputs and one output.
- The basic logic units (gates) are: AND, OR, NOT.
 - ◆ These functions are defined by their truth tables.



A	B	Y
0	0	0
1	0	0
0	1	0
1	1	1


$$A \bullet B = Y$$

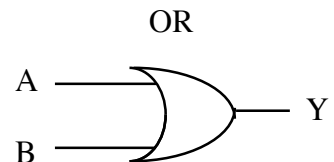

A	B	Y
0	0	0
1	0	1
0	1	1
1	1	1

$$A + B = Y$$


NOT (inverter)

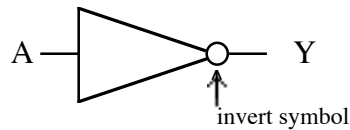


A	Y
0	1
1	0

$$\overline{A} = Y$$

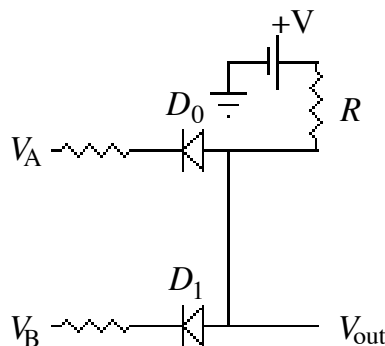
A and B stand for the inputs
Y stands for the output
0: low input or output
1: high input or output



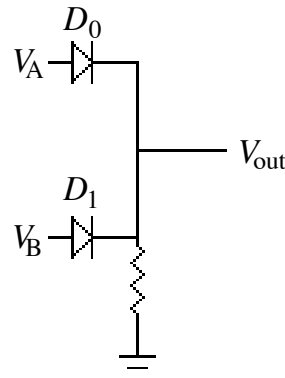$V_{out} = +V$ if both diodes off
 $= 0$ if one or more diodes conduct



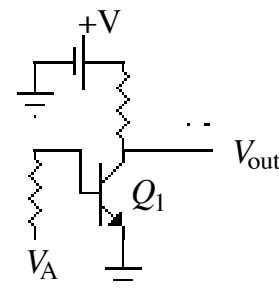$V_{out} = V_A$ or V_B if either diodes conduct
 $= 0$ if both diodes are off



$V_A > 0.6 \text{ V}$, Q_1 is on, $V_{out} \sim 0$
 $V_A < 0.6 \text{ V}$, Q_1 is off, $V_{out} = +V$

Boolean Algebra or the Algebra of 1's and 0's

- Circuits consisting of logic gates are described by Boolean algebra.
 - ◆ Use of this algebra can greatly simplify circuit design, e.g. minimize the number of components.
- The following theorems can be proved using a truth table and the definition of OR, AND, and NOT.

1) $A + A = A$, $A + 1 = 1$, $A + 0 = A$

2) $AA = A$

3) $AB = BA$

4) $ABC = (AB)C = A(BC)$

5) $A(B + C) = AB + AC$

6) $\bar{1} = 0$, $\bar{0} = 1$

7) $A + \bar{A} = 1$, $A\bar{A} = 0$, $A \cdot 1 = A$

8) $\bar{\bar{A}} = A$

9) $\overline{A + B} = \bar{A} \cdot \bar{B}$
10) $\overline{AB} = \bar{A} + \bar{B}$ } DeMorgan's Theorem

- Example using Boolean algebra:


- ◆ **Prove:** $X + YZ = (X + Y)(X + Z)$
 $(X + Y)(X + Z) = XX + XZ + YX + YZ$ by 5)
 $= X + X(Z + Y) + YZ$ by 2) and 5)
 $= X(1 + Z + Y) + YZ$ by 5)
 $= X + YZ$ by 1)

See Simpson page 540 for more theorems.


For clarity “.” (AND) is not shown in some theorems.

- ◆ We could also have proven the above using a truth table.
 - There are 8 (2^3) possible combinations of X, Y, Z.
 - For a large number of inputs using a truth table becomes unwieldy.
 - Example, if there are 10 inputs
 - 👉 $2^{10} = 1024$ possible combinations!

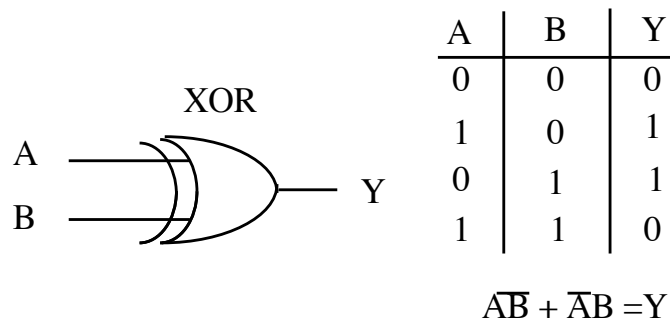- Example: Exclusive OR = XOR = $A \oplus B$.
 - ◆ Output is high if inputs are different.



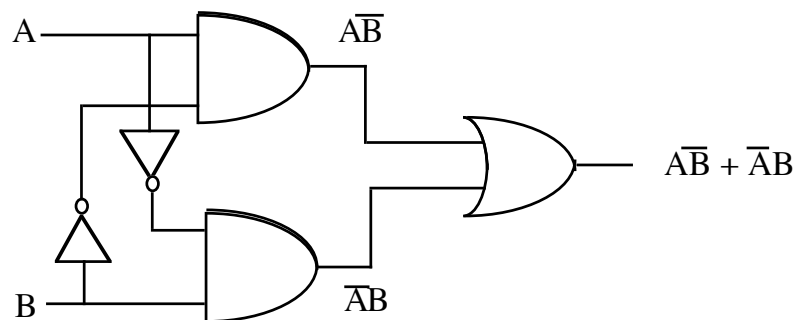- ◆ How do we make an exclusive OR with AND, OR, and NOT gates?



Brute force method

- ◆ Can we simplify this circuit with the use of less parts?

- Use logical theorems:


$$A \oplus B = A\bar{B} + \bar{A}B$$

$$= A\bar{A} + A\bar{B} + \bar{A}B + B\bar{B} \quad 7) \text{ and } 1)$$


$$= A(\bar{A} + B) + B(\bar{A} + \bar{B}) \quad 5)$$

$$= A(\bar{A}B) + B(\bar{A}\bar{B}) \quad 10)$$

$$= (A + B)(\bar{A}\bar{B}) \quad 5)$$

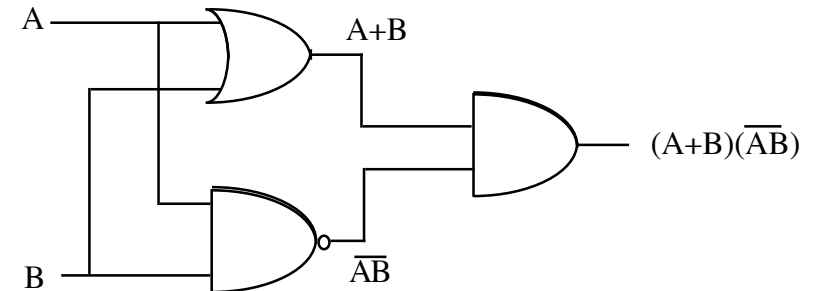


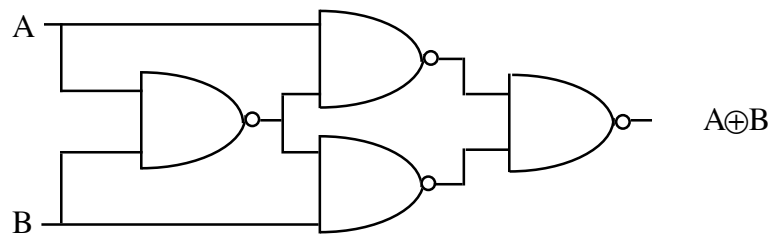- The circuit uses only 3 parts (OR, NAND, AND), but each of them is different!
- Usually there are many ways to synthesize the same function (circuit).
- Must decide if you want to minimize:
 - number of components
 - types of components
 - number of connections
 - power consumption
- For example we can make an XOR using only 4 NAND gates:



- Final example: Suppose you have a light controlled by 3 switches.
 - You want the light to be on if any one of the 3 switches is on or if all 3 switches are on.

A	B	C	Light
1	1	1	1
1	0	0	1
1	1	0	0
0	1	1	0
0	1	0	1
0	0	1	1
1	0	1	0
0	0	0	0

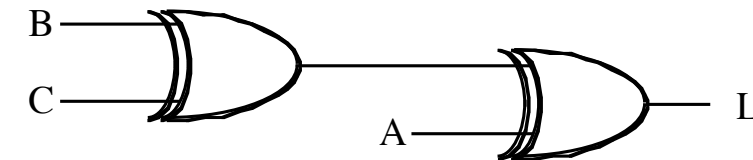


1 = ON
0 = OFF


$$\begin{aligned}
 L &= ABC + A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C \\
 &= A(BC + \bar{B}\bar{C}) + \bar{A}(B\bar{C} + \bar{B}C) \\
 &= A(B + \bar{C})(\bar{B} + C) + \bar{A}(B \oplus C) \\
 &= \overline{A\bar{B}C\bar{B}\bar{C}} + \bar{A}(B \oplus C) \\
 &= \overline{A\bar{B}C} + \overline{B\bar{C}} + \bar{A}(B \oplus C) \\
 &= \overline{A\bar{B} \oplus C} + \bar{A}(B \oplus C) \\
 &= A \oplus (B \oplus C)
 \end{aligned}$$

Flip-Flops:

- Basic counting unit in computer:
 - ◆ counters
 - ◆ shift registers
 - ◆ memory
- Circuit whose output depends on the history of its inputs.
- Can make a flip-flop with just 2 transistors (or 2 vacuum tubes 1919!).
- Lots of different types of flip-flops (e.g. RS, JK, T, D).
- Example: RS flip-flop or Reset-Set flip flop
 - ◆ Flip-flops, like logic gates are defined by their truth table.
 - ◆ Flip-flops are controlled by an external clock pulse.
 - ◆ All inputs and outputs are logic levels (e.g. TTL, ECL).
 - ◆ Can make an RSFF out of NOR gates:

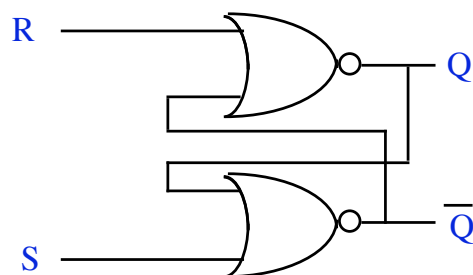


R	S	Q_{n+1}
0	0	Q_n
1	0	0
0	1	1
1	1	undefined

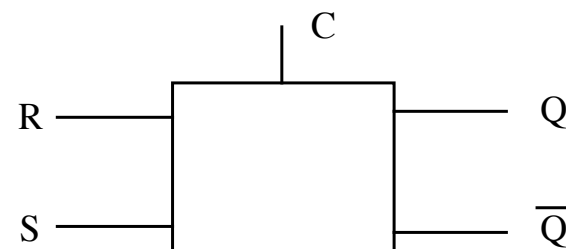


- Q_n is the present state of the FF.
- Q_{n+1} will be the output after the clock enables the FF to look at its inputs (R and S).
- Many FF change state ($Q_n \rightarrow Q_{n+1}$) on the trailing edge of the clock.

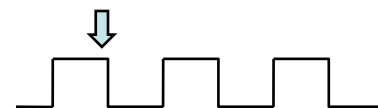The state with $R = S = 1$ is undefined. The output is not predictable!




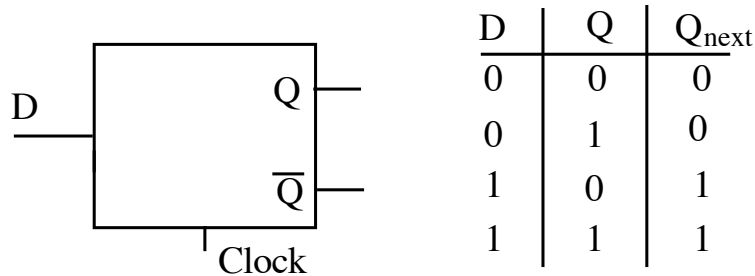- Example: D flip-flop (Like RS but only one input)



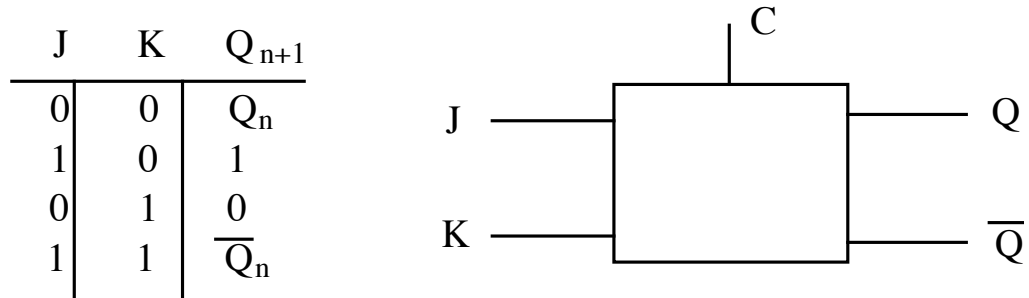- Example: JK flip-flop


- ◆ JKFF is like the RSFF except that both inputs (J and K) can be high (1).



- ◆ Most JKFF's have a connection for forcing $Q = 0$ (clear) or forcing $Q = 1$ (preset).

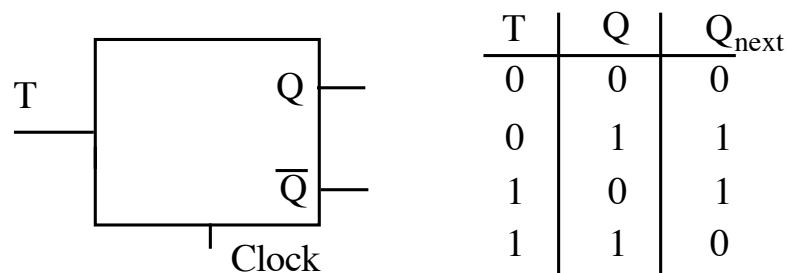- Example: T (Toggle) flip-flop

- ◆ T flip-flop is like the JKFF with both inputs (J and K) tied to each other.



- Flip-Flops are a class of circuits called “multivibrators”
 - ◆ Multivibrators are circuits with one or more stable states.
 - Monostable multivibrators (one shot) have one stable state.
 - If the circuit is forced out of its stable state (e.g. by an input pulse)
 - ☞ it eventually returns back to the stable state by itself.
 - Bistable multivibrators have two stable states.
 - Transitions between states occur only by an external action (e.g. voltage pulse for flip-flops).
 - Transition voltages can be different for the two states (e.g. Schmitt trigger).
 - Astable multivibrators are two state devices which switch on their own accord.
 - ☞ Commonly used as oscillators.

◆ Example: Bistable Multivibrator.

- This circuit has two stable states.
- When either transistor conducts there is 4 mA flowing (by design) in the collector (I_{C1} or I_{C2}).
- State 1: transistor 1 off, transistor 2 on
 - $V_{C1} \approx 11 \text{ V}$, $V_{B1} \approx 2 \text{ V}$, $V_{E1} \approx 4 \text{ V}$
 - $V_{C2} \approx 4 \text{ V}$, $V_{B2} \approx 5.5 \text{ V}$, $V_{E2} \approx 4 \text{ V}$ T₂ is saturated ($V_{CE} \approx 0$)
- Transition from state 1 to state 2:
 - Input pulse forces T₁ to conduct, T₁ conducting means that V_{C1} drops.
 - V_{C1} causes V_{B2} to drop to the point where T₂ is not conducting.
- State 2: transistor 1 on, transistor 2 off
 - $V_{C1} \approx 4 \text{ V}$, $V_{B1} \approx 5.5 \text{ V}$, $V_{E1} \approx 4 \text{ V}$ T₁ is saturated ($V_{CE} \approx 0$)
 - $V_{C2} \approx 11 \text{ V}$, $V_{B2} \approx 2 \text{ V}$, $V_{E2} \approx 4 \text{ V}$

