# **Lecture 9: Digital Electronics**

### Introduction:

- We can classify the building blocks of a circuit or system as being either analog or digital in nature.
  - If we focus on voltage as the circuit parameter of interest:
    - Analog: The voltage can take on a range of voltages, e.g. any value between 0.1 and 2 Volts.
    - Digital: The voltage can have only two values, e.g. 0 or 5 Volts
      - We say the voltage is either on or off
      - Digital circuits are useful when we don't need a continuous range of voltage or current.
      - Examples: Representing numbers, binary logic, counting circuits.
      - Example: Represent base 10 numbers using the binary system:

 $\begin{array}{l} 2|_{10} = 10|_2 = 1 \ \text{x} \ 2^1 + 0 \ \text{x} \ 2^0 \\ 10|_{10} = 1010|_2 = 1 \ \text{x} \ 2^3 + 0 \ \text{x} \ 2^2 + 1 \ \text{x} \ 2^1 + 0 \ \text{x} \ 2^0 \end{array}$ 

- Digital circuits use standard voltages (or currents) to denote <u>ON</u> (high, 1) or <u>OFF</u> (low, 0).
  - These standards are called "Logic Families" and there are several families.
  - Two of the most popular families are:
    - TTL (Transistor-Transistor-Logic): ON = 5 Volts, OFF = 0 Volts
    - **ECL** (Emitter-Coupled-Logic): ON = -1 Volt, OFF = -1.6 Volts
  - For practical reasons both ON and OFF are given by a range of voltages or currents.
  - ON for an input to a circuit might have slightly different voltage than ON for an output to a circuit.

• A description of several logic families is given in the table below:

	Delay (ns)	Max. FF Rate (MHz)	Power/Gate (mW)	High (V)	Low (V)
Standard TTL (7400)	10	35	15	3.5	0.2
Low-power Schottky (74LS00)	9.0	33	2	3.5	0.2
Fast TTL (74F00)	3.5	125	5.5	2.7	0.5
CMOS 22 (74C00) 55	25 @ 10 V 50 @ 25 V	10 @ 10 V 3.5 @ 5 V	0.01	5-15	0
High-speed CMOS (74HC00)	8.0	40	0.01	2-6	0.1
ECL	2	250	25	-0.9	-1.8
100k ECL	0.75	500	40	-1.0	-1.7

• Advantages of Digital:

- only deal with two voltage levels (either ON or OFF)
- voltages (or currents) are standardized
- do not deal with individual transistors...
- Disadvantages of Digital:
  - too many "black" boxes
  - need good power supplies, clocks etc. for circuits to work properly

K.K. Gan

#### L9: Digital Electronics

#### **Logic Gates:**

- We want to make decisions based on digital information.
  - For now consider the basic building blocks with one or two inputs and one output.
- The basic logic units (gates) are: AND, OR, NOT.
  - These functions are defined by their truth tables.



### Boolean Algebra or the Algebra of 1's and 0's

- Circuits consisting of logic gates are described by Boolean algebra.
  - Use of this algebra can greatly simplify circuit design, e.g. minimize the number of components.
- The following theorems can be proved using a truth table and the definition of OR, AND, and NOT.

1) 
$$A + A = A, A + 1 = 1, A + 0 = A$$
  
2)  $AA = A$   
3)  $AB = BA$   
4)  $ABC = (AB)C = A(BC)$   
5)  $A(B+C) = AB + AC$   
6)  $\overline{1} = 0, \overline{0} = 1$   
7)  $A + \overline{A} = 1, A\overline{A} = 0, A \cdot 1 = A$   
8)  $\overline{\overline{A}} = A$   
9)  $\overline{A + B} = \overline{A} \cdot \overline{B}$   
10)  $\overline{AB} = \overline{A} + \overline{B}$  DeMorgan's Theorem  
Example using Boolean algebra:  
• **Prove:**  $X + YZ = (X + Y)(X + Z)$ 

Prove: 
$$X + YZ = (X + Y)(X + Z)$$
 $(X + Y)(X + Z) = XX + XZ + YX + YZ$ 
 by 5)

  $= X + X(Z + Y) + YZ$ 
 by 2) and 5

  $= X(1 + Z + Y) + YZ$ 
 by 5)

  $= X + YZ$ 
 by 1)

K.K. Gan

L9: Digital Electronics

- We could also have proven the above using a truth table.
  - There are 8  $(2^3)$  possible combinations of X, Y, Z.
  - For a large number of inputs using a truth table becomes unwieldy.
  - Example, if there are 10 inputs
    - $\sim$  2<sup>10</sup> = 1024 possible combinations!
- Example: Exclusive  $OR = XOR = A \oplus B$ .
  - Output is high if inputs are different.





• How do we make an exclusive OR with AND, OR, and NOT gates?



L9: Digital Electronics

- Can we simplify this circuit with the use of less parts?
  - Use logical theorems:



- Usually there are many ways to synthesize the same function (circuit).
- Must decide if you want to minimize:
  - number of components
  - types of components
  - number of connections
  - power consumption
- For example we can make an XOR using only 4 NAND gates:



- Final example: Suppose you have a light controlled by 3 switches.
  - You want the light to be on if any one of the 3 switches is on or if all 3 switches are on.



## **Flip-Flops:**

- Basic counting unit in computer:
  - counters
  - shift registers
  - memory
- Circuit whose output depends on the history of its inputs.
- Can make a flip-flop with just 2 transistors (or 2 vacuum tubes 1919!).
- Lots of different types of flip-flops (e.g. RS, JK, T, D).
- Example: RS flip-flop or <u>R</u>eset-<u>S</u>et flip-flop
  - Flip-flops, like logic gates are defined by their truth table.
  - Flip-flops are controlled by an external clock pulse.
  - All inputs and outputs are logic levels (e.g. TTL, ECL).
  - Can make an RSFF out of NOR gates:



- $Q_n$  is the present state of the FF.
- $Q_{n+1}$  will be the output after the clock enables the FF to look at its inputs (R and S).
- Many FF change state  $(Q_n \rightarrow Q_{n+1})$  on the trailing edge of the clock.

The state with R = S = 1 is undefined. The output is not predictable!

K.K. Gan

#### L9: Digital Electronics

Ŷ

• Example: D flip-flop (Like RS but only one input)



- Example: JK flip-flop
  - JKFF is like the RSFF except that both inputs (J and K) can be high (1).



• Most JKFF's have a connection for forcing Q = 0 (clear) or forcing Q = 1 (preset).

#### • Example: T (*Toggle*) flip-flop

• T flip-flop is like the JKFF with both inputs (J and K) tied to each other.



- Flip-Flops are a class of circuits called "multivibrators"
  - Multivibrators are circuits with one or more stable states.
    - Monostable multivibrators (one shot) have one stable state.
      - If the circuit is forced out of its stable state (e.g. by an input pulse)
        - it eventually returns back to the stable state by itself.
    - Bistable multivibrators have two stable states.
      - **Transitions** between states occur only by an external action (e.g. voltage pulse for flip-flops).
      - Transition voltages can be different for the two states (e.g. Schmitt trigger).
    - Astable multivibrators are two-state devices which switch on their own accord.
      - Commonly used as oscillators.

- Example: Bistable Multivibrator.
  - This circuit has two stable states.
  - When either transistor conducts there is 4 mA flowing (by design) in the collector ( $I_{C1}$  or  $I_{C2}$ ).
  - State 1: transistor 1 off, transistor 2 on

• 
$$V_{C2} \approx 4 \text{ V}, V_{B2} \approx 5.5 \text{ V}, V_{E2} \approx 4 \text{ V}$$
 T<sub>2</sub> is saturated ( $V_{CE} \approx 0$ )

- Transition from state 1 to state 2:
  - Input pulse forces  $T_1$  to conduct,  $T_1$  conducting means that  $V_{C1}$  drops.
  - $V_{C1}$  causes  $V_{B2}$  to drop to the point where  $T_2$  is not conducting.
- State 2: transistor 1 on, transistor 2 off

• 
$$V_{C1} \approx 4 \text{ V}, V_{B1} \approx 5.5 \text{ V}, V_{E1} \approx 4 \text{ V}$$
  $T_1 \text{ is saturated } (V_{CE} \approx 0)$ 

$$\Box V_{C2} \approx 11 \text{ V}, V_{B2} \approx 2 \text{ V}, V_{E2} \approx 4 \text{ V}$$

