

## Physics 4700 Homework VII

Due November 25

1. Simpson: Problem 3, page 595

- Convert  $(49)_{10}$  to  $( )_2$
- Convert  $(49)_{10}$  to  $( )_8$
- Convert  $(49)_{10}$  to  $( )_{16}$

2. Convert the following binary numbers to decimal:

- 1110101.0110
- 11.01010101...repeats

3. Simpson: Problem 10, page 595

Diagram how would you implement the following functions using,

- only NAND gates
- only NOR gates


$$F = A \cdot \bar{B} + \bar{A} \cdot B$$

$$F = A \cdot B$$

$$F = A + B$$

$$F = \bar{A}$$


4. Simpson: Problem 12, Page 596

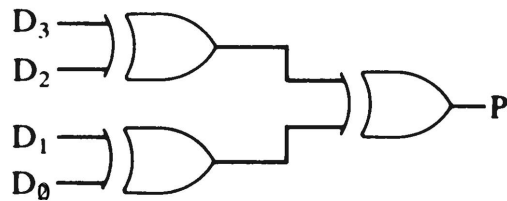

Write the truth table for P in terms of  $D_3$ ,  $D_2$ ,  $D_1$ ,  $D_0$ . What is P called?

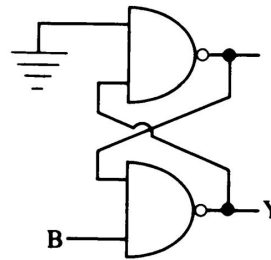
5. Simpson: Problem 4, page 665

What is the relationship between B and Y?



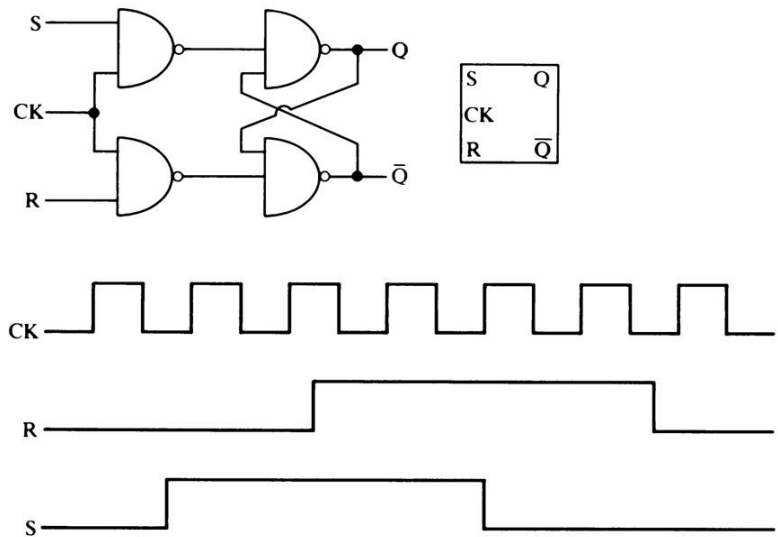
6. Simpson: Problem 8, page 666

For the clocked RS flip-flop shown, with  $Q = 0$ ,  $\bar{Q} = 1$  initially, sketch  $Q$ . If  $R$  is held at 0, sketch  $Q$  for the CK and S inputs shown.




7. The following circuit can be used to convert an input analog voltage to a digital output voltage.  $C_A$ ,  $C_B$ , and  $C_C$  are comparators which give a logic level 1 if the positive input (+) is greater than the negative input. The outputs, LSB and MSB stand for least significant bit and most significant bit respectively. Complete the following truth table. You will have a chance to build something similar to this in lab.

$V_{input} (V)$	$C_A$	$C_B$	$C_C$	LSB	MSB
0.5					
1.5					
2.3					
4.0					

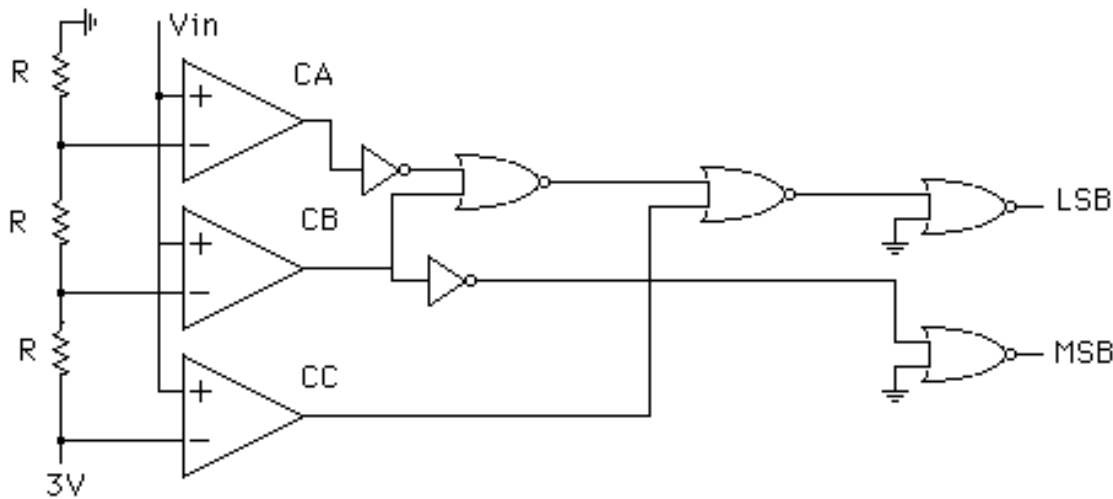

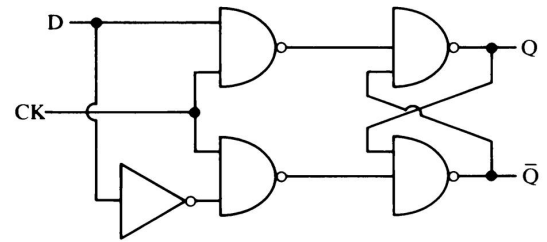8. Simpson: Problem 10, page 666

- Write a truth table.
- Write a standard schematic diagram for this flip-flop.
- This flip-flop is usually called a \_\_\_\_ flip-flop.



9. Simpson: Problem 22, page 667

Design a synchronous counter that will count through the sequence 1, 3, 5, 7, 9, 1, 3, 5, 7, 9... using JK flip-flops.