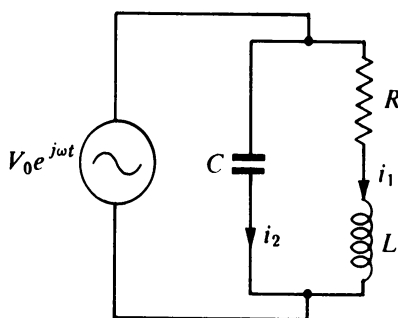



Physics 4700 HOMEWORK III

Due October 12


- Design a LC parallel circuit or tank to resonate at 1 MHz. Assume the inductance $L = 100 \mu\text{H}$ and has a DC resistance of 10Ω . What is the Q of this circuit at resonance?



- Consider the following two circuits.

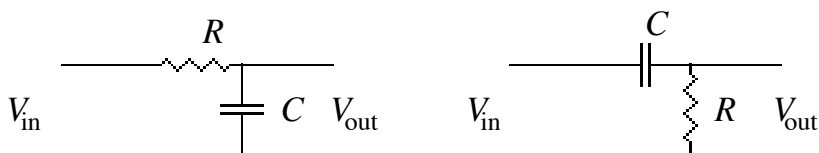


The input voltage looks like:

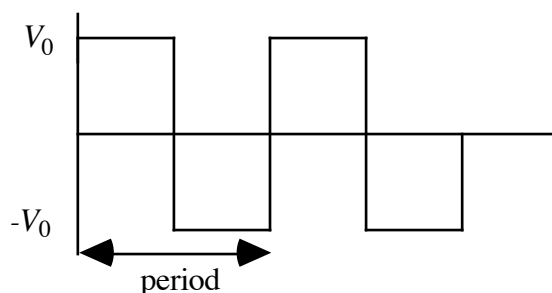

Plot the output voltage for $RC = T/20$, $T/2$, $20T$, where $T = \text{period}$, for both circuits (6 plots in all). Of the six cases which output is most like integration, and which is most like differentiation of the input signal?

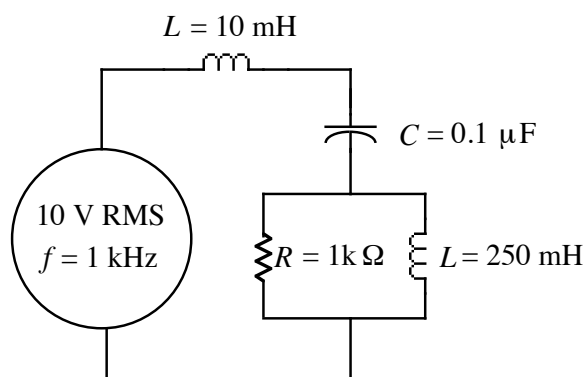
- Show that the RMS current in the $1 \text{ k}\Omega$ resistor is 6.5 mA . If the AC voltage source was replaced by a battery, what would the current in the resistor be?



- We want to design a tuner (actually a band pass filter) for an AM radio station whose frequency is $f = 700 \text{ kHz}$. The tuner must be able to detect the AM sidebands which are

located at ± 5 kHz (695 kHz and 705 kHz) from the central frequency. An easy way to achieve the above is to use a series RLC circuit and take V_R for the output voltage. The resonant frequency of this circuit is that of the radio station. The rest of the circuit parameters are fixed by matching the 3 dB points of the circuit to the upper and lower sidebands. Calculate the value of R and L necessary for the above circuit if $C = 300$ pF.

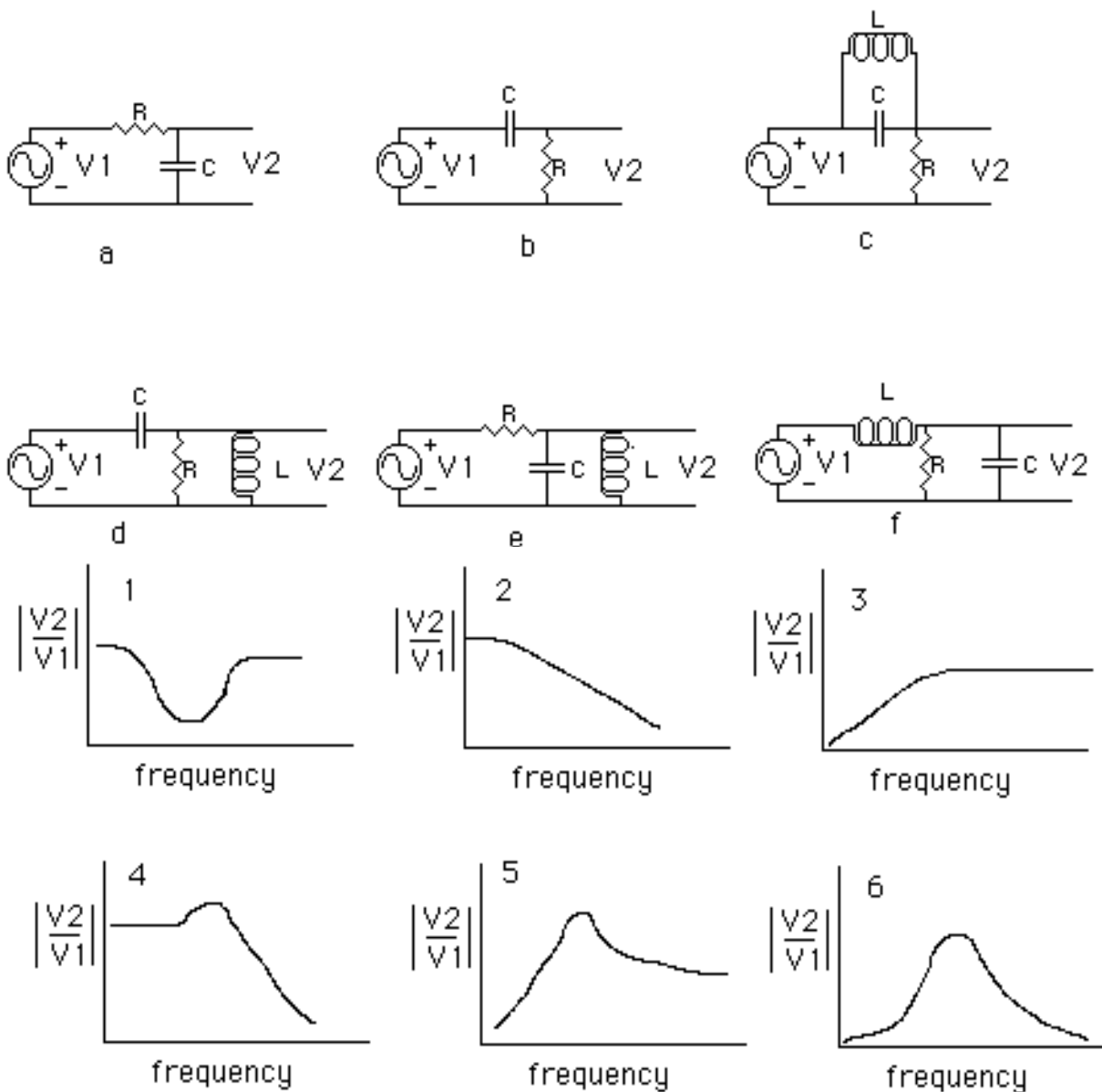5. For each of the following circuits identify the corresponding magnitude Bode plot. For most of the cases the Bode plot can be identified by considering the limits $\omega \rightarrow 0$ and $\omega \rightarrow \infty$.



6. For each of the six circuits in problem 5), find an expression for the gain $|V_2/V_1|$ in terms of R , L , and C .