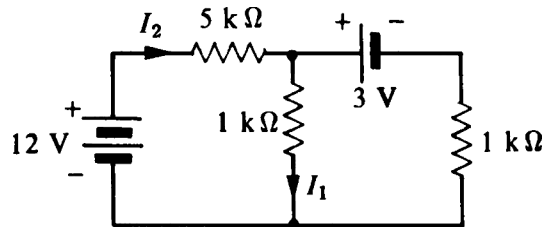


## Physics 4700 HOMEWORK 2

Due Sept 27

Hint: Use Kirchhoff's voltage or current law to solve this problem.

1. Calculate  $I_1$  and  $I_2$ .



2. This is a review problem on complex numbers. Manipulating complex numbers will become important when we discuss AC circuits.

Let  $A = 2 + 4j$

$B = -1 + 3j$

$C = 3 - 2j$

Find the magnitude and phase of,

a.  $A, B$  and  $C$



b.  $(A + B)/C$

c.  $(2A - 3B^*)/(A - C^*)$ ,  $*$  = complex conjugate

3. A current of 1 mA charges a capacitor of 1  $\mu\text{F}$  capacitor. How long does it take for the capacitor to reach 10 V?


Hint:  $V_{\text{rms}}$  for each waveform is not zero.

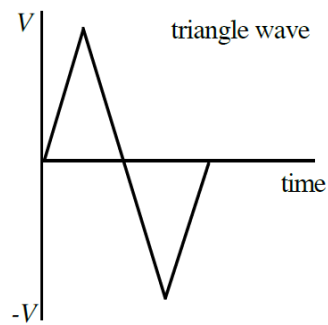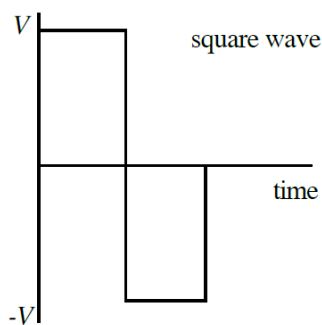4. Calculate the  $V_{\text{RMS}}$  for the following waveforms:




Hint: Simplify the equation to solve for magnitude and phase of impedance

5. Calculate the impedance  $Z_{AB}$  in the form  $a + jb$  and  $|Z|e^{j\theta}$ .

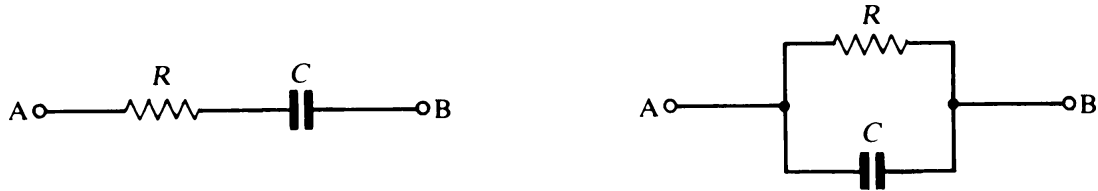

Hint: Simplify the equation to solve for magnitude and phase of impedance

6. Calculate the impedance  $Z_{AB}$  in the form  $a + jb$  and  $|Z|e^{j\theta}$ .

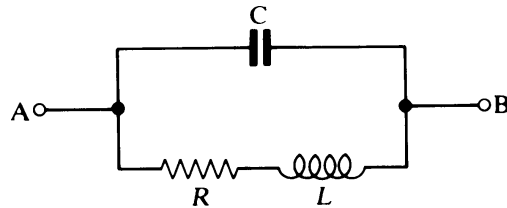


Hint: Remember  $\omega$  is angular frequency

7. Design a low pass RC filter that will attenuate a 60 Hz sinusoidal voltage by 12 dB relative to the DC gain. Use a  $100\ \Omega$  resistance. Explain in words why the low pass RC filter attenuates the high frequencies.
8. For a low pass RC filter prove that
- at the frequency  $\omega = 1/RC$  the voltage gain equals  $0.707 = \frac{1}{\sqrt{2}}$
  - the rise time of the output pulse equals  $2.2RC$  for a zero rise time input pulse (Rise time is the time for a pulse to rise from 10% to 90% of the maximum value.)

Hint: Read about Thevenin's theorem before solving the problem

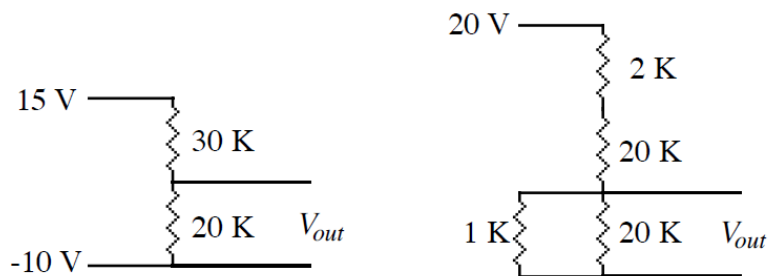9. Draw the Thevenin equivalent circuit for the following two circuits:  
(note: the load resistor has already been taken out of the circuit, if it were in the circuit, it be across the  $V_{out}$  terminals).



Hint: Solve for  $\omega_0$  and  $\Delta\omega$ . Don't just state their final answers from a book

10. For a high Q parallel RLC circuit prove that  $Q = \omega_0/\Delta\omega$ , where  $\omega_0$  is the (angular) resonant frequency and  $\Delta\omega$  is the width at the half power points.