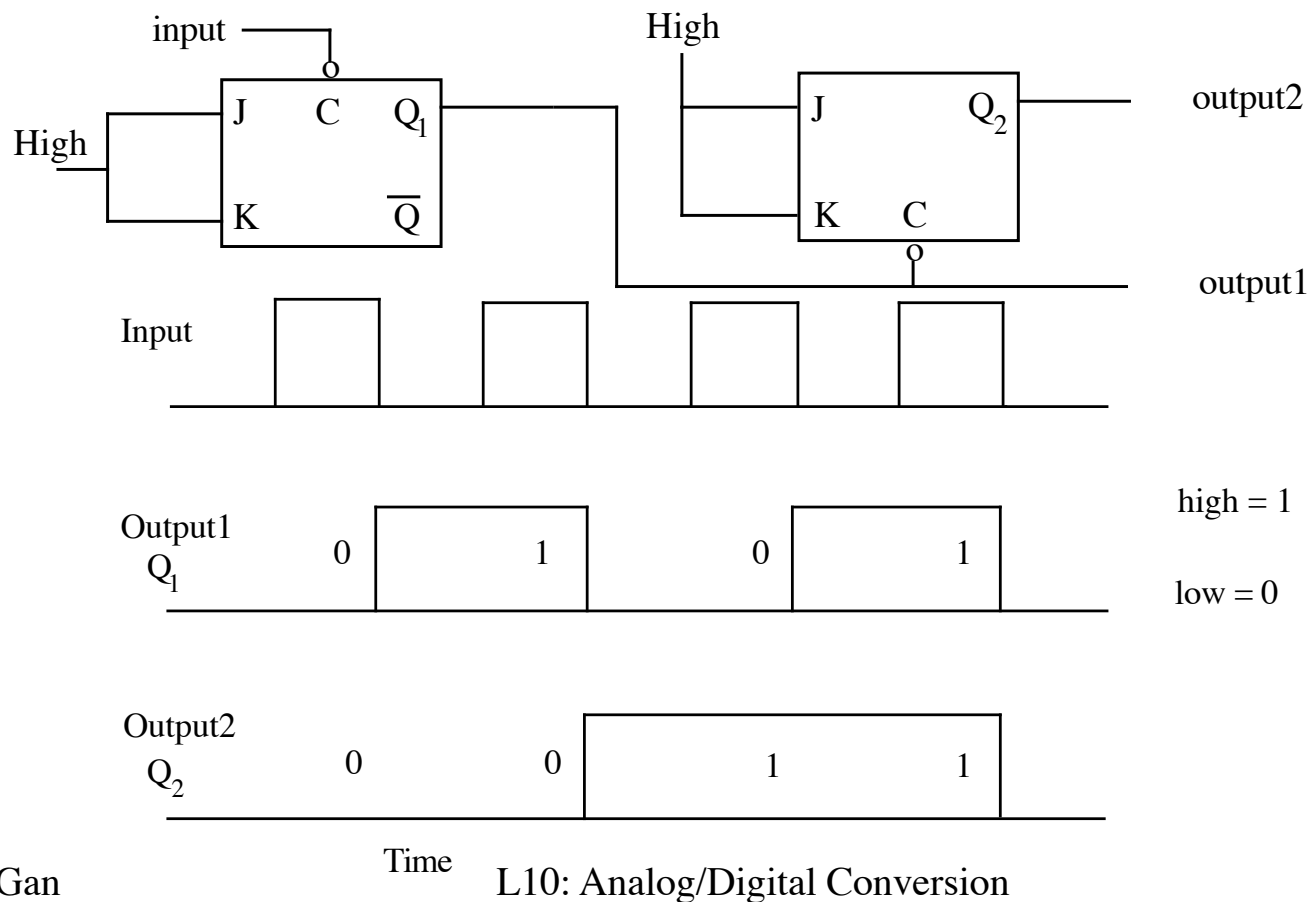


## Lecture 10: Analog/Digital Conversion


- Example: Counter made from two JK flip-flops.
  - ◆ This circuit counts from 0 1 2 3 0 1 2 3 0...
  - ◆  $Q_1$  is the lowest order bit,  $Q_2$  is the higher order bit.
  - ◆ The output is a binary number =  $Q_2Q_1$ .
  - ◆ The o's on the clock means that the output transition occurs on the trailing edge of the clock pulse.
  - ◆ Output of circuit is most conveniently displayed using a timing diagram:



- A few words about clocking the flip-flops and timing of inputs.
  - ◆ Setup time:
 


For each type of flip-flop there is a minimum specified time relative to the clock pulse during which time the input(s) to the FF must be stable (i.e. not change logic levels).
  - ◆ Hold time:
 

For each type of flip-flop there is a minimum specified time after Q changes state that the input(s) to the FF must be stable (i.e. not change logic levels).
  - ◆ Example: 74LS112 JK flip-flop (the one we use in lab)
    - This FF changes state (Q) relative to the trailing edge of the clock.
    - The setup time is 20 nsec ( $2 \times 10^{-8}$  sec) while the hold time is  $\approx 0$  nsec.
    - The maximum clock speed of this FF is 30 MHz.

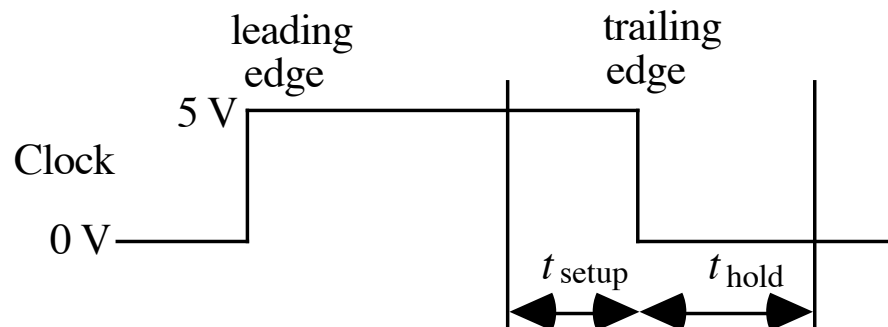

⇒ the data on J and K must be stable for at least  $t_{\text{setup}} + t_{\text{hold}}$ .

- Sometimes circuits with flip-flops are classified according to how the clock is distributed to the FF's.
  - ◆ There are two clocking schemes:
    - Synchronous: All FF's are clocked at the same time.
      - The easiest way to do this is to use one clock and distribute it to all the FF's.
    - Asynchronous: FF's are clocked at different times, usually by different clocks.
      - The previous circuit with two flip-flops was an example of this type of circuit.
        - The first FF was clocked by a “clock”.
        - The second FF was clocked by the output (Q) of the first FF.

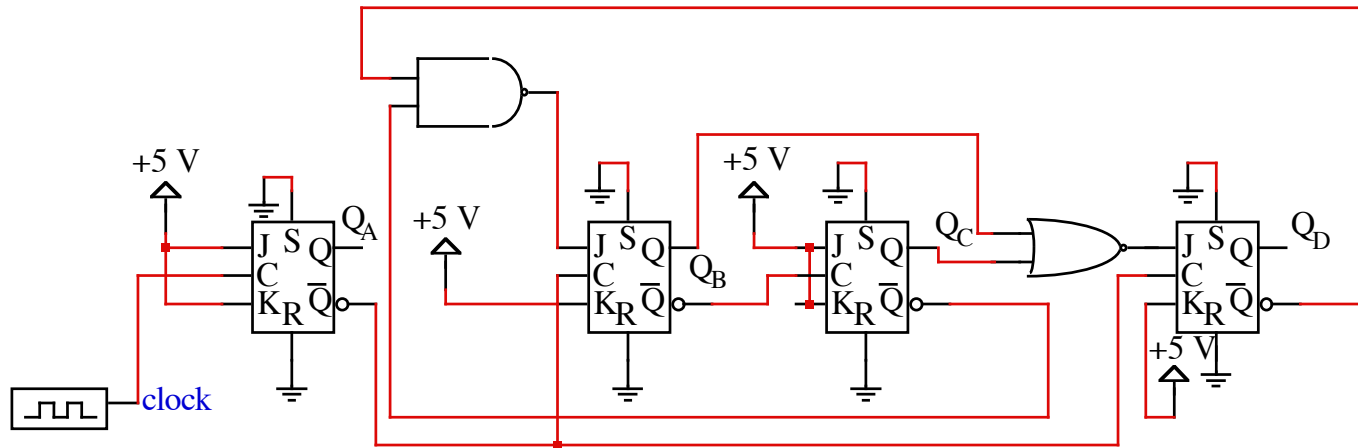


$$J_A = 1 \quad J_B = \overline{Q_C} \overline{Q_D} = Q_C + Q_D \quad J_C = 1 \quad J_D = \overline{Q_B} + Q_C = \overline{Q_B} \overline{Q_C}$$

$$K_A = 1 \quad K_B = 1 \quad K_C = 1 \quad K_D = 1$$

Divide by 10 ripple down counter  
(counts from 9 to zero)

Asynchronous counter

 

## Digital to Analog Conversion (DAC):

- There are two simple circuits commonly used to convert a digital signal to an analog voltage.

- ◆ **Weighted Resistor Ladder:**

- We assume that the input voltages ( $V_1$ ,  $V_2$ ,  $V_3$ , and  $V_4$ ) are logic levels.
- Let us assume a high = 1 V and a low = 0 V.
- The output voltage is given by:

$$V_{\text{out}} = \frac{\frac{R_b}{R_a} + 1}{\frac{1}{R_0} + \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} \left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_4}{R_4} \right]$$


- If we choose the resistors as follows:

$$R_1 = R_a = 1 \text{ k}\Omega, R_2 = 2 \text{ k}\Omega, R_3 = 4 \text{ k}\Omega, \\ R_4 = R_0 = 8 \text{ k}\Omega \text{ and } R_b = 15 \text{ k}\Omega,$$


- ⇒ we get the following simple relationship for  $V_{\text{out}}$ :

$$V_{\text{out}} = 8V_1 + 4V_2 + 2V_3 + V_4$$

- If  $V_{\text{in}}$  represents a binary number (e.g. 1001 =  $V_1V_2V_3V_4$  with  $V_1$  being the highest order bit)
  - the output voltage varies from 0 to 15 Volts (remember  $V_1..V_4$  are all either 0 or 1 V)
  - example: the digital input 1001 has an analog output of 9 V = (8 + 1) V.
- Unfortunately there are several bad points with this conversion scheme:
  - the output can be a large voltage (e.g. 15 V)
  - circuit needs 5 high precision resistors (expensive)
  - the current (and therefore power) in the resistors varies by a factor of 15

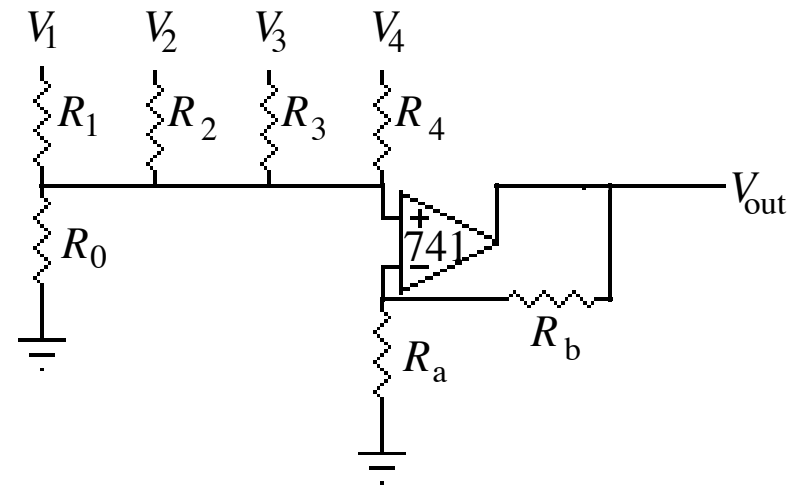

- Binary Ladder Network (R-2R Network):

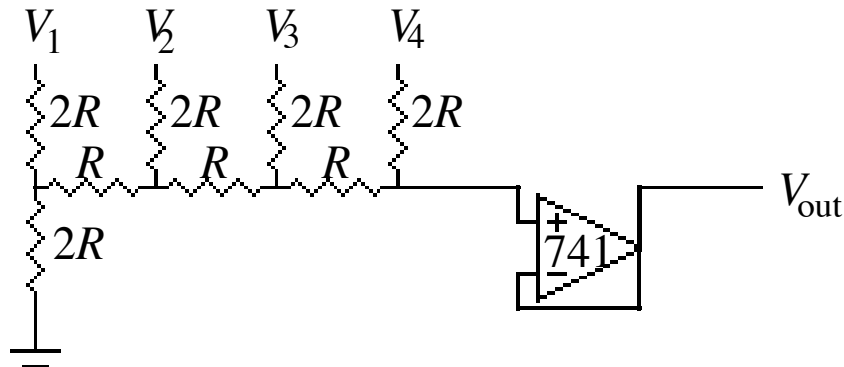

This circuit fixes up many of the problems in previous circuit

- The output voltage for this circuit is:

$$V_{\text{out}} = V_4/2 + V_3/4 + V_2/8 + V_1/16$$

- This circuit needs only 2 precision resistors compared with the 5 in the previous design.

- Power dissipated in the resistors varies by a factor of 2, compared with 15 in the previous design.

- There are still some bad points:


- need precision components
- the output voltage will usually be a fraction of the input (low noise immunity)
  - Example: if  $V_{\text{in}} = 1001$ , then  $V_{\text{out}} = 1/2 + 0/4 + 0/8 + 1/16 = 9/16$  V for high = 1 V.

## Analog to Digital Conversion (ADC)


- Parallel A to D conversion (“Flash Encoder” or Flash ADC)

- very fast and very simple method
- use comparators for the conversion
- Example: one bit ADC using one comparator

 - $V_{\text{out}} = 1$  (high) if  $V_{\text{in}} > V_{\text{ref}}$
- $V_{\text{out}} = 0$  (low) if  $V_{\text{in}} < V_{\text{ref}}$



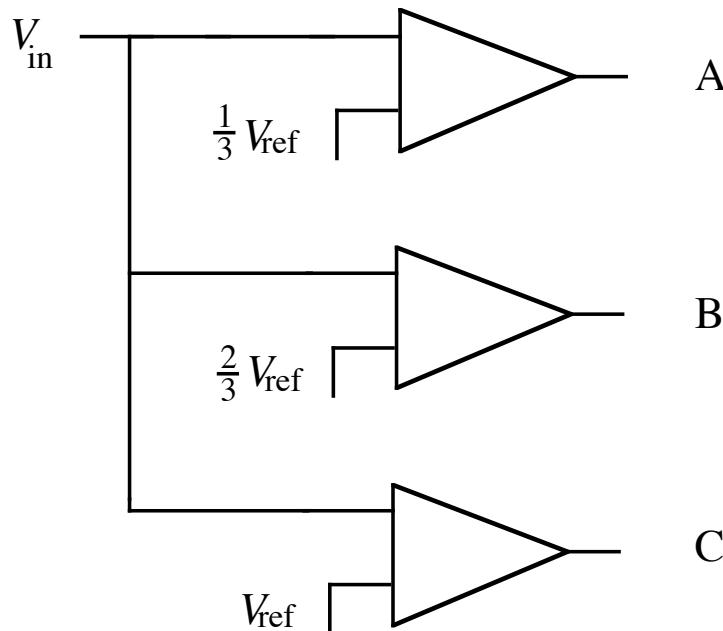- ◆ How many comparators do we need for a given accuracy?
  - Suppose we want to convert an analog number into a 2 bit digital number.
    - For 2 bits there are 4 possible outcomes (00, 01, 10, 11), it takes 3 comparators.
- ◆ Example: 2 bit parallel converter



Truth Table				
$V_{in}$	A	B	C	Output
$< \frac{1}{3} V_R$	0	0	0	0
$\frac{1}{3} V_R < V_{in} < \frac{2}{3} V_R$	1	0	0	1
$\frac{2}{3} V_R < V_{in} < V_R$	1	1	0	2
$> V_R$	1	1	1	3


- Logic gates are needed to implement the truth table:

$$LSB = A\bar{B}\bar{C} + ABC = A(\bar{B}\bar{C} + BC)$$


$$MSB = A\bar{B}\bar{C} + ABC = AB(C + \bar{C}) = AB$$

- ◆ There are two problems with this scheme:

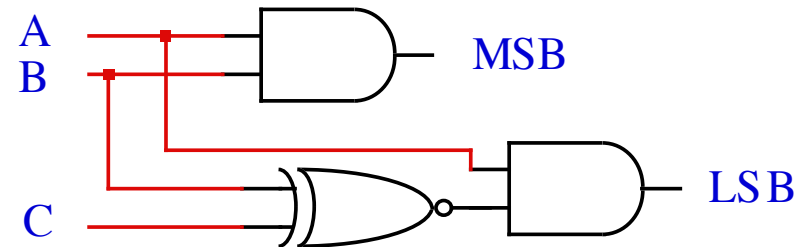- Need lots of comparators:  $2^n - 1$  for n bit accuracy.
  - If we want 1 part in 1000 accuracy (0.1%), it takes 10 bits
    - ⇒  $2^{10} - 1 = 1023$  comparators!
- Number of logic gates necessary to code the output is large and the logic gets complicated.



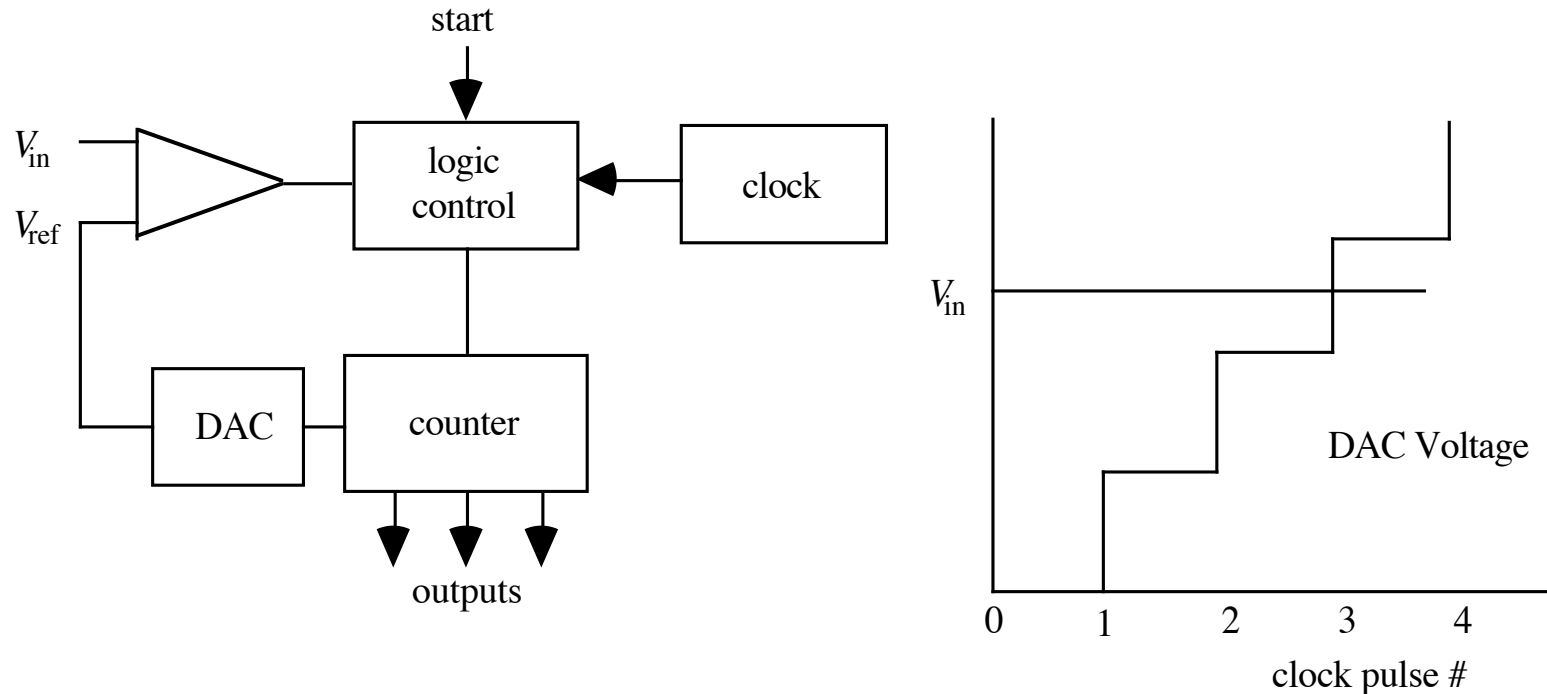- Counter ADC (staircase method):
  - Good news: only uses one comparator
  - Bad news: much more complicated than parallel method



- When  $V_{DAC} > V_{in}$ 
  - the logic circuit stops the clock
  - the counter outputs a binary number which is just the number of clock pulses
- The DAC could be:
  - an integrator
  - a resistor ladder
  - a voltage reference



- ◆ Problems with this system:
  - control logic is complicated (use microprocessors + gates +...)
  - time to digitize depends on  $V_{in}$ .
  - Example: suppose clock runs at 5 MHz, and you want 10 bit accuracy.
    - 10 bits = 1024 clock pulses.
      - ⇒ Can only digitize at 5 MHz/1024 ~ 5 kHz, *which is fairly slow!*
- Successive Approximation ADC:
  - ◆ Control logic is very complicated, but easy to program, like a binary search.
  - ◆ Conversion time is fast and almost independent of  $V_{in}$ .
  - ◆ Example: 5 bit ADC:
    - Steps for converting  $V_{in}$  into a binary number:
      - turn on MSB in DAC and compare with  $V_{in}$ .
        - output = 0 if  $V_{DAC} > V_{in}$  (steps 1, 2, 5)
        - output = 1 if  $V_{DAC} < V_{in}$  (steps 3, 4)
      - turn on next highest bit, output = 1 if  $V_{DAC} > V_{in}$
      - repeat until least significant bit is checked
      - ⇒  $n$  comparisons for  $n$  bit accuracy
      - staircase approach requires  $2^n - 1$  comparisons
      - parallel ADC requires 1 step, independent of accuracy
      - Time for a 10 bit conversion for the three methods:
 

parallel : success approx. : staircase    1:10:1023

