Lecture 6: Transistors Amplifiers

Common Emitter Amplifier ("Simplified"):

- What's common (ground) in a common emitter amp?
 - The emitter!
 - The emitter is connected (tied) to ground usually by a capacitor
 - To an AC signal this looks like the emitter is connected to ground.



- What use is a Common Emitter Amp?
 - Amplifies the input voltage (the voltage at the base of the transistor).
 - The output voltage has the opposite polarity as the input voltage.
 - We want to calculate the following for the common emitter amp:
 - Voltage Gain = V_{out}/V_{in}
 - Input Impedance
 - Output Impedance

K.K. Gan

- DC Voltage Gain:
 - The voltage gain we are about to derive is for small signals only.
 - A small signal is defined here to be in the range of a few mV.
 - As in all of what follows we assume that the transistor is biased on at its DC operating point.

 $V_{\rm out} = V_{cc} - I_{\rm C} R_{\rm C}$

- Since V_{cc} is fixed (its a DC power supply) we have for a change in output voltage V_{out} $\Delta V_{out} = -\Delta I_C R_C$
 - Δ stands for a small change in either the voltage or current.
- The input voltage is related the emitter voltage by a diode drop:

$$V_{\rm in} = V_{\rm B}$$

$$= V_{\rm E} + 0.6 \,\,{\rm V}$$

$$\Delta V_{\rm in} = \Delta V_{\rm E}$$

• We want to relate the emitter voltage to the emitter current (I_E) : $V_E = I_E R_E$

$$\Delta V_{\rm E} = \Delta I_{\rm E} R_{\rm E}$$

• We can relate the emitter and collector currents by remembering that for a transistor:

$$I_{\rm E} \approx I_{\rm C}$$

$$\Delta I_{\rm E} \approx \Delta I_{\rm C}$$

$$\Delta V_{\rm E} = \Delta I_{\rm E} R_{\rm E} = \Delta I_{\rm C} R_{\rm E}$$

$$\Delta V_{\rm in} = \Delta V_{\rm E} = \Delta I_{\rm C} R_{\rm E} = (-\Delta V_{\rm out} / R_{\rm C}) R_{\rm E}$$

K.K. Gan

Lecture 6: Transistors Amplifiers



DC voltage gain (G) for a common emitter amp:

Gain =
$$\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = -\frac{R_{\text{C}}}{R_{\text{E}}}$$
 The minus sign in the gain means that the output is the opposite polarity as the input (180° out of phase).

- What happens if $R_{\rm E} = 0???$
- Do we have infinite gain?
- No, we get a new model for the transistor.
- The base-emitter junction is a diode.
- Describe the behavior of the junction using the Ebers-Moll equation:

$$I = I_s \left[e^{q V/kT} - 1 \right]$$

$$V = V_{\rm BE}$$

$$kT/q = 25 \text{ mV at } 20^{\circ}\text{C}$$

• Neglecting the -1 term:

$$V_{\rm BE} = \frac{kT}{q} [\ln I - \ln I_{\rm s}]$$

• Calculate the dynamic resistance of the base-emitter junction,

$$r_{\rm BE} = \frac{dV_{\rm BE}}{dI}$$
$$= \frac{kT}{qI}$$
$$= 25 \times 10^{-3} / I \qquad r_{\rm BE} = 25 \ \Omega \text{ for current of 1 mA}$$
$$Gain = -\frac{R_C}{r_{\rm BE} + R_{\rm E}} \parallel X_{\rm CE}$$

K.K. Gan

Lecture 6: Transistors Amplifiers

We can now write the gain for the case $R_{\rm E} = 0$ (neglecting $X_{\rm CE}$ too):

Gain = $-R_{\rm C}/r_{\rm BE} = -R_{\rm C}(I_{\rm C}/25)$ with $I_{\rm C}$ measured in mA.

Simpson (page 227) writes an equivalent formula for the gain using the transistor parameter β and a slightly different temperature, $T = 300^{\circ}$ K.

In terms of the hybrid parameter model (we will see this model soon)

$$r_{\rm BE} = h_{\rm ie} / h_{\rm fe}$$

- Using $r_{\rm BE}$ to design a circuit is a dangerous practice as it depends on temperature
 - varies from transistor to transistor even for same type of transistor.
- Input impedance
 - Input impedance of the common emitter amp can be calculated from the equivalent circuit:



K.K. Gan

٠

- Output impedance
 - Harder to calculate than the input impedance and only a hand waving argument will be given.
 - The output impedance of the amp is the parallel impedance of $R_{\rm C}$ and the output impedance of the transistor looking into the collector junction.
 - The collector junction is reversed biased and hence looks like a huge resistor compared to $R_{\rm C}$.
 - The output impedance is simply $R_{\rm C}$
 - assume that the load impedance (the thing the amp is hooked up to) is less than $R_{\rm C}$.



• Current Gain: As always we can use Kirchhoff's current rule.

$$I_{\rm E} = I_{\rm B} + I_{\rm C}$$
$$= I_{\rm B}(\beta + 1)$$
$$\frac{\Delta I_{\rm E}}{\Delta I_{\rm B}} = \beta + 1$$
$$\frac{\Delta I_{\rm out}}{\Delta I_{\rm in}} = \beta + 1$$

- Since a typical value for β is 100, there is lots of current gain.
- Input impedance:
 - By definition the input impedance is

$$R_{\rm in} = \frac{\Delta V_{\rm in}}{\Delta I_{\rm in}}$$
$$= \frac{\Delta V_{\rm B}}{\Delta I_{\rm B}}$$
$$= \frac{\Delta V_{\rm E}}{\Delta I_{\rm E} / (\beta + 1)}$$
$$= \frac{\Delta I_{\rm E} R_{\rm E}}{\Delta I_{\rm E} / (\beta + 1)}$$
$$R_{\rm in} = (\beta + 1) R_{\rm E}$$

- Since $R_{\rm E}$ is usually a few k Ω and β is typically 100
 - the input impedance of the common collector amp is large.





K.K. Gan



$$V_{\text{tin}} = \frac{V_{\text{in}}R_{\text{in}}}{R_{\text{in}} + R_{\text{s}}}$$
$$\approx \frac{V_{\text{in}}\beta R_{\text{E}}}{\beta R_{\text{E}} + R_{\text{s}}}$$

• If we look from the other (output) side of the amp with R_{out} the output impedance of the transistor

- The voltage drop at A is the same as the voltage at the base $(V_{\rm B})$ since the amp has unity gain.
- We can rewrite the equation into a voltage divider equation to find R_{out} .

$$V_{A} = \frac{V_{in}R_{E}}{R_{E} + R_{out}}$$

$$= V_{tin} = \frac{V_{in}\beta R_{E}}{\beta R_{E} + R_{s}} = \frac{V_{in}R_{E}}{R_{E} + R_{s}/\beta}$$

$$R_{out} = \frac{R_{s}}{\beta}$$

 \sim $R_{\rm out}$ is small since β is typically 100.

K.K. Gan

Lecture 6: Transistors Amplifiers

7

- What good is the common collector amp?
 - Example: In stereo systems very often loud speakers have 8 Ω input impedance. Assume that you want to drive the speakers with a 5 Volt voltage source with 92 Ω of serious resistance. Lets look at 2 ways of driving the speakers and the power each method delivers to the speaker.
 - a. Hook the speakers directly to the voltage source:



- The voltage delivered to the speaker is $(8/100)V_{in}$.
- The power delivered is:

$$P = V^2/R = (5 \times 8 / 100)^2/8 = 0.02$$
 Watts

not much power!

b. Use a common collector (emitter follower):



• An AC signal at the input sees

 $\beta R_{\rm sp} = \beta 8 \ \Omega = 800 \ \Omega$

- From the speakers point of view the amp impedance looks like $92 \ \Omega/\beta \sim 1 \ \Omega$
- The power delivered to the speaker can now be calculated: $V_{\rm sp} = (\beta 8 \ \Omega V_{\rm in})/(\beta 8 \ \Omega + 92 \ \Omega) = 0.9V_{\rm in}$

$$P_{\rm sp} = V_{\rm sp}^2 / R_{\rm sp} = (0.9 \times 5)^2 / 8 = 2.5$$
 Watts (rms)

• over a **hundred** times more power delivered to the speaker.

Emitter Followers (common collectors) are used to match high impedances to low impedances