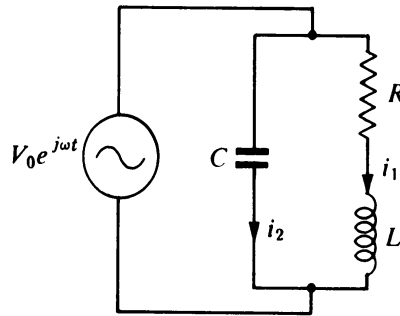



# Physics 4700 HOMEWORK III

Due February 24


- Design a LC parallel circuit or tank to resonate at 1 MHz. Assume the inductance  $L = 100 \mu\text{H}$  and has a DC resistance of  $10 \Omega$ . What is the  $Q$  of this circuit at resonance?



- Consider the following two circuits.

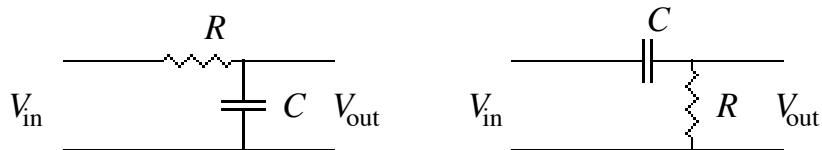


The input voltage looks like:

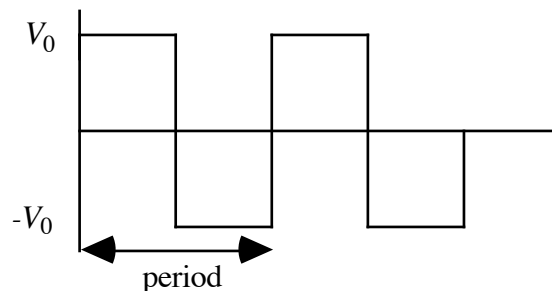

Plot the output voltage for  $RC = T/20$ ,  $T/2$ ,  $20T$ , where  $T = \text{period}$ , for both circuits (6 plots in all). Of the six cases which output is most like integration, and which is most like differentiation of the input signal?

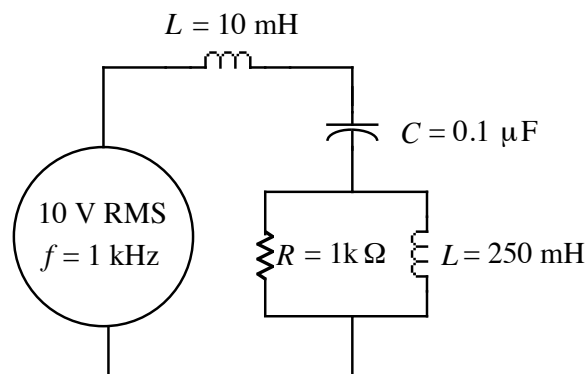
- Show that the RMS current in the  $1 \text{ k}\Omega$  resistor is  $6.5 \text{ mA}$ . If the AC voltage source was replaced by a battery, what would the current in the resistor be?



- We want to design a tuner (actually a band pass filter) for an AM radio station whose frequency is  $f = 700 \text{ kHz}$ . The tuner must be able to detect the AM sidebands which are

located at  $\pm 5$  kHz (695 kHz and 705 kHz) from the central frequency. An easy way to achieve the above is to use a series RLC circuit and take  $V_R$  for the output voltage. The resonant frequency of this circuit is that of the radio station. The rest of the circuit parameters are fixed by matching the 3 dB points of the circuit to the upper and lower sidebands. Calculate the value of  $R$  and  $L$  necessary for the above circuit if  $C = 300$  pF.

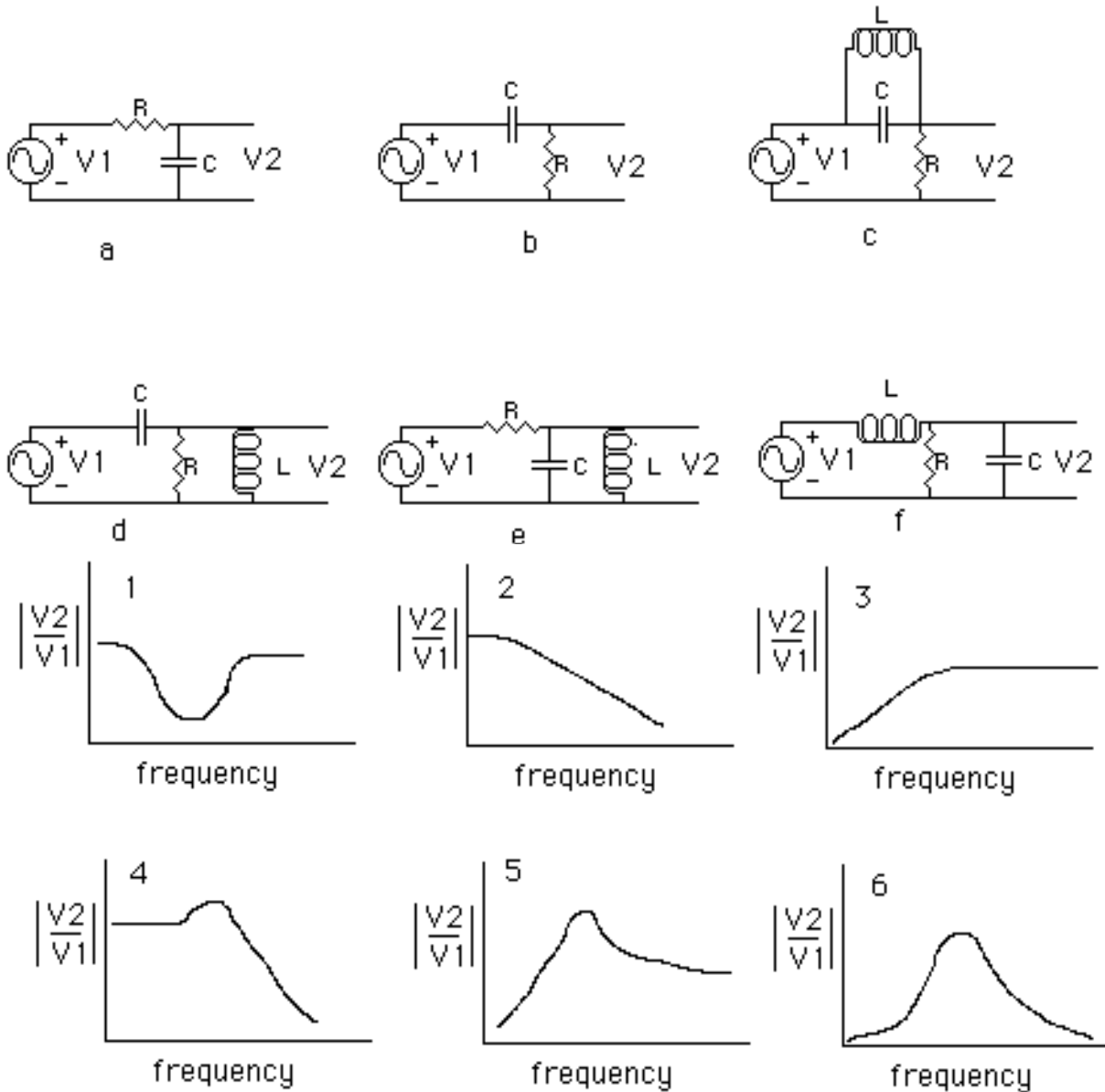5. For each of the following circuits identify the corresponding magnitude Bode plot. For most of the cases the Bode plot can be identified by considering the limits  $\omega \rightarrow 0$  and  $\omega \rightarrow \infty$ .



6. For each of the six circuits in problem 5), find an expression for the gain  $|V_2/V_1|$  in terms of  $R$ ,  $L$ , and  $C$ .