
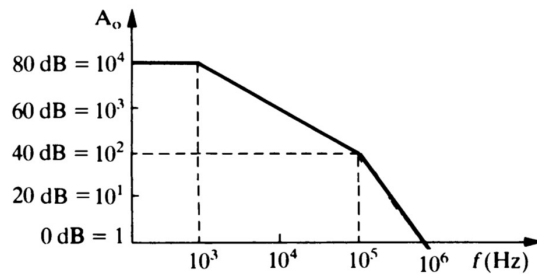


**Physics 4700 HOMEWORK VI**  
**Due March 29**


Note: Determine the gain roll-off vs. frequency for both parts a and b and compare it to the open loop gain roll-off vs. frequency for the op amp.

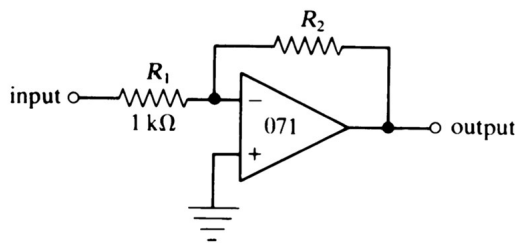1. The open loop gain versus frequency for an uncompensated op amp is shown below. Would the inverting amplifier be stable for
  - a.  $R_2 = 10 \text{ k}\Omega$ ?
  - b.  $R_2 = 100 \text{ k}\Omega$ ?




Note: The  $\pm 15 \text{ V}$  power supplies for the op amp limit the output amplitude.

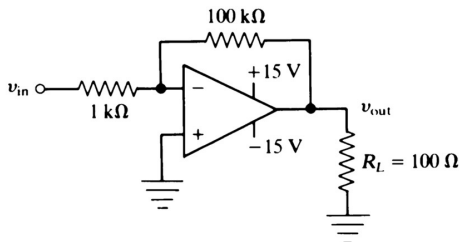2. Although the output resistance of most op amps is extremely low when negative feedback is used, a typical inexpensive op amp can supply only a maximum current of approximately 25 mA. Calculate the maximum amplitude of a sinusoidal input (at low frequencies  $\sim 1 \text{ kHz}$ ) that will produce an undistorted output across  $R_L = 100 \Omega$ . Repeat it for  $R_L = 1 \text{ k}\Omega$ .



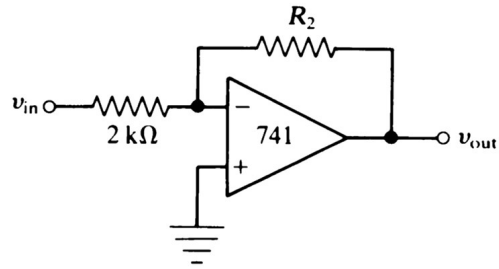3. Design a summing amplifier circuit to sum from inputs  $v_A$ ,  $v_B$ ,  $v_C$ ,  $v_D$  and to produce an output of  $v_o = v_A + 2v_B + 4v_C + 8v_D$ .
4. Design a voltage-to-current converter to convert a 1 mV input voltage to a 1 mA current through a 1 kΩ load resistor.
5. Design an op-amp differentiator whose output is,
 
$$v_{out} = -(10^{-6}) \frac{dv_{in}}{dt}$$
6. For a 741 op-amp with a slew rate of  $0.5 \text{ V}/\mu\text{s}$ , for  $R_2 = 20 \text{ k}\Omega$ , what is the maximum frequency of a sinusoidal input to avoid slew rate distortion in the output? The input peak-to-peak amplitude is 10 mV. Repeat for  $R_2 = 200 \text{ k}\Omega$ .



Note: For part c, you cannot just lower the power supply input to the op amp

7. The comparator is bipolar.
  - a. Sketch the output waveform if  $V_{bb} = +5$  V.
  - b. Repeat for  $V_{bb} = -5$  V
  - c. How would you change the circuit to produce output voltages of  $+5$  V and  $-0.6$  V?

