Some Definitions:

Current (I):	Amount of electric charge (Q) moving past a point per unit time. I = dQ/dt = Coulombs/sec units = Amps (1 Coul. = $6x10^{18}$ electrons)
$\frac{\text{Voltage }(V):}{\Rightarrow}$ \Rightarrow \Rightarrow	Work needed to move charge from point a to point b. Work = $V \ge Q$ Volt = Work/Charge = Joules/Coulomb Voltage is always measured with respect to something. "ground" is defined as zero Volts.
<u>DC:</u>	Stands for <u>direct current</u> . In a DC circuit the current and voltage are constant as a function of time.
<u>Power (<i>P</i>):</u>	Rate of doing work. P = dW/dt, units = Watts
<u>Ohms Law:</u>	Linear relationship between voltage and current. $V = I \alpha R$ $R = \text{Resistance} (\Omega)$, units = Ohms
	nonlinear (diode) linear



Joules Law: When current flows through a resistor energy is dissipated.

W = QV P = dW/dt = VdQ/dt + QdV/dtbut dV/dt = 0 for DC circuit and averages to 0 for AC. Power = VdQ/dt = VdUsing Ohms law \Rightarrow $P = \tilde{I^2}R = V^2/R$ \Rightarrow

100 Watts = 10 V and 10 Amps or 10 V through 1 Ω



y <u>Convention</u>: Current flow is in the direction of <u>positive</u> charge flow. When we go across a battery in direction of current $(- \rightarrow +)$ we get a +V. Voltage drop across a resistor in direction of current $(+ \rightarrow -)$ gives -IR.

Conservation of Energy says that sum of potential drops around the circuit has to add up to zero.

For above circuit: V - IR = 0 or V = IR!!

Next simple(st) circuit: Two resistors in series (same current in each R)



Conservation of charge says that $I_1 = I_2 = I$ **at point A.** $V = I(R_1 + R_2) = IR$ with $R = R_1 + R_2$

Resistors in Series Add: $R = R_1 + R_2 + R_3...$

What's voltage across R_2 ?

 $V_2 = I_2 R_2 = V R_2 / (R_1 + R_2)$ "Voltage Divider Equation"

Two resistors in parallel (same voltage across each R)

+
$$I \rightarrow A$$

 $\downarrow V \stackrel{+}{-} I_1 \downarrow R_1 I_2 \downarrow R_2$
At point A: $I = I_1 + I_2$
Also we have: $V = I_1R_1$ and $V = I_2R_2$
so: $I = V/R_1 + V/R_2 = V/R$
 $1/R = 1/R_1 + 1R_2$
 $\therefore R = \frac{R_1R_2}{R_1 + R_2}$
Parallel Resistors add like: $1/R = 1/R_1 + 1/R_2 + 1/R_3 + ...$

In a circuit with 3 resistors (series and parallel), what's I_2 ?



From Ohms law we know $I_2 = V_2/R_2$ Try to reduce to a simpler circuit



Now looks like a series circuit!

$$R_{23} = R_2 \| R_3 = \frac{R_2 R_3}{R_2 + R_3}$$

 $R = R_1 + R_2 \parallel R_3$ and $I = V/R = V/(R_1 + R_{23})$ Can now find V_2 using $V_2 = IR_{23}$

$$V_{2} = \frac{V}{R_{1} + \frac{R_{2}R_{3}}{R_{2} + R_{3}}} \times \frac{R_{2}R_{3}}{R_{2} + R_{3}}$$
$$= \frac{VR_{2}R_{3}}{R_{1}R_{2} + R_{1}R_{3} + R_{2}R_{3}}$$
$$I_{2} = \frac{V_{2}}{R_{2}}$$
$$= \frac{VR_{3}}{R_{1}R_{2} + R_{1}R_{3} + R_{2}R_{3}}$$

Note: if $R_3 \rightarrow \infty$ then $I_2 = I = V/(R_1 + R_2)$ as expected!

Kirchoff's Laws

We can formalize and generalize the previous examples using Kirchoff's Laws:

1) $\Sigma I = 0$ at a node. This is a restatement of conservation of charge. 2) $\Sigma V = 0$ around a closed loop. This is just conservation of energy.



at node B: $I_1 = I_2 + I_3$

at node E: $I_1 = I_2 + I_3$ (Same as above equation, there's no new info here)

Again, as with previous examples solve for I₂

at node B from loop ABEF from loop ACDF $I_1 = I_2 + I_3 \text{ or } I_1 - I_2 - I_3 = 0$ $V - I_1R_1 - I_2R_2 = 0$ $V - I_1R_1 - I_3R_3 = 0$

We have 3 linear equations with 3 unknowns (I_1, I_2, I_3) We will always wind up with as many linear equations as unknowns!

Can use matrix methods to solve these equations: V = RI,

with V and I column vectors and \hat{R} a matrix (3x3).

If we have n (n = 3 here) linearly independent equations then the determinant of $R \neq 0$. See any decent book on linear algebra or Diefenderfer Appendix A.

$$\begin{bmatrix} V \\ V \end{bmatrix} \begin{bmatrix} R_1 & R_2 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I \\ V \end{bmatrix} = \begin{bmatrix} R_1 & 0 & R_3 \end{bmatrix} \begin{bmatrix} I_2 \\ I_2 \end{bmatrix}$$
$$\begin{bmatrix} 0 \\ 1 & -1 & -1 \end{bmatrix} \begin{bmatrix} I_3 \end{bmatrix}$$

Can solve for I_2 using determinants:

$$I_{2} = \frac{\begin{bmatrix} R_{1} & V & 0 \\ \det & R_{1} & V & R_{3} \end{bmatrix}}{\begin{bmatrix} 1 & 0 & -1 \end{bmatrix}} = \frac{VR_{3}}{R_{1}R_{2} + R_{1}R_{3} + R_{2}R_{3}}$$
$$\det \begin{bmatrix} R_{1} & 0 & R_{3} \\ 1 & -1 & -1 \end{bmatrix}$$

Note: This is the same solution as on previous page!

Measuring Things

<u>Voltmeter:</u> <u>Always</u> put in <u>parallel</u> with what you want to measure.



If no voltmeter we would have:

$$V_{AB} = \left[\frac{R_L}{R_S + R_L}\right] V$$

If the voltmeter has a finite resistance R_m then circuit looks like:



From previous page we have:

$$V_{AB}^{*} = \left[\frac{R_{m} \|R_{L}}{R_{S} + R_{m} \|R_{L}}\right] V$$
$$= \frac{V R_{m} R_{L}}{R_{S} R_{L} + R_{m} R_{L} + R_{S} R_{m}}$$
$$= \frac{V R_{L}}{R_{L} + R_{S} + \frac{R_{S} R_{L}}{R_{m}}}$$
$$\cong V_{AB} \quad \text{if } R_{L} << R_{m}$$

A good voltmeter has high resistance (> $10^6 \Omega$)

Ammeter: Measures Current. Always put in series with what you want to measure.



Without meter: $I = V/(R_S + R_L)$ With meter: $I^* = V/(R_S + R_L + R_m)$ So a good ammeter has $R_m << (R_S + R_L)$, i.e. low (0.1-1 Ω) resistance.

Thevenin's Equivalent circuit Theorem

"Any network of resistors and batteries having 2 output terminals may be replaced by a series combination of resistor and battery."

Useful when solving complicated (!?) networks:

Solve problems by finding V_{eq} and R_{eq} for circuit without load, then add load to circuit. Use basic voltage divider equation:



Two rules for using Thevenin's Thereom:

1) Take the load out of the circuit to find V_{eq} :



2) Short circuit all power supplies (batteries) to find R_{ea} :



Can now solve for I_L as in previous examples:

$$I_{L} = \frac{V_{eq}}{R_{eq} + R_{L}}$$
$$= \left[\frac{VR_{3}}{R_{1} + R_{3}}\right] \times \frac{1}{\frac{R_{1}R_{3}}{R_{1} + R_{3}} + R_{L}}$$
$$= \frac{VR_{3}}{R_{1}R_{L} + R_{1}R_{3} + R_{L}R_{3}}$$

Same answer as previous examples!