


Review from last week:

Flip-Flops:

Basic counting unit in computer
 counters
 shift registers
 memory

 Example: RS flip-flop or Reset-Set flip-flop

Flip-flops, like logic gates are defined by their truth table. Flip-flops are controlled by an external clock pulse.




Q_n is the present state of the FF and Q_{n+1} will be the output after the clock enables the FF to look at its inputs (R and S).

Many FF's change state ($Q_n \neq Q_{n+1}$) on the trailing edge of the clock.


Note: *The state with $R = S = 1$ is undefined. The output is not predictable!*

 Example: D flip-flop (Like RS but only one input)



 Example: JK flip-flop


JKFF is like the RSFF except that both inputs (J and K) can be high (1).



Most JKFF's have a connection for forcing $Q = 0$ (reset) or forcing $Q = 1$ (set).

 Example: T (*Toggle*) flip-flop

T flip-flop is like the JKFF with both inputs (J and K) tied to each other.



- A few words about clocking the flip-flops and timing of inputs.

Setup time:

For each type of flip-flop there is a minimum specified time relative to the clock pulse during which time the input(s) to the FF must be stable (i.e. not change logic levels).

Hold time:


For each type of flip-flop there is a minimum specified time after Q changes state that the input(s) to the FF must be stable (i.e. not change logic levels).

Example: 74LS112 JK flip-flop (the one we use in lab)

This FF changes state (Q) relative to the trailing edge of the clock.

The setup time is 20 nsec (2×10^{-8} sec) while the hold time is \square 0 nsec.

 The maximum clock speed of this FF is 30 MHz.



Thus the data on J and K must be stable for at least $t_{\text{setup}} + t_{\text{hold}}$.


- Sometimes circuits with flip-flops are classified according to how the clock is distributed to the FF's.

There are two clocking schemes:


Synchronous: All FF's are clocked at the same time. The easiest way to do this is to use one clock and distribute it to all the FF's.

Asynchronous: FF's are clocked at different times, usually by different clocks. Last week's example was an example of this type of circuit. The first FF was clocked by a "clock", while the second FF was clocked by the output (Q) of the first FF.

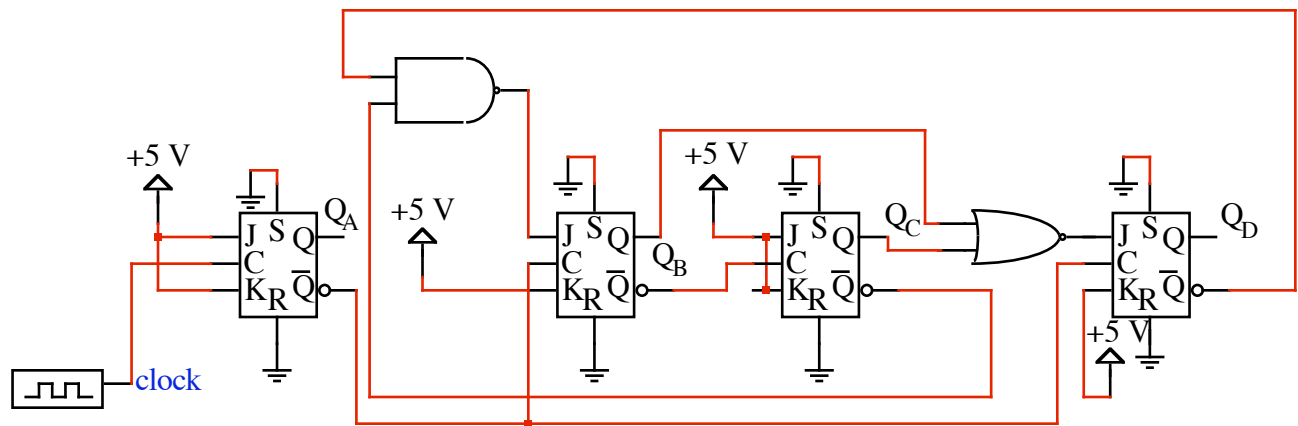Example: Divide by 10 ripple down counter (counts from 9 to zero)
Asynchronous counter


 
$$\begin{array}{llll} J_A = 1 & J_B = \overline{Q_C Q_D} = Q_C + Q_D & J_C = 1 & J_D = \overline{Q_B + Q_C} = \overline{Q_B} \overline{Q_C} \\ K_A = 1 & K_B = 1 & K_C = 1 & K_D = 1 \end{array}$$




Conversion between Analog and Digital Signals

- Digital to Analog Conversion (DAC): There are two simple circuits commonly used to convert a digital signal to an analog voltage.

Weighted Resistor Ladder: The circuit is shown below.

 We assume that the input voltages (V_1 , V_2 , V_3 , and V_4) are logic levels. For this example let us use TTL levels and assume a high = 3 V and a low = 0 V.



The output voltage is given by:

$$V_{\text{out}} = - \frac{\frac{R_b}{R_a} + 1}{\frac{1}{R_0} + \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_4}{R_4} \right]$$

If we choose the resistors as follows:

$R_1 = R_a = 1 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, $R_3 = 4 \text{ k}\Omega$, $R_4 = R_0 = 8 \text{ k}\Omega$ and $R_b = 15 \text{ k}\Omega$,
then we get the following simple relationship for V_{out} :

$$V_{\text{out}} = 8V_1 + 4V_2 + 2V_3 + V_4$$


Thus if V_{in} represents a binary number (e.g. 1001 = $V_1 V_2 V_3 V_4$ with V_1 being the highest order bit) then the output voltage varies from 0 to 45 Volts (remember $V_1 \dots V_4$ are all either 0 or 3 V). Therefore the digital input 1001 has an analog output of 27 V = $(3 \times 8 + 3)$ V.

Unfortunately there are several bad points with this conversion scheme:

- a) the output can be a large voltage (e.g. 45 V)
- b) circuit needs 5 high precision resistors (expensive)
- c) the current (and therefore power) in the resistors varies by 15.

The following circuit fixes up many of these problems:

Binary Ladder Network (R-2R Network):

 

The output voltage for this circuit is:

$$V_{\text{out}} = V_1/2 + V_2/4 + V_3/8 + V_4/16$$

This circuit needs only 2 values of precision resistors compared with the 5 of the previous design. Also the power dissipated in the resistors only varies by a factor of 2, compared with the previous factor of 15.

There are still some bad points:

- a) still need precision components
- b) the output voltage will usually be a fraction of the input (low noise immunity)

For example if $V_{\text{in}} = 1001$, then $V_{\text{out}} = 3/2 + 0/4 + 0/8 + 3/16 = 27/16$ V for TTL logic levels.


• Analog to Digital Conversion (ADC)

Parallel A to D conversion ("Flash Encoder" or Flash ADC)

very fast and very simple method

use comparators for the conversion

 Example: one bit ADC using one comparator




$V_{\text{out}} = 1$ (high) if $V_{\text{in}} > V_{\text{ref}}$

$V_{\text{out}} = 0$ (low) if $V_{\text{in}} < V_{\text{ref}}$

How many comparators do we need for a given accuracy?


Suppose we want to convert an analog number into a 2 bit digital number.

For 2 bits there are 4 possible outcomes (00, 01, 10, 11), it takes 3 comparators.

 Example: 2 bit parallel converter

Truth Table				
V_{in}	A	B	C	Output
$< \frac{1}{3} V_R$	0	0	0	0
$\frac{1}{3} V_R < V_{in} < \frac{2}{3} V_R$	1	0	0	1
$\frac{2}{3} V_R < V_{in} < V_R$	1	1	0	2
$> V_R$	1	1	1	3

 Logic gates are needed to implement the truth table:



$$LSB = A\bar{B}\bar{C} + ABC = A(\bar{B}\bar{C} + BC)$$

$$MSB = A\bar{B}\bar{C} + ABC = AB(C + \bar{C}) = AB$$

There are several problems with this scheme:

1) need lots of comparators: $2^n - 1$ for n bit accuracy.

Suppose we want 1 part in 1000 accuracy (0.1%), it takes 10 bits


$$= 2^{10} - 1 = 1023 \text{ comparators!}$$

2) the number of logic gates necessary to code the output is large and the logic gets very complicated.

Counter ADC (staircase method):

Good news: only uses one comparator

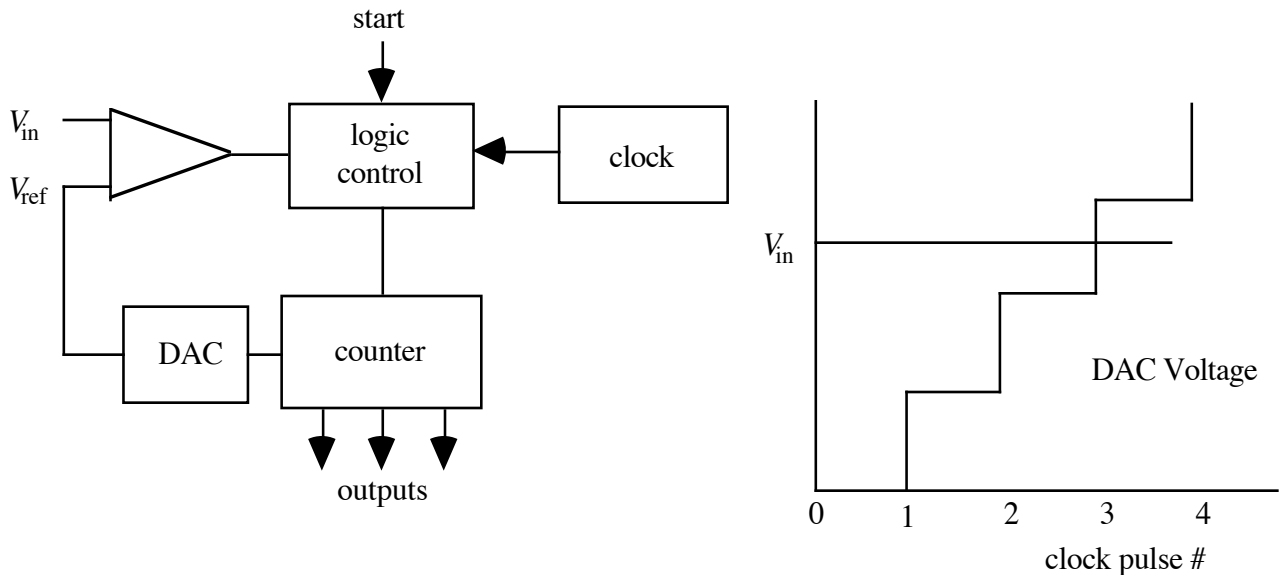Bad news: much more complicated than parallel method



When $V_{DAC} > V_{in}$ the logic circuit stops the clock and the counter outputs a binary number which is just the number of clock pulses.

The DAC could be:

- an integrator
- a resistor ladder
- a voltage reference

Problems with this system:

- a) control logic is complicated (use microprocessors + gates +...)
- b) time to digitize depends on V_{in} .

Example: suppose clock runs at 5 MHz, and you want 10 bit accuracy.

10 bits = 1024 clock pulses.

Can only digitize at about 5 kHz, *which is fairly slow!*

Successive Approximation ADC:


control logic is very complicated, but easy to program, like a binary search.
 conversion time is almost independent of V_{in} , very fast.

Example: 5 bit ADC:

The circuit:

outputs 0 when $V_{DAC} > V_{in}$ (steps 1, 2, 5)

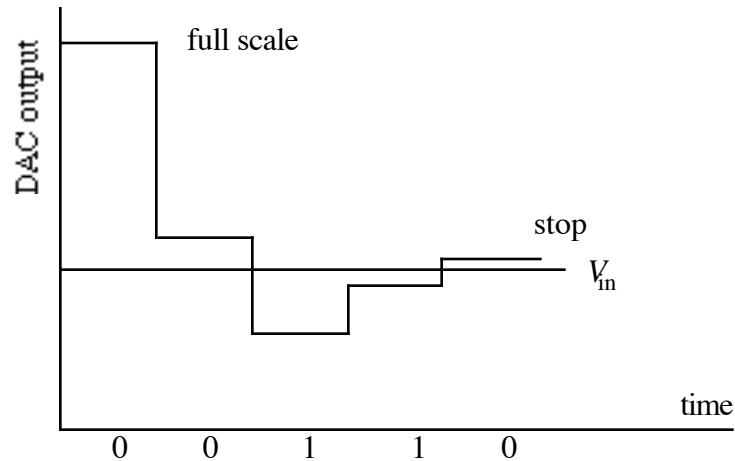outputs 1 when $V_{DAC} < V_{in}$ (steps 2, 3)



In order to convert V_{in} to a binary number the following steps are followed:

a) turn on MSB in DAC and compare with V_{in} .

0 if $V_{in} < \text{MSB}$

1 if $V_{in} > \text{MSB}$ (leave bit on if true)

b) turn on next highest bit, leave bit on if $V_{DAC} > V_{in}$.

c) repeat until least significant bit is checked (5 in this example).

Thus the method requires n comparisons for n bit accuracy.

Note: the staircase approach requires $2^n - 1$ comparisons

parallel ADC requires 1 step, independent of accuracy

Time for a 10 bit conversion for the three methods we have considered:

parallel : success Approx. : staircase 1:10:1023