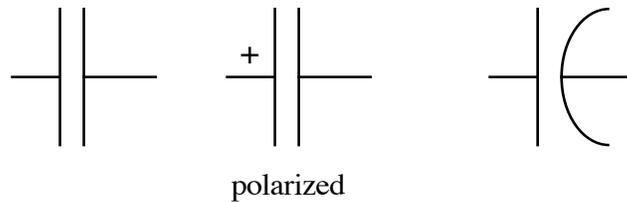


Capacitors and Inductors

1) Capacitance:

- Capacitance (C) is defined as the ratio of charge (Q) to voltage (V) on an object.
- Define capacitance by: $C = Q/V = \text{Coulombs/Volt} = \text{Farad}$.
- Capacitance of an object depends on geometry and its dielectric constant.
- Symbol(s) for capacitors:




- A capacitor is a device that stores electric charge (memory devices).
- A capacitor is a device that stores energy

$$E = \frac{Q^2}{2C}$$

- Capacitors are easy to fabricate in small sizes ($\square\text{m}$), use in chips.

Some Simple Capacitor circuits:

- Two capacitors in series:

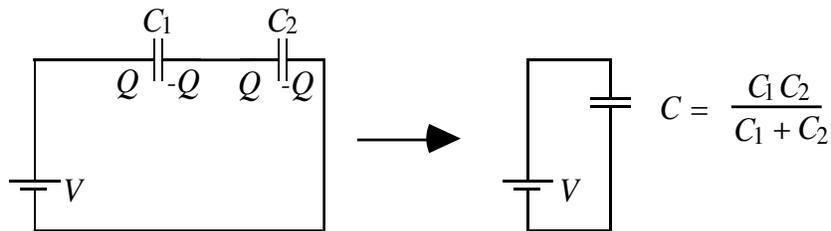


Apply Kirchhoff's law:

$$\begin{aligned} V &= V_1 + V_2 \\ &= \frac{Q}{C_1} + \frac{Q}{C_2} \\ &\equiv \frac{Q}{C_{tot}} \\ \frac{1}{C_{tot}} &= \frac{1}{C_1} + \frac{1}{C_2} = \square \frac{1}{C_i} \end{aligned}$$

i.e. capacitors in series add like resistors in parallel.

Note the *total* capacitance is *less* than the individual capacitance.

- Two capacitors in parallel:

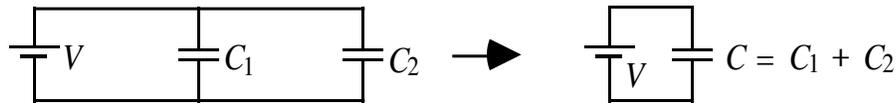

Again, use Kirchhoff's law:

$$V = \frac{Q_1}{C_1} = \frac{Q_2}{C_2}$$

The total charge in the circuit is:

$$\begin{aligned} Q &= Q_1 + Q_2 \\ &= V(C_1 + C_2) \\ &= VC_{tot} \end{aligned}$$

$$C_{tot} = C_1 + C_2 = \sum C_i$$

i.e. capacitors in parallel add like resistors in series.

Note the *total* capacitance is *more* than the individual capacitance.

Energy and Power in Capacitors

- How much energy is stored in a capacitor?

If a charge (Q) moves through a potential difference (V) the amount of energy (E) the charge gains or loses is:

$$E = Q \cdot V$$

If we consider the case of the capacitor where we add charge and keep the voltage constant, the change in energy is:

$$dE = V \cdot dQ$$

$$V = Q / C$$

$$dE = \frac{Q}{C} dQ$$

$$E = \int_0^Q \frac{Q}{C} dQ$$

$$E = \frac{Q^2}{2C} \text{ or } \frac{CV^2}{2}$$

Example: How much energy can a "typical" capacitor store?

Pick a 4 μ F Cap (it would read 4 mF) rated at 3 kV.

Then $E = 0.5 \cdot (4 \times 10^{-6}) \cdot (3 \times 10^3)^2 = 18$ Joules

This is the same as dropping a 2 kg weight (about 4 pounds) 1 meter.

- How much power is dissipated in a capacitor?

$$\begin{aligned} \text{Power} &= \frac{dE}{dt} \\ &= \frac{d}{dt} \left[\frac{CV^2}{2} \right] \\ P &= CV \frac{dV}{dt} \end{aligned}$$

Note: dV/dt must be finite otherwise we source (or sink) an infinite amount of power! THIS WOULD BE UNPHYSICAL!

Thus, the voltage across a capacitor cannot change instantaneously. This is a useful fact when trying to guess the transient (short term) behavior of a circuit.

However, the voltage across a resistor can change instantaneously as the power dissipated in a resistor does not depend on dV/dt ($P = I^2 \cdot R$ or V^2/R for a resistor).

- Why do capacitors come in such small values?

Example: Calculate the size of a 1 Farad parallel capacitor with air between the plates.

For a parallel plate capacitor:

$$C = \frac{k\epsilon_0 A}{d}$$

k = dielectric constant (= 1 for air)

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ N}^{-1} \text{ m}^{-2}$$


d = distance between plates (assumed 1 mm)

$$A = \text{area of plates} = 1.1 \times 10^8 \text{ m}^2!!!!$$

This corresponds to square plate *6.5 miles* per side! Thus 1 Farad capacitor is gigantic in size. However, breakthroughs in capacitor technologies (driven by the computer industries) allow the production of 0.5-5 F capacitors of small size (1-2 cm high) and low cost (< \$5).

- How small can we make capacitors?

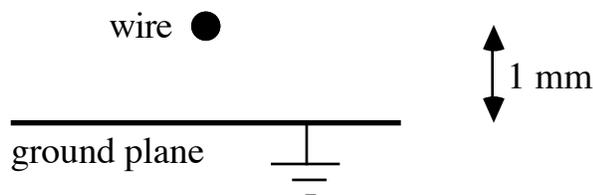A wire near a ground plane has $C \approx 0.1 \text{ pf} = 10^{-13} \text{ F}$.



- Some words to the wise on capacitors and their labeling.

Typical capacitors are multiples of microFarads (10^{-6} F) or picoFarads (10^{-12} F).


Caution: Whenever you see mF it almost always is micro, *not* milli F and *never* mega F.

picoFarad (10^{-12} F) is sometimes written as pf and pronounced *puff*.

There is no *single* convention for labeling capacitors. Many manufacturers have their own labeling scheme. See Horowitz and Hill lab manual for a discussion on this topic.

Resistors and Capacitors

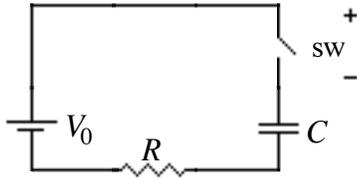- Examine voltage and current vs. time for a circuit with one R and one C .



Assume that at $t < 0$ all voltages are zero, $V_R = V_C = 0$.

At $t \geq 0$ the switch is closed and the battery (V_0) is connected.

Apply Kirchhoff's voltage rule:

$$V_0 = V_R + V_C$$

$$= IR + \frac{Q}{C}$$

$$= R \frac{dQ}{dt} + \frac{Q}{C}$$

Thus we have to solve a differential equation. For the case where we have a DC voltage (our example) it's easier to solve for the current (I) by differentiating both sides of above equation.

$$\frac{dV_0}{dt} = \frac{1}{C} \frac{dQ}{dt} + R \frac{d^2Q}{dt^2}$$

$$0 = \frac{I}{C} + R \frac{dI}{dt}$$

$$\frac{dI}{dt} = - \frac{I}{RC}$$

This is just an exponential decay equation with time constant RC (sec). The current as a function of time through the resistor and capacitor is:

$$I(t) = I_0 e^{-t/RC}$$

- What's $V_R(t)$?

By Ohm's law:


$$V_R(t) = I_R \cdot R$$

$$= I_0 R e^{-t/RC}$$

$$= V_0 e^{-t/RC}$$

At $t = 0$ all the voltage appears across the resistor, $V_R(0) = V_0$.

At $t = \infty$, $V_R(\infty) = 0$.

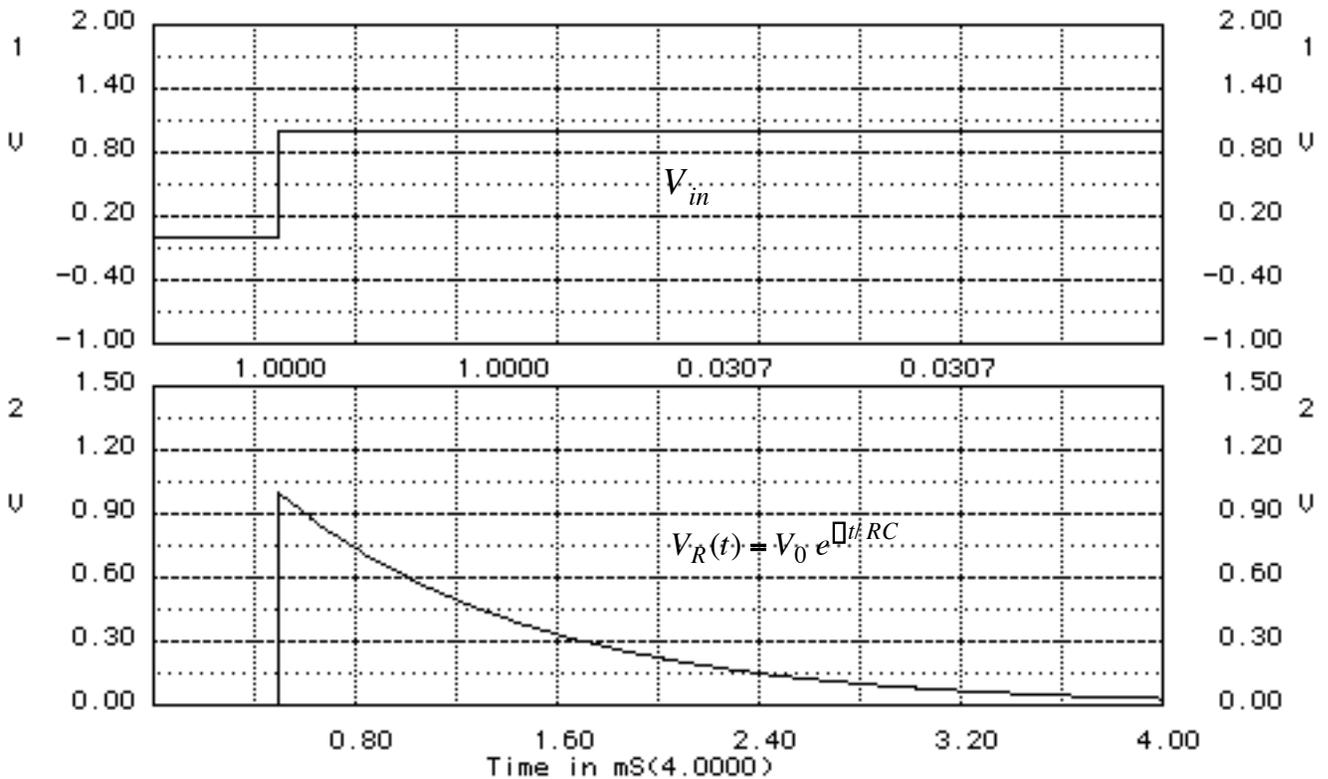

•What's $V_C(t)$?

Easiest way to answer is to use the fact that $V_0 = V_R + V_C$ is valid for all t .

$$V_C = V_0 - V_R$$

$$V_C = V_0 \left(1 - e^{-t/RC} \right)$$

At $t = 0$ all the voltage appears across the resistor so $V_C(0) = 0$.

At $t = \infty$, $V_C(\infty) = V_0$.

•Suppose we wait until $I = 0$ and then short out the battery.

We now have

$$0 = V_R + V_C$$

$$V_R = -V_C$$

$$R \frac{dQ}{dt} = -\frac{Q}{C}$$

$$\frac{dQ}{dt} = -\frac{Q}{RC}$$

Solving the exponential equation yields,


$$Q(t) = Q_0 e^{-t/RC}$$

We can find V_C using $V = Q / C$,

$$V_C(t) = V_0 e^{-t/RC}$$

Finally we can the voltage across the resistor using $V_R = -V_C$,

$$V_R(t) = -V_0 e^{-t/RC}$$

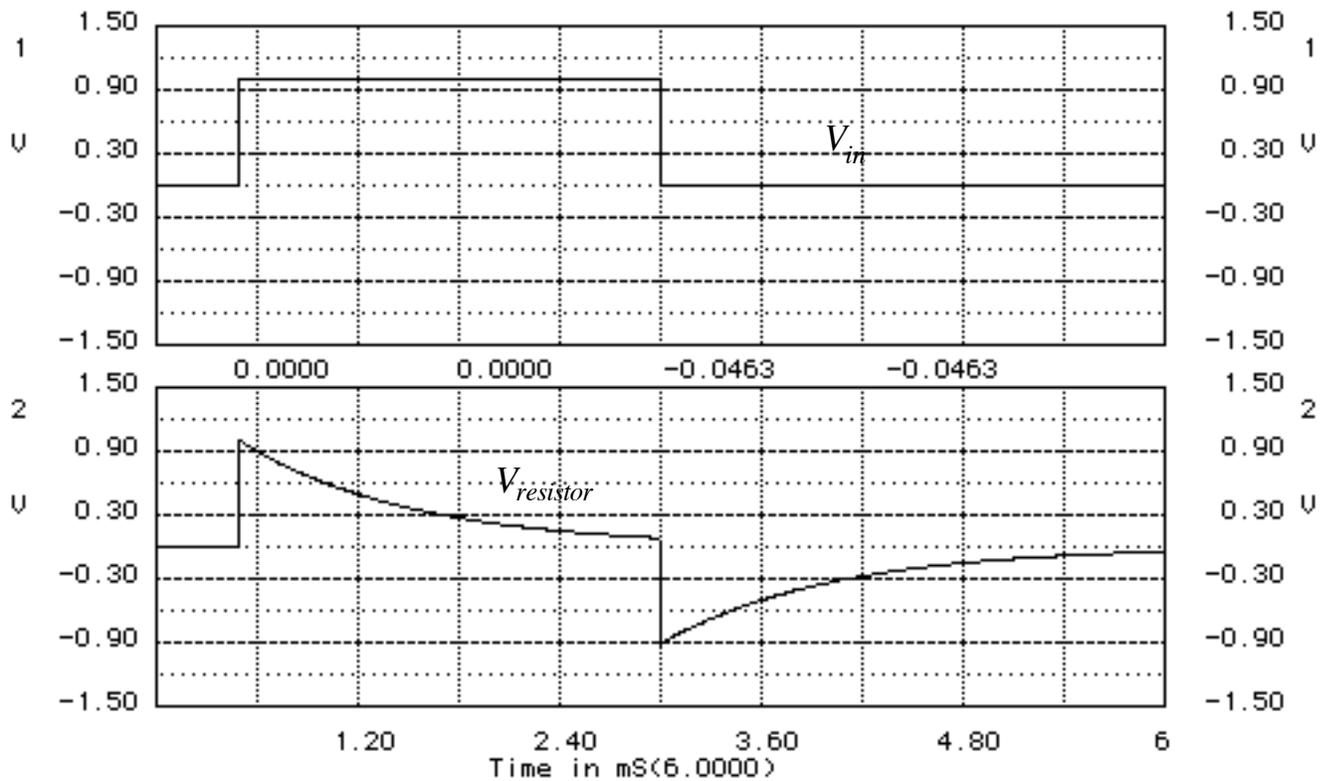

• Suppose $V(t) = V_0 \sin \omega t$ instead of DC, what happens to V_C and I_C ?

$$Q(t) = CV(t)$$

$$= CV_0 \sin \omega t$$

$$I_C = dQ / dt$$

$$= \omega CV_0 \cos \omega t$$

$$= \omega CV_0 \sin(\omega t + \pi / 2)$$

The current in the capacitor varies like a sine wave too, but it is 90° out of phase with the voltage.

We can write an equation that looks like Ohm's law by defining V^* :

$$V^* = V_0 \sin(\omega t + \pi / 2)$$

Then the relationship between the voltage and current in C looks like:

$$V^* = I_C / \omega C$$

$$= I_C R^*$$


Indeed $1/\omega C$ can be identified as a kind of resistance. We call it capacitive reactance, X_C :

$$X_C \equiv 1/\omega C \text{ (Ohms)}, X_C = 0 \text{ if } \omega = \infty \text{ and } X_C = \infty \text{ if } \omega = 0.$$

Thus at high frequencies a capacitor looks like a short circuit, while at low frequencies a capacitor looks like an open circuit (high resistance).

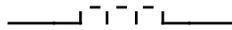2) Inductance:

- Define inductance by: $V = L dI / dt$, unit = Henry.
- Electric component commonly called inductors.
- Symbol(s) for inductor:



- Useful circuit element that provides a voltage proportional to dI/dt .
- An inductor is a device that stores energy

$$E = \frac{1}{2} LI^2$$

- Inductors are usually made from a coil of wire. They tend to be bulky and are hard to fabricate in small sizes (μm), not used in chips.
- Two inductors next to each other (transformer) can step up or down a voltage without changing the frequency of the voltage. Also provide isolation from the rest of the circuit.

Energy and Power in Inductors

- How much energy is stored in an inductor?

$$dE = VdQ$$

$$I = \frac{dQ}{dt}$$

$$dE = VI dt$$

$$V = L \frac{dI}{dt}$$

$$dE = LI dI$$

$$E = L \int_0^I dI$$

$$E = \frac{1}{2} LI^2$$

- How much power is dissipated in an inductor?

$$Power = \frac{dE}{dt}$$


$$= \frac{d}{dt} \left[\frac{LI^2}{2} \right]$$

$$P = LI \frac{dI}{dt}$$

Note: dI/dt must be finite otherwise we source (or sink) an infinite amount of power in an inductor!
THIS WOULD BE UNPHYSICAL.

Thus the *current* across an inductor cannot change *instantaneously*.

- Two inductors in series:

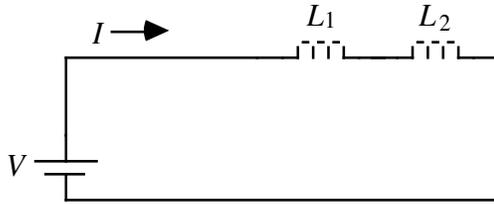


Apply Kirchhoff's Laws,

$$\begin{aligned}
 V &= V_1 + V_2 \\
 &= L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt} \\
 &\equiv L_{tot} \frac{dI}{dt} \\
 L_{tot} &= L_1 + L_2 \\
 &= \sum L_i
 \end{aligned}$$

Inductors in series add like resistors in series.

Note the *total* inductance is *greater* than the individual inductances.

- Two inductors in parallel:

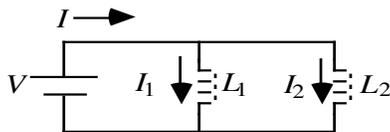

Since the inductors are in parallel,

$$V_1 = V_2 = V$$

The total current in the circuit is

$$\begin{aligned}
 I &= I_1 + I_2 \\
 \frac{dI}{dt} &= \frac{dI_1}{dt} + \frac{dI_2}{dt} \\
 &= \frac{V}{L_1} + \frac{V}{L_2} \\
 &\equiv \frac{V}{L_{tot}} \\
 \frac{1}{L_{tot}} &= \frac{1}{L_1} + \frac{1}{L_2} \\
 L_{tot} &= \frac{L_1 L_2}{L_1 + L_2}
 \end{aligned}$$

If we have more than 2 inductors in parallel, they combine like:

$$\frac{1}{L_{tot}} = \sum \frac{1}{L_i}$$

Inductors in parallel add like resistors in parallel.


Note: the *total* inductance is *less* than the individual inductances.

Resistors and Inductors

- Examine voltage and current versus time for a circuit with one R and one L .

Assume that at $t < 0$ all voltages are zero, $V_R = V_L = 0$.

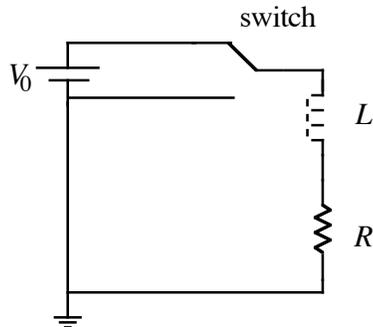At $t \geq 0$ the switch is closed and the battery (V_0) is connected.



Like the capacitor case, apply Kirchhoff's voltage rule:

$$\begin{aligned} V_0 &= V_R + V_L \\ &= IR + L \frac{dI}{dt} \end{aligned}$$

Solving the differential equation, assuming at $t = 0$, $I = 0$:

$$I(t) = \frac{V_0}{R} \left(1 - e^{-tR/L} \right)$$

This is just an exponential decay equation with time constant L/R (seconds).

- What's $V_R(t)$?

By Ohm's law $V_R = I_R R$ at any time:

$$V_R = I(t)R = V_0 \left(1 - e^{-tR/L} \right)$$

At $t = 0$, none of the voltage appears across the resistor, $V_R(0) = 0$.

At $t = \infty$, $V_R(\infty) = V_0$.

- What's $V_L(t)$?

Easiest way to answer is to use the fact that $V_0 = V_R + V_L$ is valid for all t .


$$V_L = V_0 - V_R$$

$$V_L(t) = V_0 e^{-tR/L}$$

At $t = 0$, all the voltage appears across the inductor so $V_L(0) = V_0$.

At $t = \infty$, $V_L(\infty) = 0$.

Pick $L/R = 1$ millisecond:

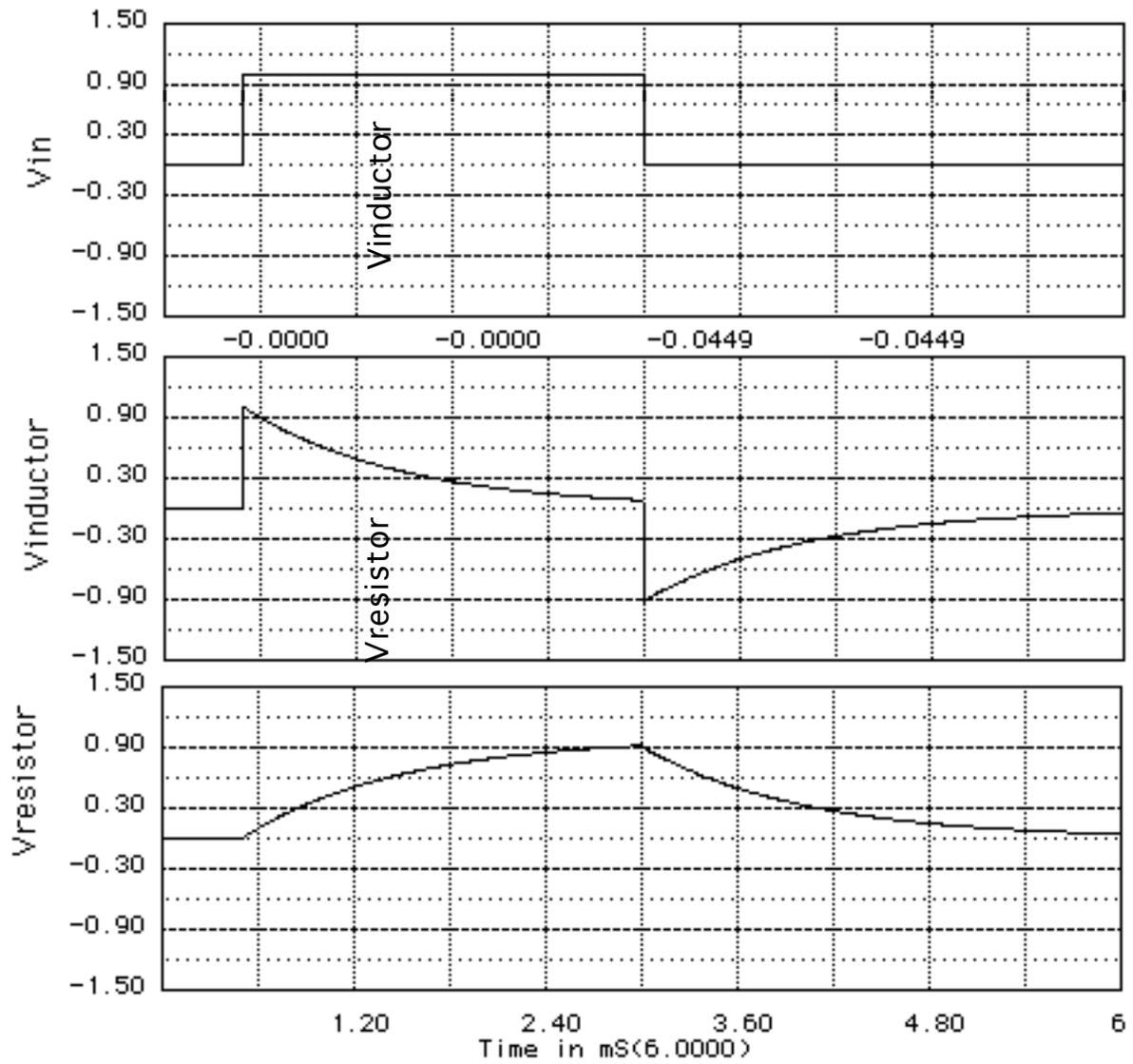

- Suppose $V(t) = V_0 \sin \omega t$ instead of DC, what happens to V_L and I_L ?

$$V = L \frac{dI_L}{dt}$$

$$I_L = \frac{1}{L} \int V dt$$

$$= \frac{1}{L} \frac{V_0}{\omega} \cos \omega t$$

$$I_L(t) = \frac{V_0}{\omega L} \sin(\omega t - \pi/2)$$

The current in an inductor varies like a sine wave too, but it is 90° out of phase with the voltage.

We can write an equation that looks like Ohm's law by defining V^* :

$$V^* = V_0 \sin(\omega t - \pi/2)$$

Then the relationship between the voltage and current in L looks like:

$$V^* = I_L \omega L = I_L R^*$$

Indeed, ωL can be identified as a kind of resistance. We call it inductive reactance, X_L :

$$X_L \equiv \omega L \text{ (Ohms)}, \quad X_L = 0 \text{ if } \omega = 0 \text{ and } X_L = \infty \text{ if } \omega = \infty.$$

Thus at high frequencies an inductor looks like an open circuit, while at low frequencies an inductor looks like a short circuit (low resistance).

- Some things to remember about R , L , and C 's.

For DC circuits, after many time constants (L/R or RC):

Inductor acts like a wire (0Ω).

Capacitor acts like an open circuit ($\infty \Omega$).

For circuits where the voltage changes very rapidly or transient behavior:

Capacitor acts like a wire (0Ω).

Inductor acts like an open circuit ($\infty \Omega$).

Example, RLC circuit with DC supply:

At $t = 0$, voltages on R , C are zero and $V_L = V_0$.

At $t = \infty$, voltages on R , L are zero and $V_C = V_0$.

