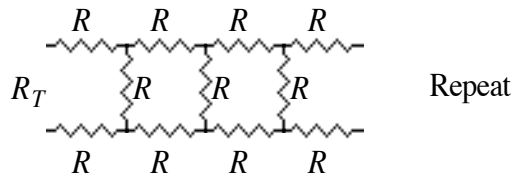


Physics 517/617 HOMEWORK 1
Due 7/5/2005

- 1) Simpson P47 problem 4.
- 2) Simpson P47 problem 11.
- 3) Simpson P48 problem 14.
- 4) Simpson P49 problem 17.
- 5) Simpson P50 problem 28.
- 6) Simpson P50 problem 30.
- 7) Simpson P52 problem 42. What's the largest value R can be if we want the voltmeter to always be within 10% of the correct voltage?

Additional problems for Physics 617:

- 8) Show that the resistance of this infinite network of resistors is:
 $R_T = (1+\sqrt{3})R$ with R_T the resistance looking into the network.



- 9) Find the current going through each resistor and the voltage drop across each resistor. The resistor values are in Ohms.

