

## QUIZ #5

25 points, 18 minutes


SCORE \_\_\_\_\_

$$\vec{E} = \rho \vec{J} \quad R = \rho L / A \quad J = i/A \quad \vec{J} = (ne) \vec{v}_d \quad i = \frac{dq}{dt} \quad V = iR \quad e = 1.6 \times 10^{-19} \text{ C}$$

(1) [15 points]. In the circuit given in the figure:

 $E = 100 \text{ V}$ ,  $R_1 = 100 \Omega$ ,  $R_2 = 100 \Omega$ ,  $R_3 = 400 \Omega$ , and  $R = 600 \Omega$ .

- Find  $i$  = the current supplied by the battery.
- $V_3$  = the voltage across  $R_3$ .
- $i_1$  = the current through  $R_1$ .

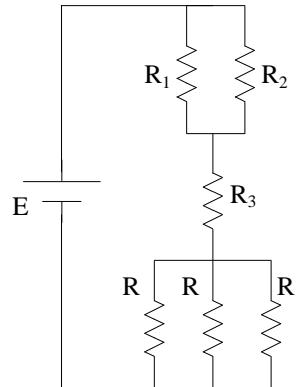(2) [10 points]. A conductor is in the shape of a cylinder of length 5.0 mm and radius 1.0 mm. A current is flowing through it with current density magnitude  $5.0 \times 10^5 \text{ A/m}^2$ . The conductor has resistivity  $3.0 \times 10^{-2} \Omega\text{m}$ . What is the voltage across the conductor?